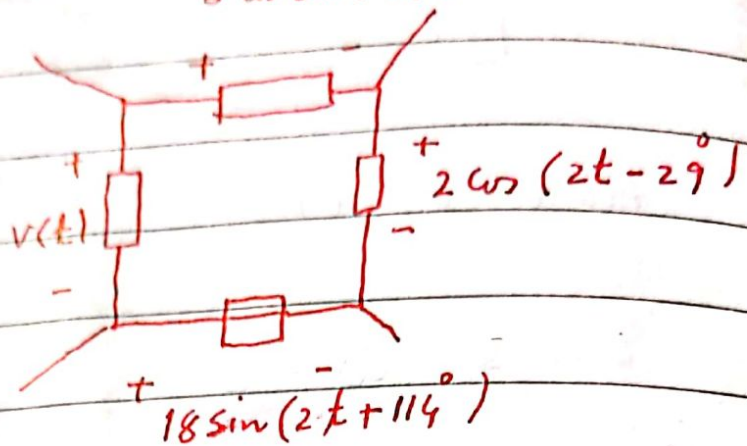


① Find $v(t)$ $6 \cos(2t + 17^\circ)$




$$\bar{V} = 6 \angle 17^\circ + 2 \angle -29^\circ + 18 \angle 114^\circ$$

$$\bar{V} = 11.09 \angle -143.9^\circ$$

$$\therefore v(t) = 11.09 \cos(2t - 143.9^\circ)$$

② Find $i(t)$

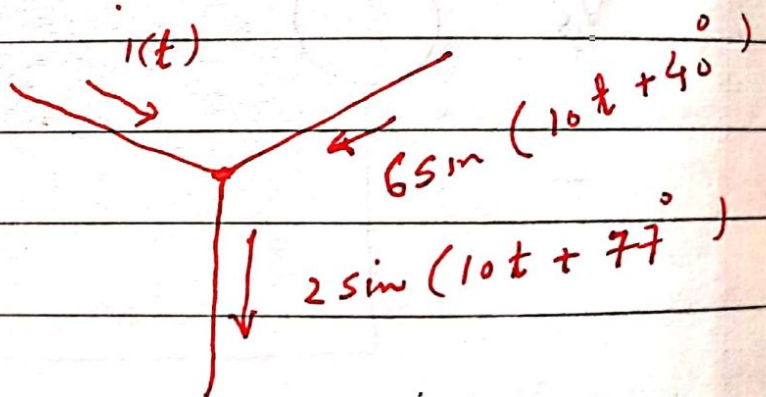




$$\bar{I} = -6 \angle 40^\circ + 2 \angle 77^\circ$$

$$\bar{I} = 4.56 \angle 114.7^\circ + 90^\circ$$

$$= 4.56 \sin(10t + 204.7^\circ)$$

$$\begin{aligned} \bar{I} &= -8 \angle -50^\circ + 2 \angle -13^\circ \\ &= 4.56 \angle 114.7^\circ \text{ A} \\ i(t) &= 4.56 \cos(10t + 114.7^\circ) \text{ A} \end{aligned}$$

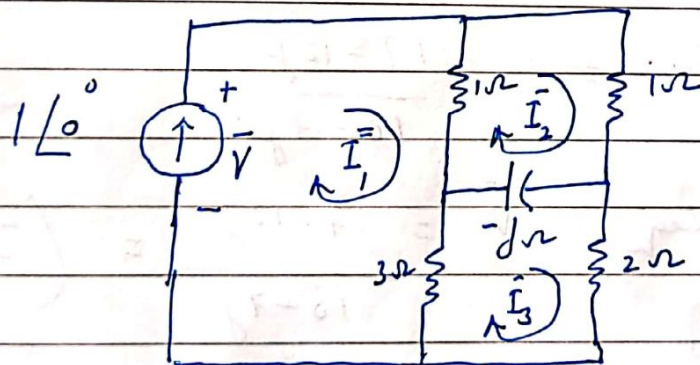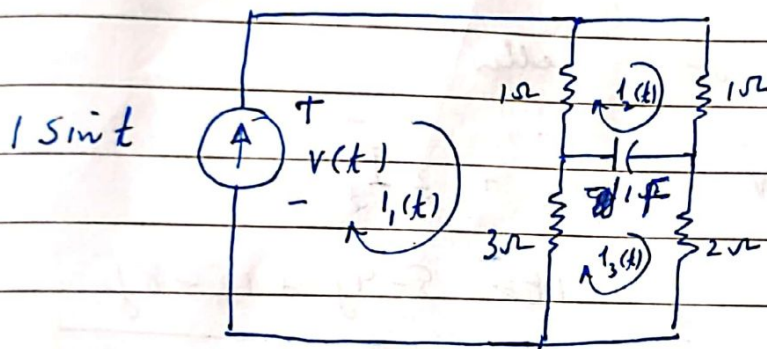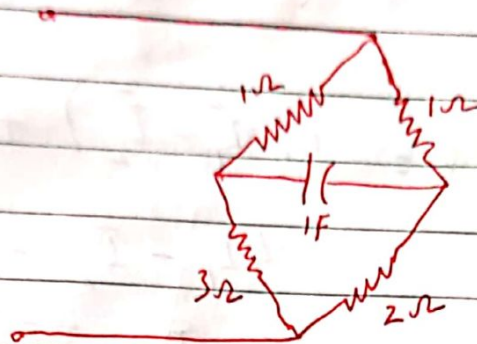3) What is the impedance looking into this two-terminal network at $\omega = 1 \text{ rad/s}$?



$$\bar{I}_1 = 1 \angle 0^\circ$$

$$-\bar{I}_1 + (2 - j)\bar{I}_2 + j\bar{I}_3 = 0$$

$$(2 - j)\bar{I}_2 + j\bar{I}_3 = 1 \angle 0^\circ \quad \text{--- (1)}$$

$$-3\bar{I}_1 + j\bar{I}_2 + (5-j)\bar{I}_3 = 0$$

$$j\bar{I}_2 + (5-j)\bar{I}_3 = 3\angle 0^\circ$$

$$\bar{I}_2 = \left(\frac{5-4j}{10-7j} \right), \quad \bar{I}_3 = \left(\frac{6-4j}{10-7j} \right)$$

$$\begin{aligned} \checkmark \left[\begin{aligned} \bar{V} &= 1(\bar{I}_1 - \bar{I}_2) + 3(\bar{I}_1 - \bar{I}_3) \\ &= 4\bar{I}_1 - \bar{I}_2 - 3\bar{I}_3 \\ &= 4 - \bar{I}_2 - 3\bar{I}_3 \end{aligned} \right. \end{aligned}$$

or better


$$\bar{V} = \bar{I}_2 + 2\bar{I}_3$$

$$= \frac{5-4j + 12-8j}{10-7j}$$


$$= \frac{17-12j}{10-7j}$$

$$\therefore Z_{eq} = \bar{V} = \frac{17-12j}{10-7j} = \left(\frac{254-j}{199} \right) \Omega$$

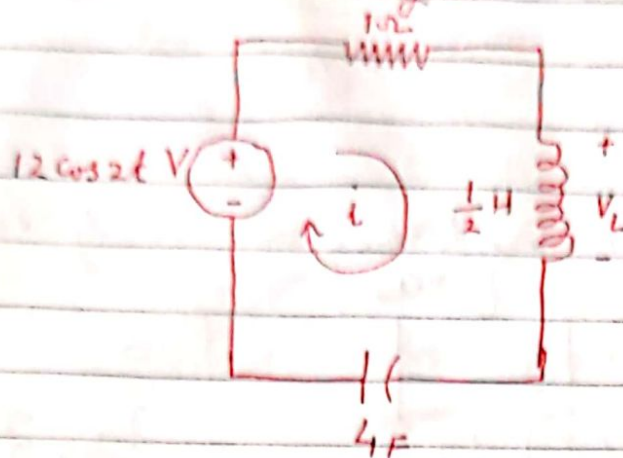- (4) Find ac steady-state value of $v_L(t)$ and $i(t)$



Phasor equivalent ckt. :

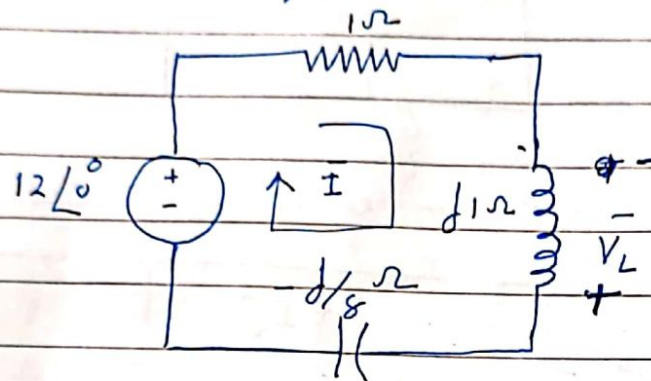

$$\vec{V}_L = \frac{-j}{1 + j\left(1 - \frac{1}{8}\right)} \times 12 \angle 0^\circ$$

$$= \frac{-j}{1 + j\frac{7}{8}} \times 12 \angle 0^\circ$$

$$= \frac{8j}{8 + j7} \times 12 \angle 90^\circ$$


$$= \frac{96 \angle -90^\circ}{\sqrt{64 + 49} \angle \tan^{-1} \frac{7}{8}}$$

$$= 9.03 \angle -131.2^\circ$$


$$\therefore v_L(t) = 9.03 \cos(2t - 131.2^\circ)$$

$$\bar{I} = \frac{12 \angle 0^\circ}{1 + j7/8} = 9.03 \angle -41.12^\circ$$

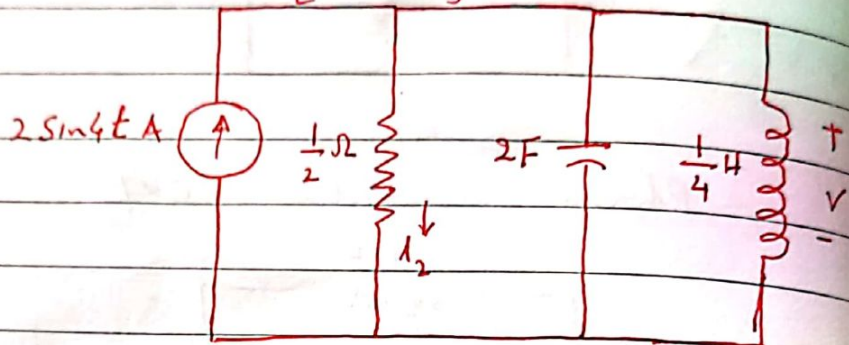5) Find $\{ i_r(t) \}$ in steady state
& $\{ v(t) \}$



Phasor equivalent ckt.:

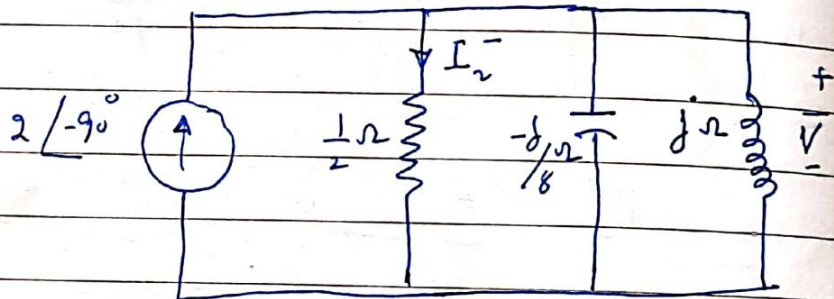

$$\bar{I}_r = \frac{1/1/2}{2 + j8 - j} \times 2 \angle -90^\circ$$

$$= \left(\frac{2}{2 + j7} \right) \angle -90^\circ$$

$$= 0.55 \angle -164.1^\circ$$

$$\therefore \bar{V} = \frac{\bar{I}_r}{2} = 0.275 \angle -164.1^\circ$$


$$\therefore i_p(t) = 0.55 \cos(4t - 164.1^\circ)$$

$$\text{and } v(t) = 0.27 \cos(4t - 164.1^\circ)$$

6) Use superposition to find the output voltage $v_o(t)$ in the following circuit

$$i_s(t) = 100 \cos(10,000t) \text{ mA and}$$


$$v_s(t) = 20 \cos(20,000t - 45^\circ)$$

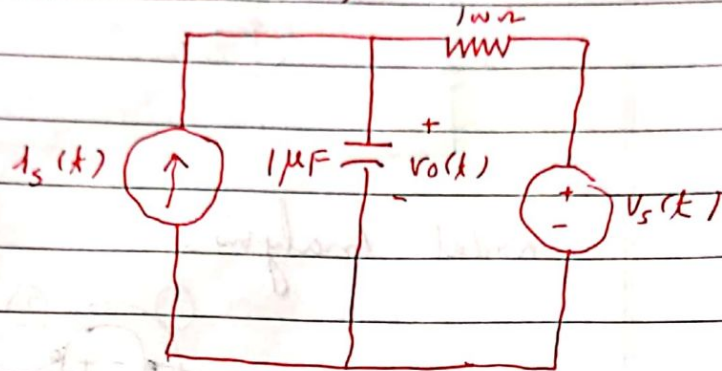

$$v_o(t) = 7.07 \cos(10kt - 45^\circ) + 8.94 \cos(20kt - 108.4^\circ) \text{ V}$$

7) Find the phasor current \bar{I}_x


Two sources have same frequency

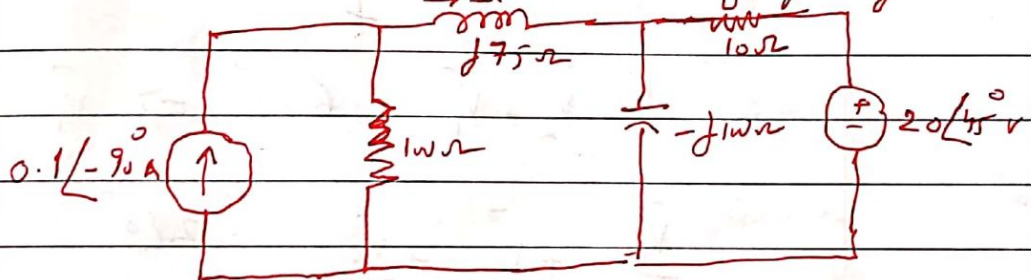


$$\bar{I}_x = 0.206 \angle -158^\circ \text{ A}$$

(8) Find current \bar{I} using:

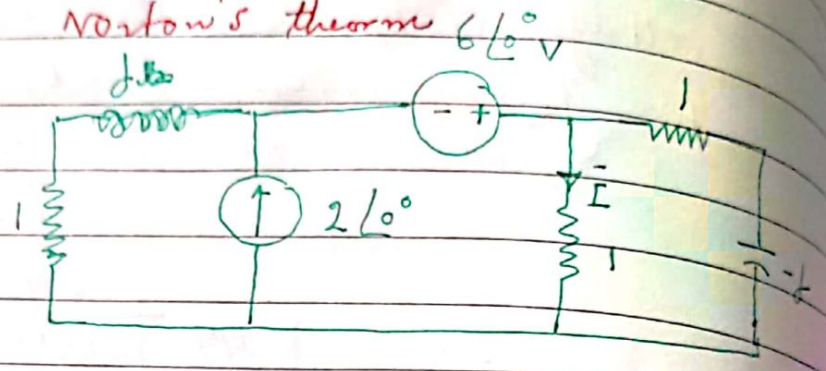- 1) Nodal Analysis
- 2) Mesh Analysis
- 3) Superposition theorem
- 4) Thevenin's theorem
- 5) Norton's theorem



Nodal Analysis:

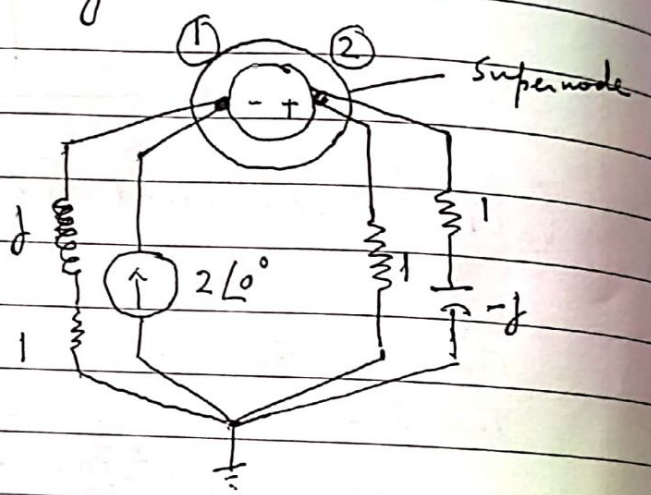

$$\bar{V}_2 - \bar{V}_1 = 6\angle 0^\circ \Rightarrow \bar{V}_1 = \bar{V}_2 - 6\angle 0^\circ$$

$$\frac{\bar{V}_1}{j+1} + \frac{\bar{V}_2}{1} + \frac{\bar{V}_2}{1-j} = 2\angle 0^\circ$$

$$\bar{V}_2 \left[1 + \frac{1}{1-j} \right] + \frac{\bar{V}_2 - 6\angle 0^\circ}{j+1} = 2\angle 0^\circ$$

$$\bar{V}_2 \left[\frac{1-j+1}{1-j} \right] + \frac{\bar{V}_2 - 6}{1+j} = 2$$

$$V_2 \left[\frac{2-j}{2} \right] (1+j) + \frac{\bar{V}_2 - 6}{2} (1-j) = 2$$

$$\bar{V}_2 [2+j-j+1] + \bar{V}_2 - 6 + 6j = 4$$


$$3\bar{V}_2 + \bar{V}_2 = 10 - 6j$$

$$4\bar{V}_2 = 10 - 6j$$

$$\bar{V}_2 = \frac{5 - 3j}{2}$$

$$\bar{I} = \frac{5 - 3j}{2}$$

Mesh Analysis:

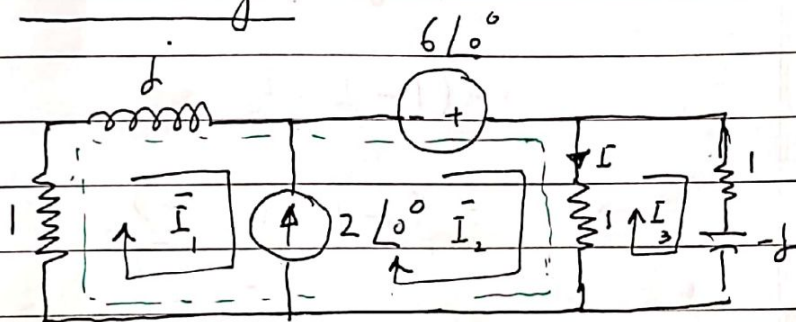

$$-\bar{I}_1 + \bar{I}_2 = 2 \angle 0^\circ \quad \text{Constraint equation}$$

$$-\bar{I}_2 + (2-j)\bar{I}_3 = 0 \quad \text{essential loop}$$

$$(1+j)\bar{I}_1 + (\bar{I}_2 - \bar{I}_3) = 6 \angle 0^\circ \quad \text{Superloop}$$

$$\bar{I}_1 = \bar{I}_2 - 2 \angle 0^\circ$$

$$-\bar{I}_2 + (2-j)\bar{I}_3 = 0 \quad \text{--- (1)}$$

$$(1+j)[\bar{I}_2 - 2] + (\bar{I}_2 - \bar{I}_3) = 6$$

$$\bar{I}_2 - 2 + j\bar{I}_2 - 2j + \bar{I}_2 - \bar{I}_3 = 6$$

$$(2+j)\bar{I}_2 - \bar{I}_3 = 8+2j \quad \text{--- (ii)}$$

↓

$$(2+j)(2-j)\bar{I}_3 - \bar{I}_3 = 8+2j$$

$$4-2j\bar{I}_3 + 2j\bar{I}_3 - \bar{I}_3 = 8+2j$$

$$-2j\bar{I}_3 = 4-2j$$

$$(4+1)\bar{I}_3 - \bar{I}_3 = 8+2j$$

$$4\bar{I}_3 = 8+2j$$

$$\bar{I}_3 = \left(\frac{4+j}{2}\right)$$

$$\bar{I} = \bar{I}_2 - \bar{I}_3$$

$$= (2-j)\bar{I}_3 - \bar{I}_3$$


$$= (1-j)\bar{I}_3$$

$$= (1-j)\left(\frac{4+j}{2}\right)$$

$$= \frac{4+j-4j+1}{2}$$

$$\bar{I} = \frac{5-3j}{2}$$

Superposition

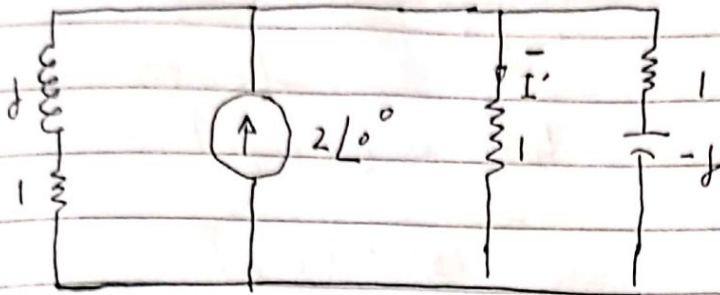


$$\bar{I}' = \left(\frac{\frac{1}{1}}{\frac{1}{1+j} + 1 + \frac{1}{1-j}} \right) 2\angle 0^\circ$$

$$= 2\angle 0^\circ$$

$$\frac{2 + \frac{1-j}{2} + 1+j}{2}$$
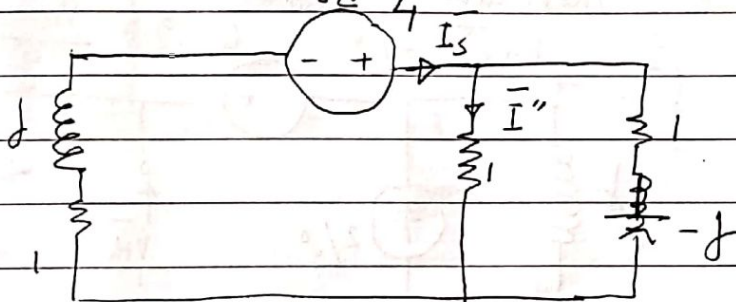
$$= \frac{4\angle 0^\circ}{6\angle 0^\circ} = 1\angle 0^\circ$$



$$I'' = \left(\frac{1-j}{2-j} \right) \bar{I}_s$$

$$\bar{I}_s = \left(\frac{2-j}{1-j} \right) I''$$

KVL:

$$\left(\frac{2-j}{1-j} \right) (1+j) I'' + I'' = 6\angle 0^\circ$$

$$\left[\frac{2 + 2j - j + 1 + 1 - j}{(1-j)} \right] \bar{I}'' = 6$$

$$4\bar{I}'' = 6(1-j)$$


$$\bar{I}'' = \frac{3}{2}(1-j)$$

$$\bar{I} = 1 + \frac{3}{2}(1-j)$$

$$= \frac{2 + 3 - 3j}{2}$$

$$\bar{I} = \frac{5 - 3j}{2}$$

Therem's theorem :

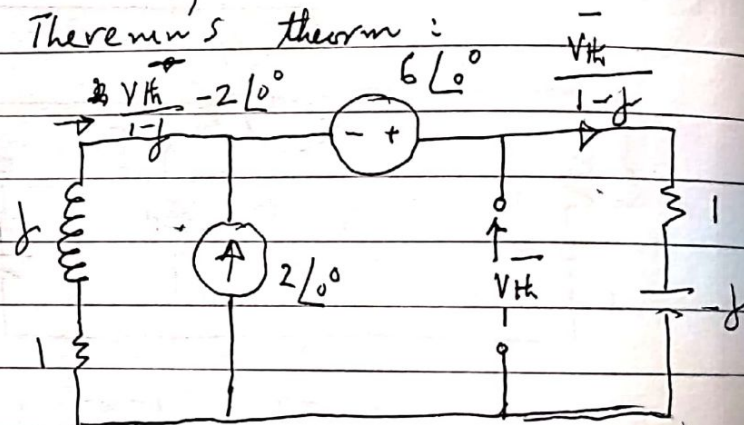

$$(1+j) \left(\frac{V_{th}}{1-j} - 2 \right) + V_{th} = 6\angle 0^\circ$$

$$(1+j) \frac{V_{th}}{2} + V_{th} = 6$$

$$2 + 2(1+j)$$

$$\frac{(1+2j-1)\bar{v}_{th}}{2} + \bar{v}_{th} = 6 + 2 + 2j$$

$$(2+2j)\bar{v}_{th} = 12 + 4 + 4j$$


$$\bar{v}_{th} = \frac{16+4j}{2(1+j)}$$

$$= \frac{8+2j}{1+j}$$


$$= \frac{(8+2j)(1-j)}{1+j(1-j)}$$

$$Z_{th} = \frac{(1-j)(1+j)}{2}$$
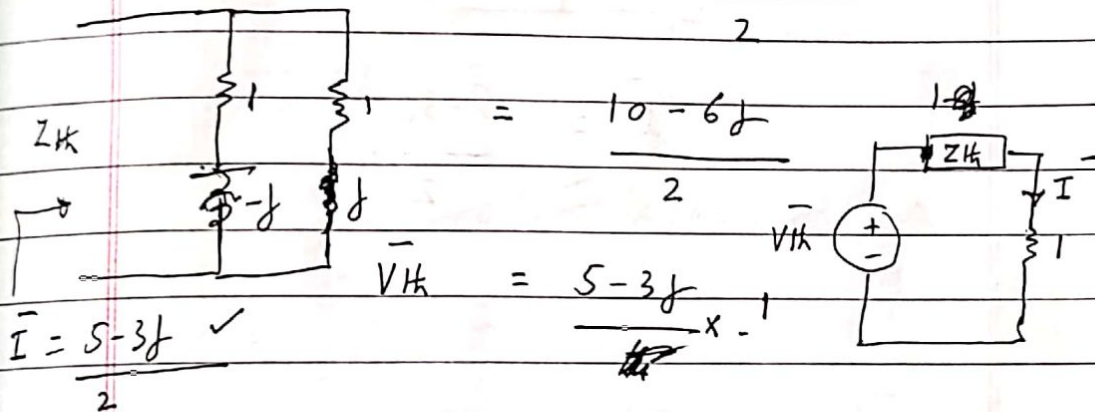
$$= \frac{1+1}{2} = 1 = \frac{8-8j+2j+2}{2}$$



Norton's theorem $6\angle 0^\circ$

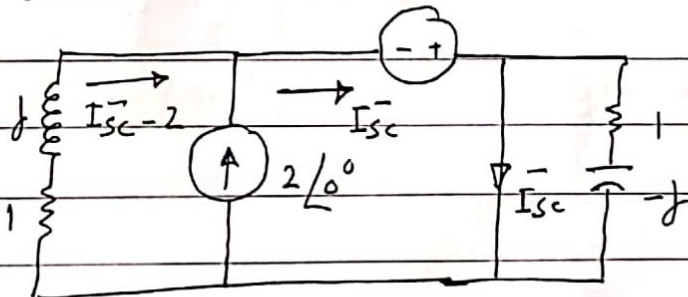

KVL:

$$(1+j)(\bar{I}_{sc}-2) = 6\angle 0^\circ$$

$$\bar{I}_{sc} - 2 + j\bar{I}_{sc} - 2j = 6$$


$$(1+j)\bar{I}_{sc} = 8+2j$$

$$\bar{I}_{sc} = \frac{8+2j}{1+j} = \frac{(8+2j)(1-j)}{2}$$

$$= \frac{8-8j+2j+2}{2}$$

$$= \frac{10-6j}{2}$$


$$= 5-3j$$

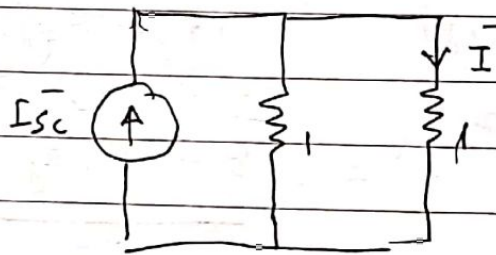

$$\bar{I} = \frac{5-3j}{2}$$


Problem:

2000 μF

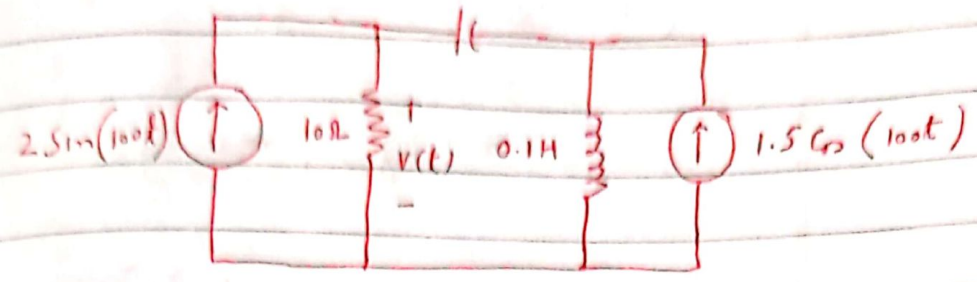

Find $V(t)$ using various methods.

Phasor equivalent circuit:

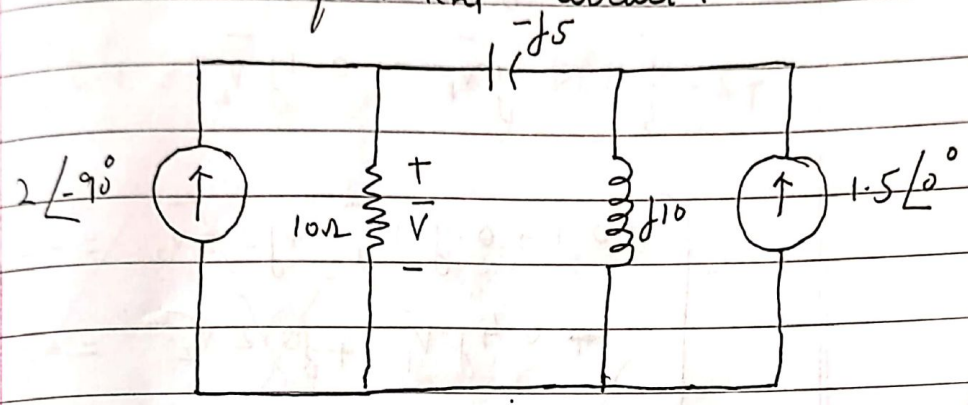


$$X_C = \frac{-j \times 10^6}{100 \times 2000} = -j5$$

$$X_L = j \times 2000 \times 10^{-6} \times 100 \times 0.1 \Omega$$

$$= 10j \Omega$$

Node Analysis

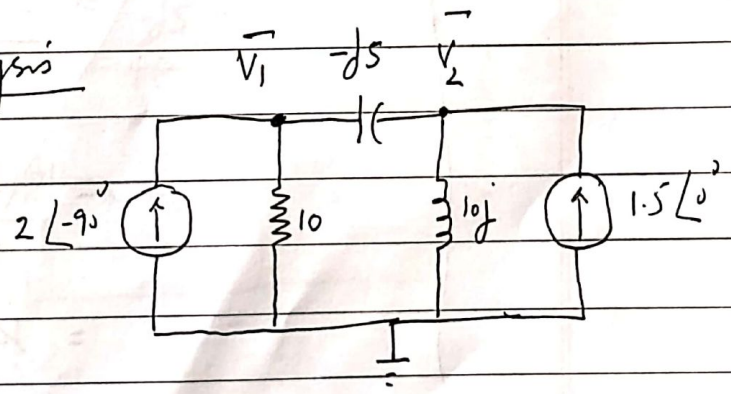

$$\frac{V_1}{10} + \frac{V_1 - V_2}{-j5} =$$

$$\left(\frac{1}{10} + \frac{1}{-j5}\right) \bar{V}_1 + \frac{\bar{V}_2}{j5} = -2j$$

$$(0.1 + 0.2j) \bar{V}_1 + 0.2j \bar{V}_2 = -2j \quad \text{--- (1)}$$

$$\frac{\bar{V}_1}{j5} + \left(\frac{1}{10j} - \frac{1}{j5}\right) \bar{V}_2 = 1.5$$

$$-0.2j \bar{V}_1 + (0.2j - 0.1j) \bar{V}_2 = 1.5$$

$$+2 \times \left[-0.2j \bar{V}_1 + 0.1j \bar{V}_2 = 1.5\right] \quad \text{--- (2)}$$

$$(0.1 + j0.2) \bar{V}_1 - j0.2 \bar{V}_2 = -j2 \quad \text{--- (1)}$$

$$2 \left[\begin{aligned} -j0.2 \bar{V}_1 + j0.1 \bar{V}_2 &= 1.5 \\ -j0.4 \bar{V}_1 + j0.2 \bar{V}_2 &= 3 \end{aligned} \right] \quad \text{--- (2)}$$

$$(0.1 - j0.2) \bar{V}_1 = 3 - j2$$

$$\bar{V}_1 = \frac{(3 - j2) 10}{1 - j2}$$

$$= \frac{10}{2} (3 - j2)(1 + j2)$$

$$= 2 [3 + j6 - j2 + 4]$$


$$= 14 + j8$$

$$= 16.1 \angle 29.7^\circ \quad \text{check}$$

$$v(t) = 16.1 \cos(100t + 29.7^\circ) \quad \checkmark$$

$$16.1245 \cos(100t + 29.7449^\circ)$$

Mesh analysis:

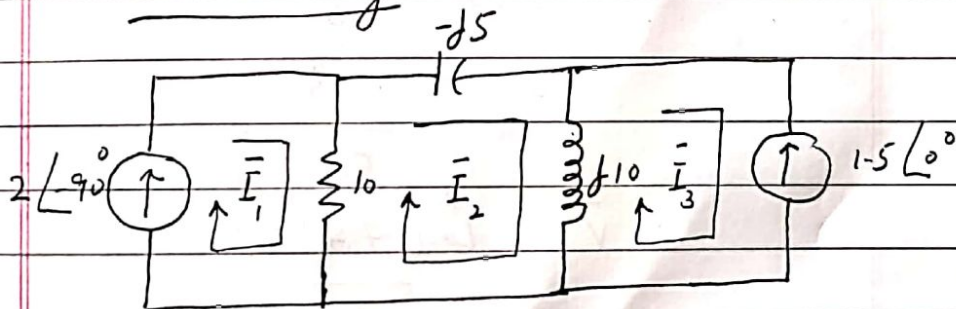

$$\bar{I}_1 = 2 \angle -90^\circ = -j2 \quad \text{--- (1)}$$

$$\bar{I}_3 = -1.5 \angle 0^\circ = -1.5 \quad \text{--- (2)}$$

$$-10 \bar{I}_1 + (10 + j5) \bar{I}_2 - j10 \bar{I}_3 = 0 \quad \text{(3)}$$

from (3)

$$\cancel{j20} - \cancel{j20} + 10 - j10\bar{I}_2 = 0$$

$$j20 + (10 + j5)\bar{I}_2 + j15 = 0$$

$$(10 + j5)\bar{I}_2 = -j35$$

$$(2 + j)\bar{I}_2 = -j7$$

$$\bar{I}_2 = \frac{-j7}{2+j}$$

$$\therefore \bar{I} = \bar{I}_1 - \bar{I}_2$$

$$= -2j + \frac{j7}{2+j}$$

$$= \frac{-4j + 2 + j7}{2+j}$$

$$= \frac{(2+j3)j}{(2+j)}$$

$$= \frac{(2+j3)(2-j)}{5}$$

$$= \frac{4 + j6 - 2j + 3}{5}$$


$$= \frac{7 + j4}{5}$$

$$\therefore \bar{V} = 10 \frac{7 + j4}{5}$$

$$= 14 + j8$$

$$\bar{V} = 16.1 \angle 29.7^\circ$$


$$v(t) = 16.1 \cos(100t + 29.7^\circ)$$

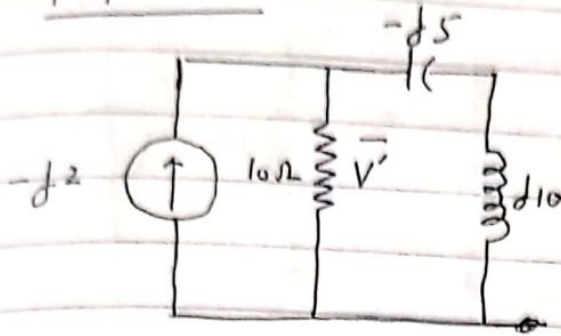Superposition theorem

$$\bar{V}' = \left(\frac{j5}{10 + j5} \right) \times -j2 \times 10$$

current division
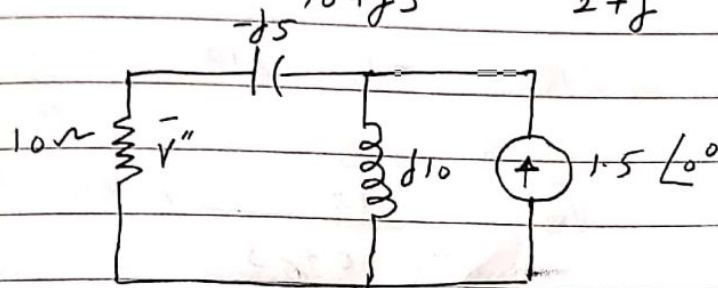
$$= \frac{100}{10 + j5} = \frac{20}{2 + j}$$



$$\bar{V}'' = \left(\frac{j10}{10 - j5 + j10} \right) 1.5 \times 10$$

current division


$$= \frac{j150}{10 + j5} = \frac{j30}{2 + j}$$

$$\bar{V} = \frac{20 + j30}{2 + j} = \frac{(20 + j30)(2 - j)}{5}$$

$$= \frac{40 + j60 - 20j + 30}{5}$$

$$= \frac{70 + j40}{5} = 14 + j8$$

$$= 16.1 / 29.7^\circ$$

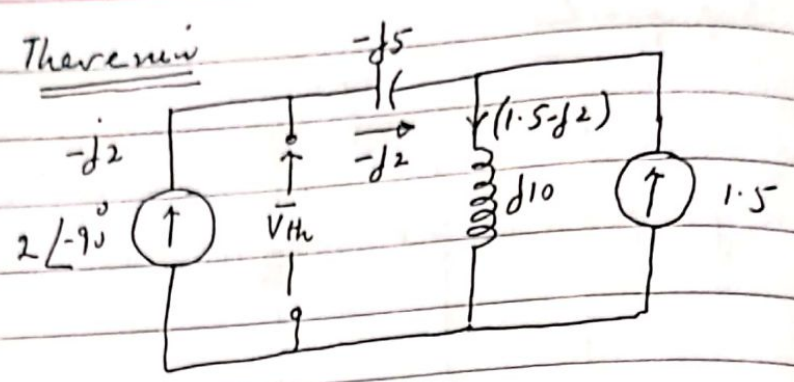


$$\begin{aligned} \bar{V}_{th} &= (-j5)(-j2) + (1.5-j2)j10 \\ &= -10 + 15j + 20 \\ &= 10 + 15j \end{aligned}$$

$$Z_{th} = -j5 + j10 = j5$$

$$\bar{V}_{AB} = \frac{10}{10+j5} \times V_{th}$$

voltage division

$$\begin{aligned} &= \left(\frac{10}{10+j5} \right) \times (10+15j) \\ &= 10 \frac{(2+j3)}{(2+j)} \\ &= \frac{10^2 (2+j3)(2-j)}{8} \\ &= 2 [4 - 2j + 6j + 3] \\ &= 2(7+4j) \\ &= 14+j8 = 16.1 \angle 29.7^\circ \end{aligned}$$

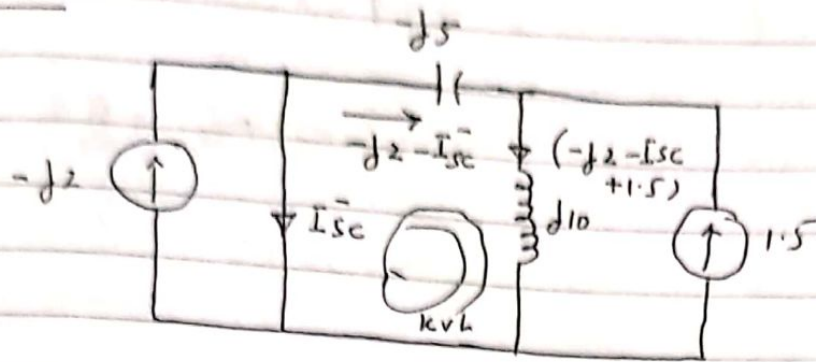Norton

$$\text{KVL} \quad -1 \quad 2$$


$$(-j2 - \bar{I}_{sc}) \times j5 + (-j2 - \bar{I}_{sc} + 1.5) j10$$

$$= 10$$

$$\underline{j2} + \underline{\bar{I}_{sc}} - \underline{j4} - \underline{2\bar{I}_{sc}} + \underline{3} = 0$$

$$-\bar{I}_{sc} = -3 + j2$$

$$\bar{I}_{sc} = 3 - j2$$

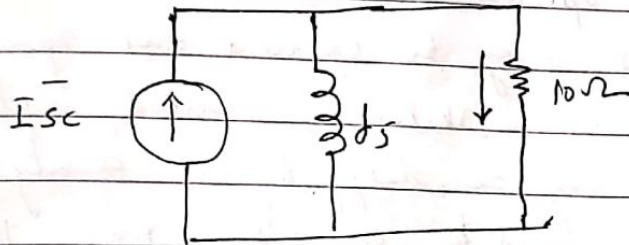

$$\bar{V} = \left(\frac{j5}{10 + j5} \right) \bar{I}_{sc} \times 10$$

$$= \left(\frac{j5}{10 + j5} \right) (3 - j2) \times 10$$

$$= 10 \left(\frac{j}{2 + j4} \right) (3 - j2)$$

$$= \underline{10(j)(2 - j1)(3 - j2)}$$

classmate

Date

Page

$$\bar{V} = 2 [1 + j2] [3 - j2]$$

$$= 2 [3 - j2 + 6j + 4]$$

$$= 2 [10 + j]$$

$$= 2 [7 + j4]$$

$$= 14 + j8 = 16.1 \angle 29.7^\circ$$