

# Basic Electrical Engg. :->

## 1.) Circuit Element:

2.) Branch

3.) Network V.S Circuit.

↳ closed network

↳ Interconnection of circuit element

↳ need not to be closed

↳ Every circuit is a network but vice versa is not true

4.) Lumped network (n/t) V.S Distributed n/t

↳ electrical elements can be separate physical

↳ network in which elements can neither be electrically or physically separated

5.) Charge:  $1.6 \times 10^{-19} \text{ C}$

Charge in motion is known as Current

6.) Current:  $C = \frac{dq}{dt}$  or  $I = \frac{dq}{dt}$


rate of change of charge is Current

Q = Coulomb

t = sec

I = Ampere = C/s


$I_e$

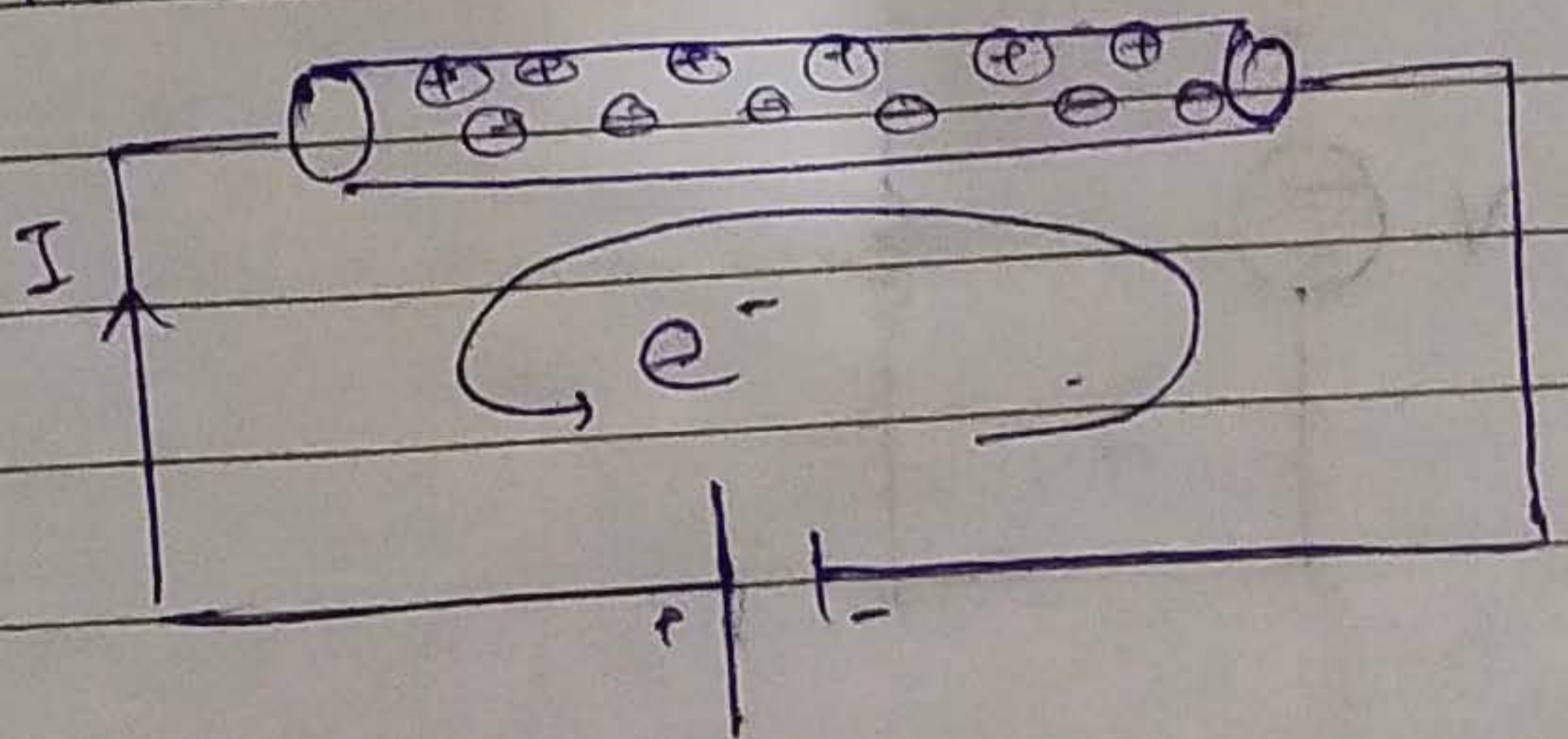

7) Voltage:  $\frac{dw}{dq}$  → work done per unit charge

8) Power:  $V \cdot I = \frac{dw}{dq} \cdot \frac{dq}{dt}$   
 $\Rightarrow \frac{dw}{dt}$  (Watts)  
 Volts → Amp → Watts

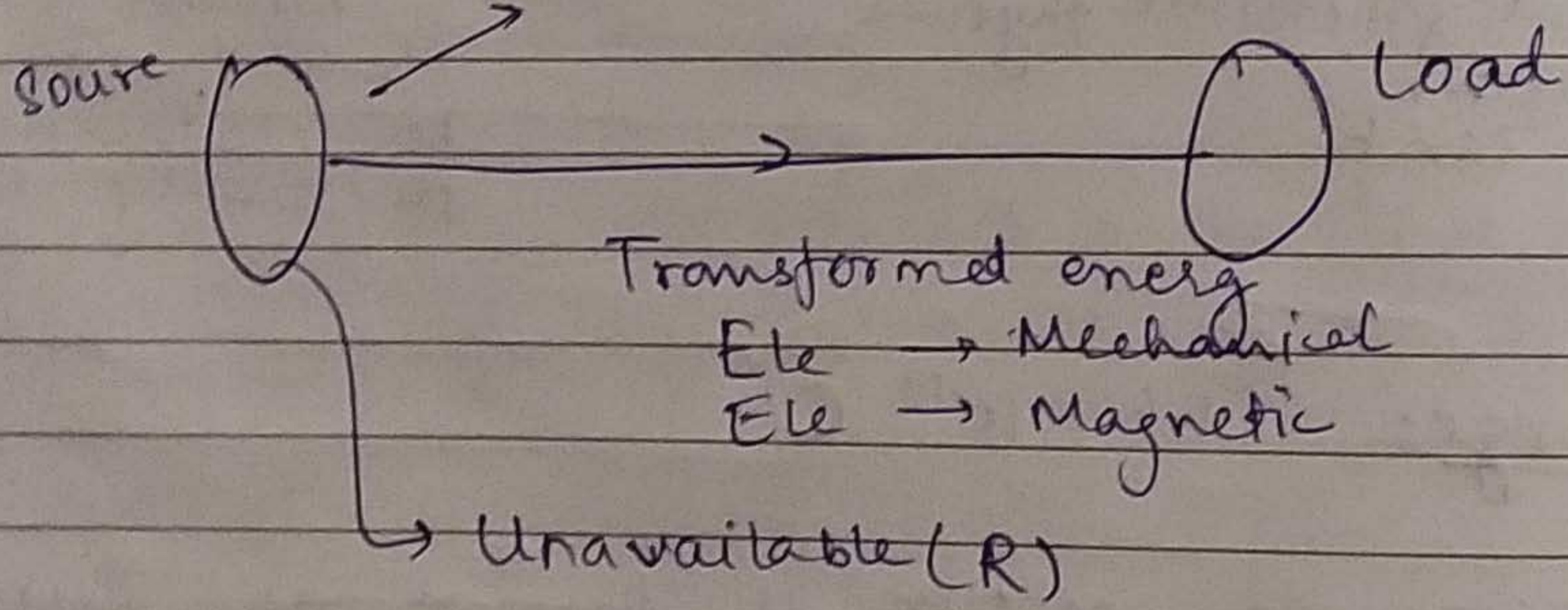9) Energy  $\equiv \int \frac{dw}{dt} dt = \text{Work done}$   
 stored (L, C)





# Classification of Elements :-



1) Active Elements  
(Transistors, Amplifier)

2) Passive Elements  
(R, L, C)


# V-I characteristic:

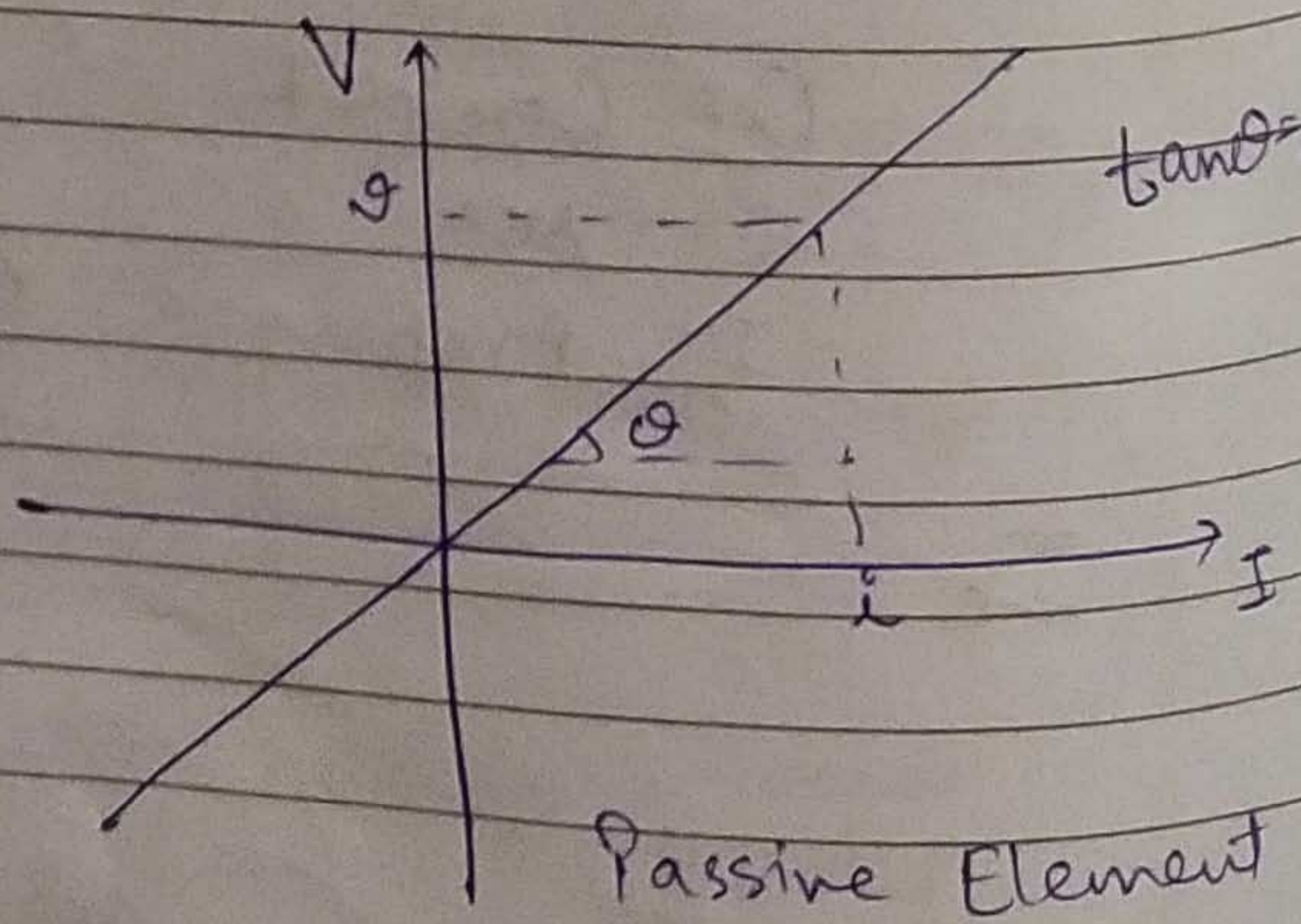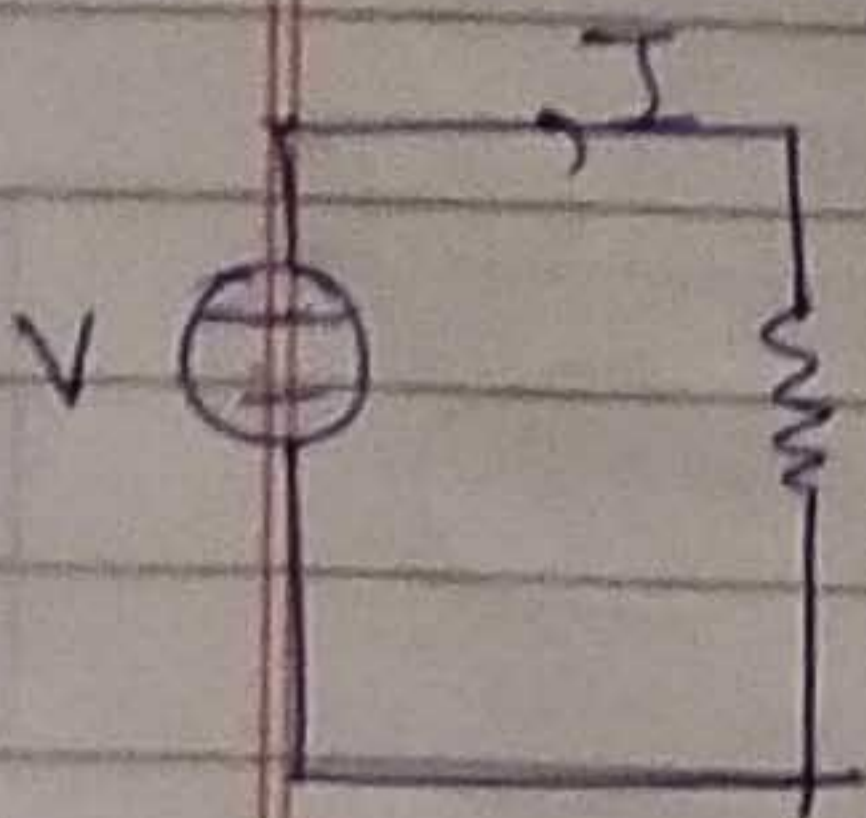

$$\tan \theta = \frac{v}{-i}$$

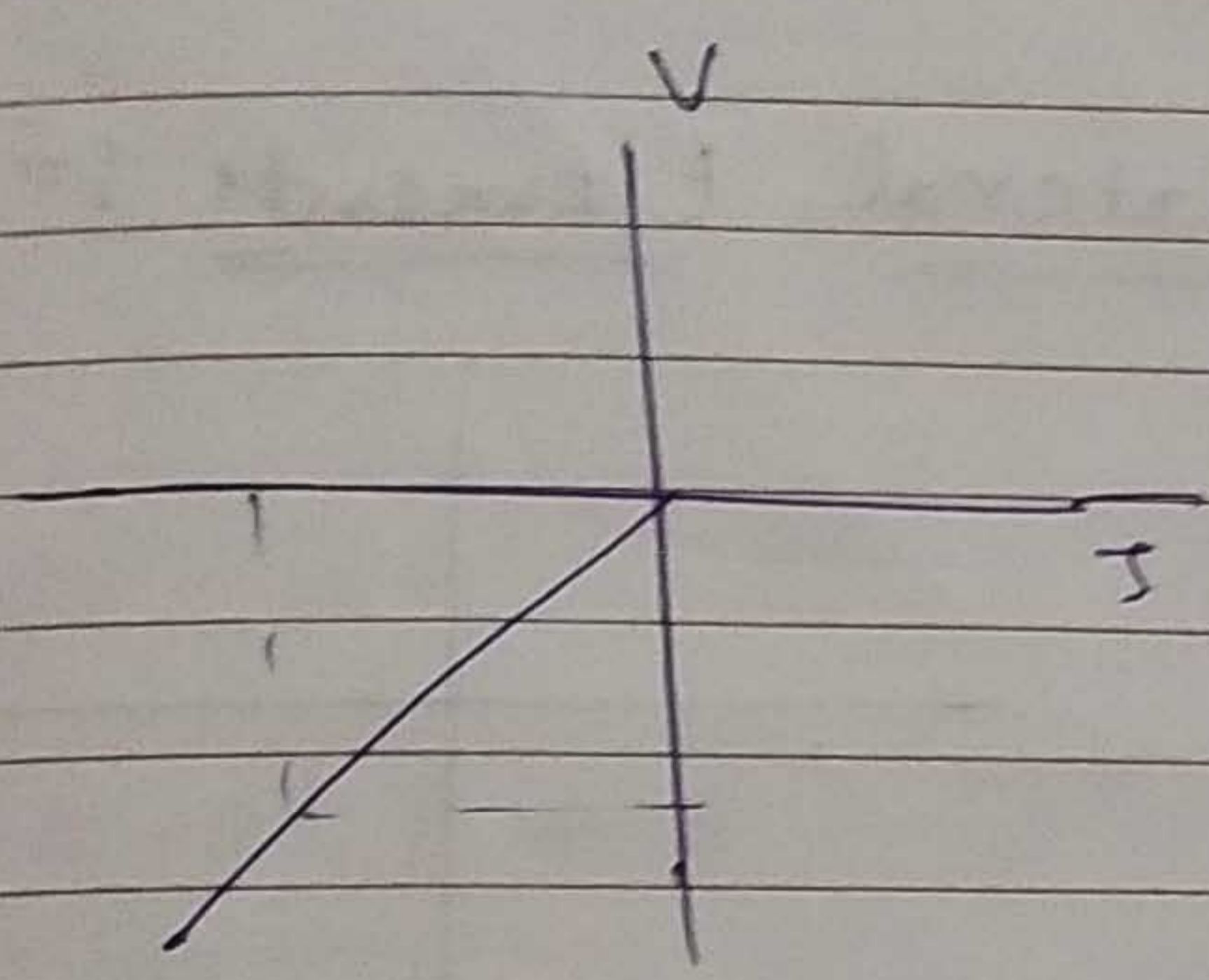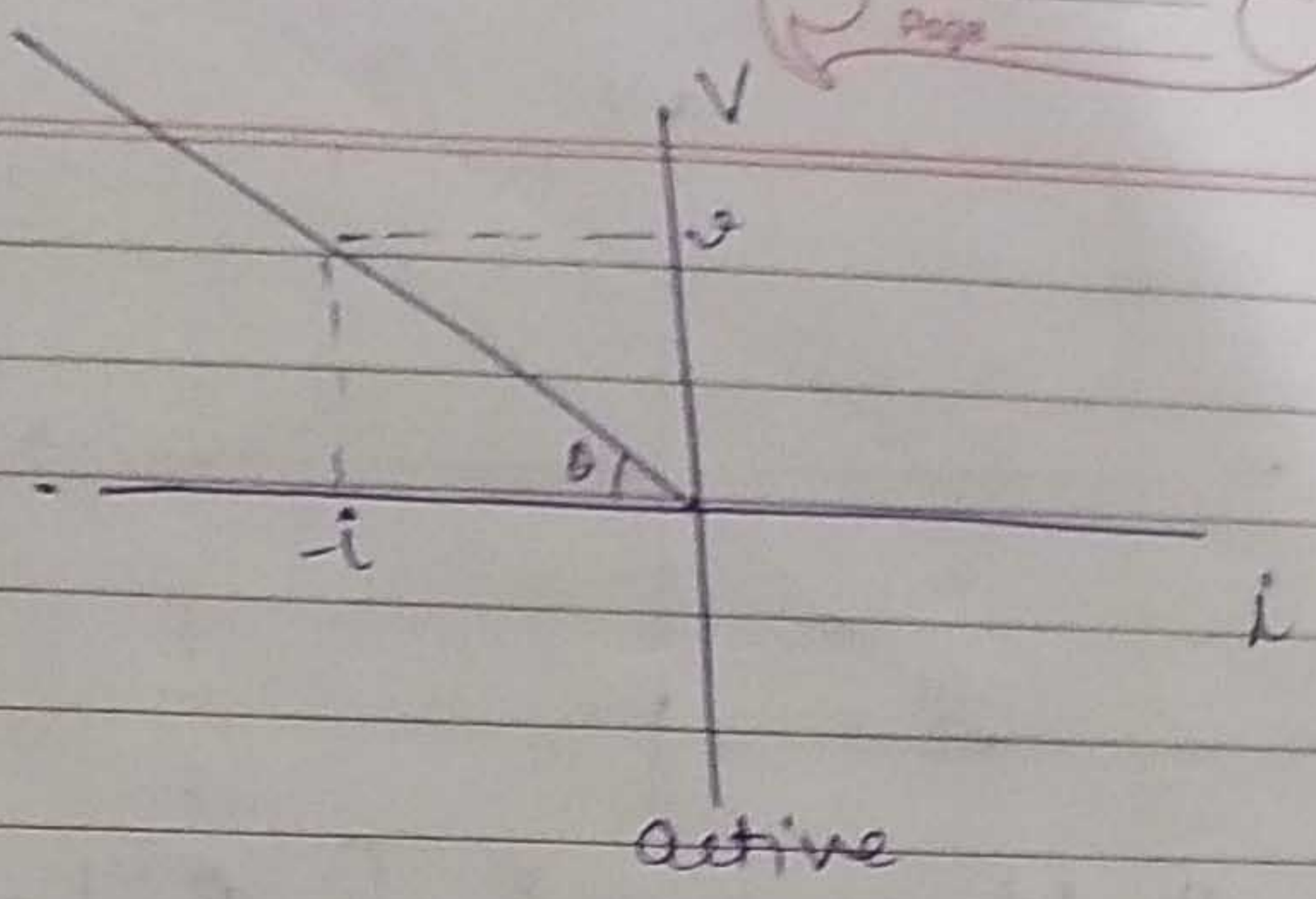


slope = +ve  
Passive

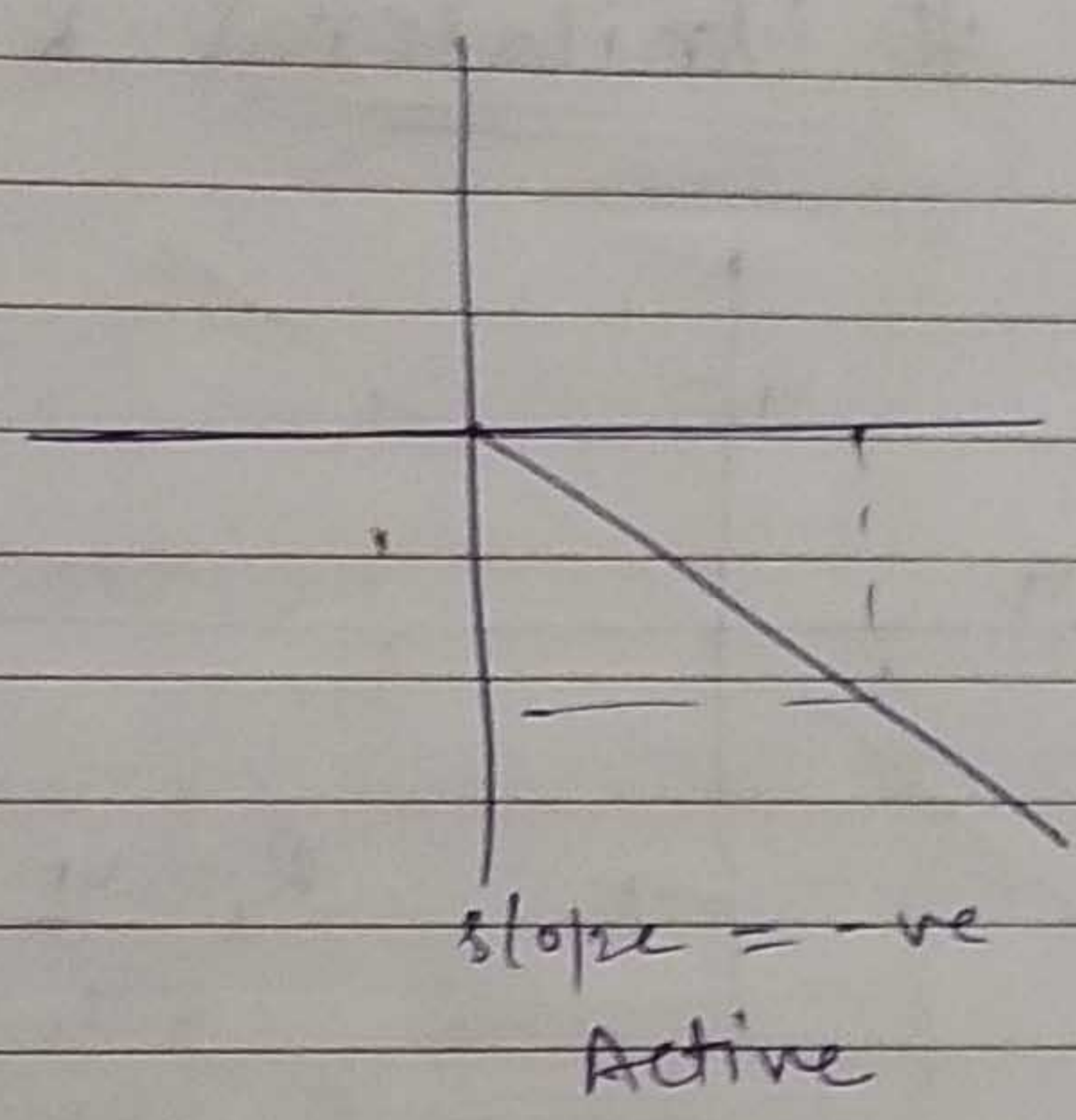


slope = -ve  
Active


#. Linear & Non-Linear Elements :->

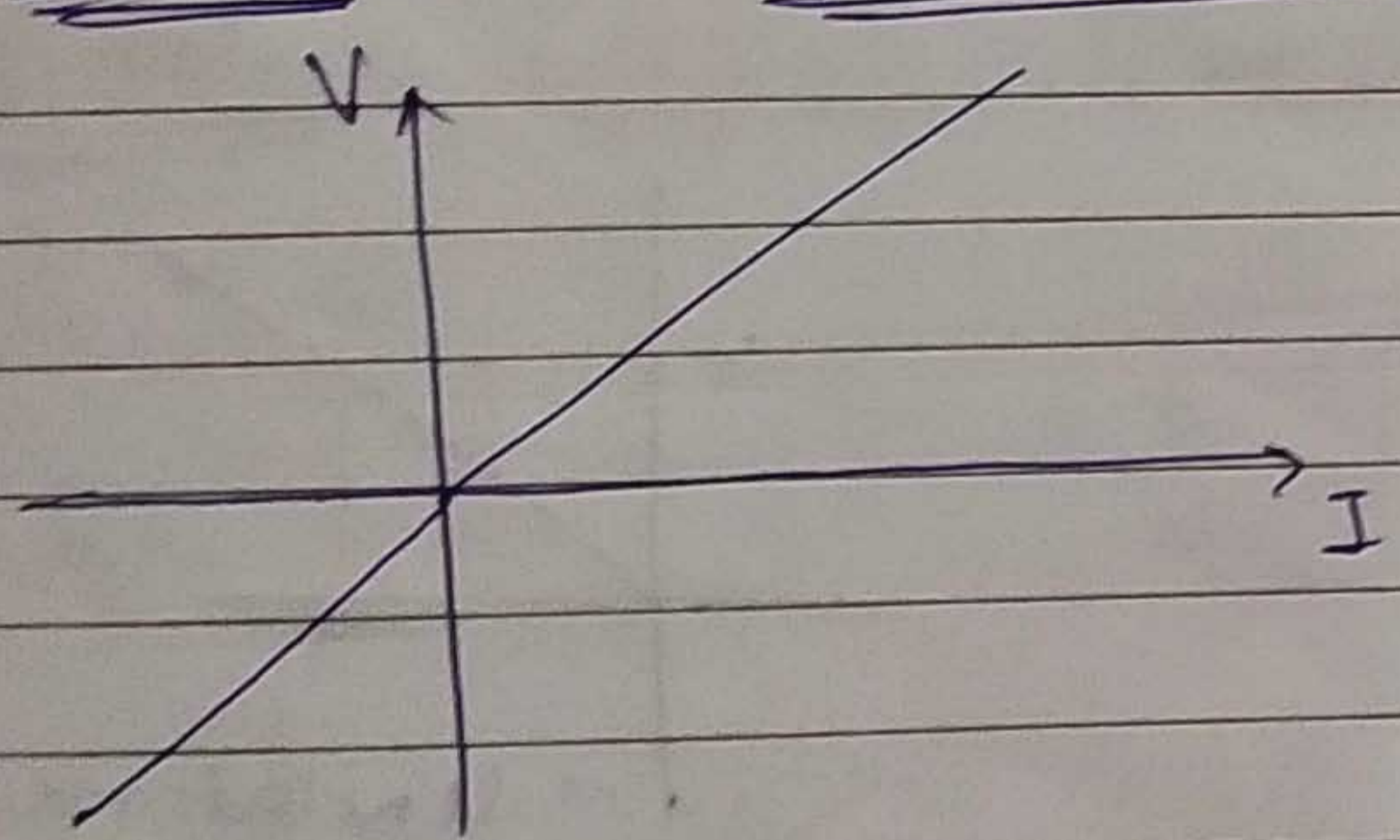

Linear Element

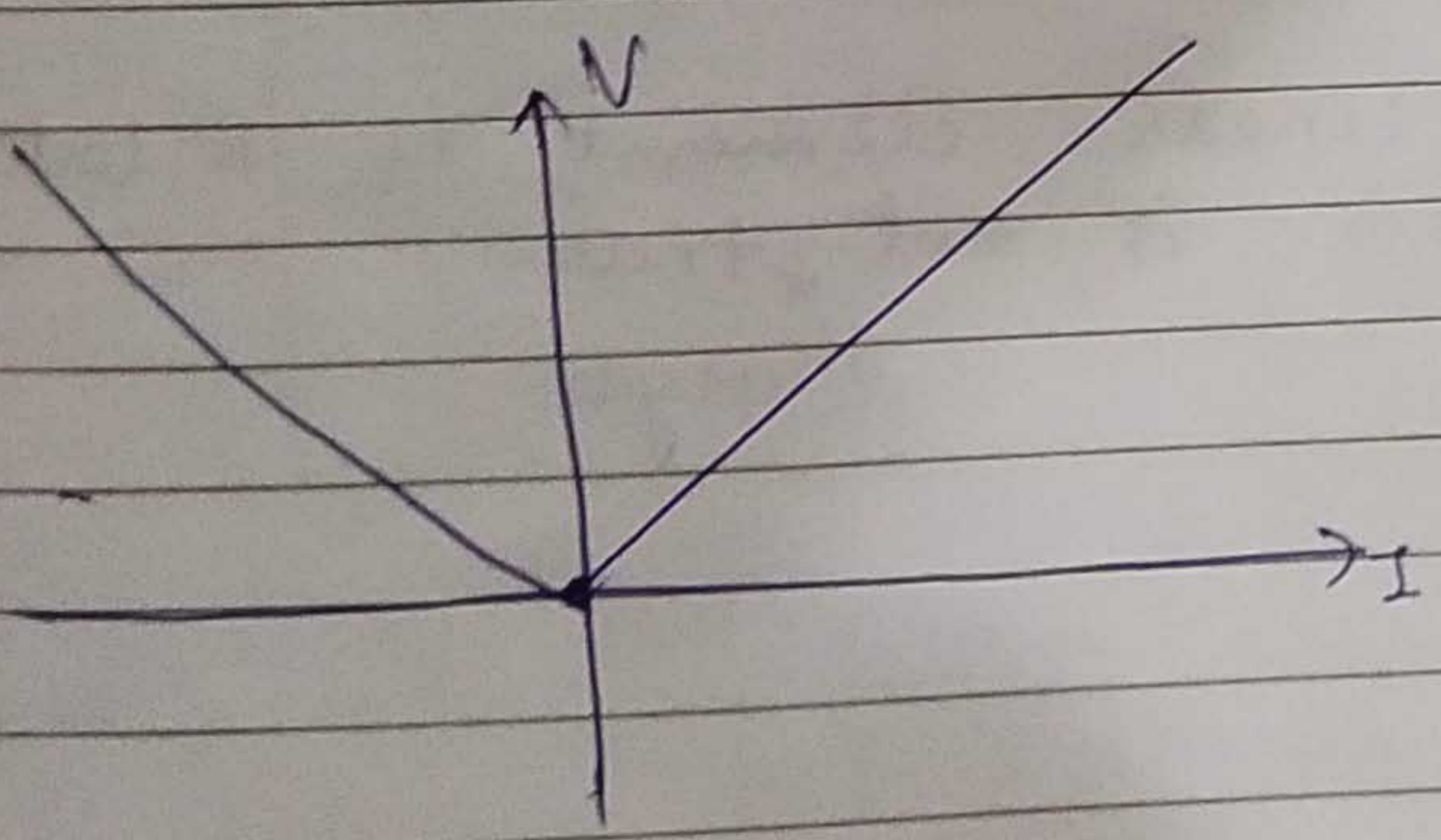


Non-linear Element

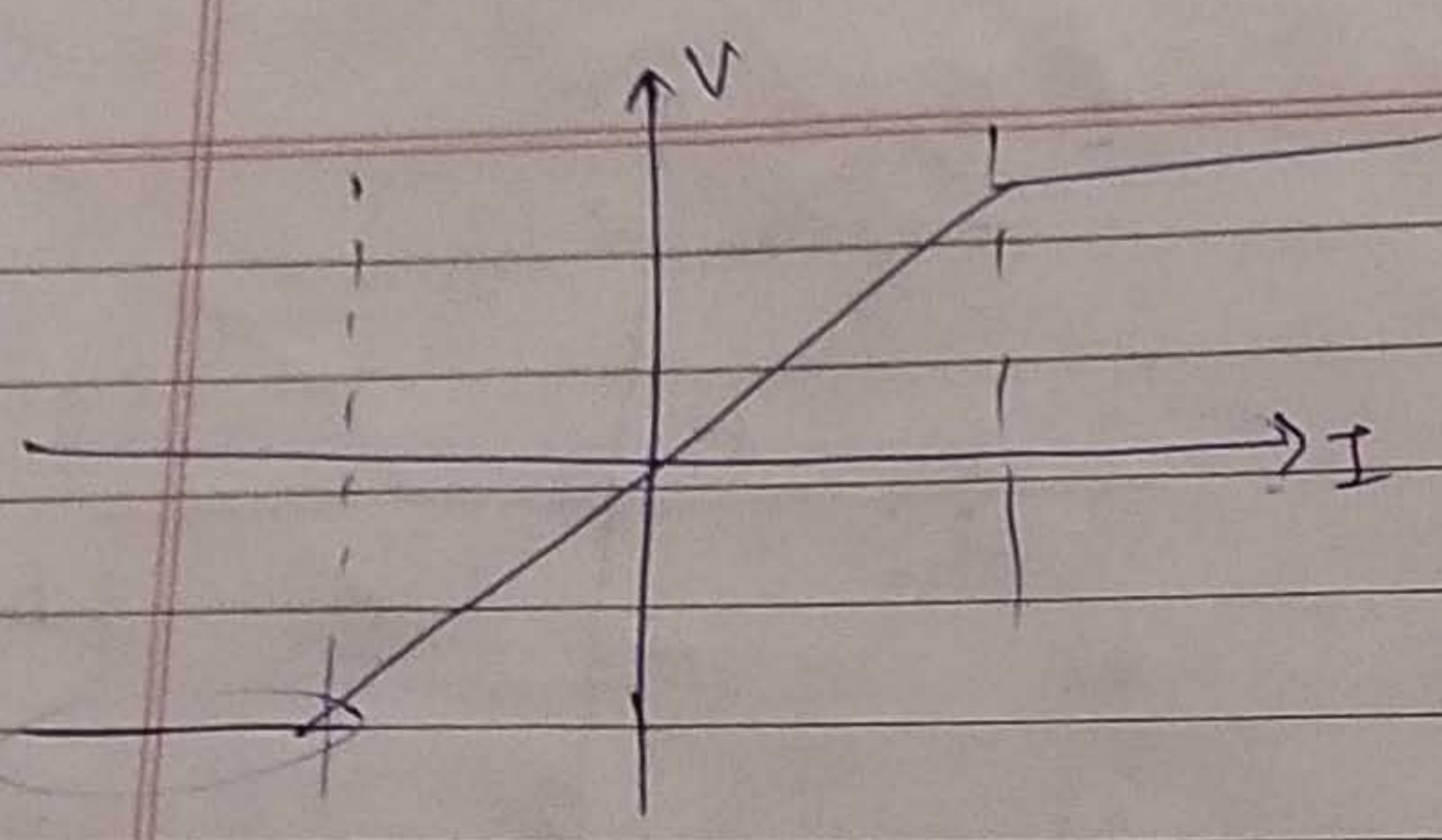

Non-linear

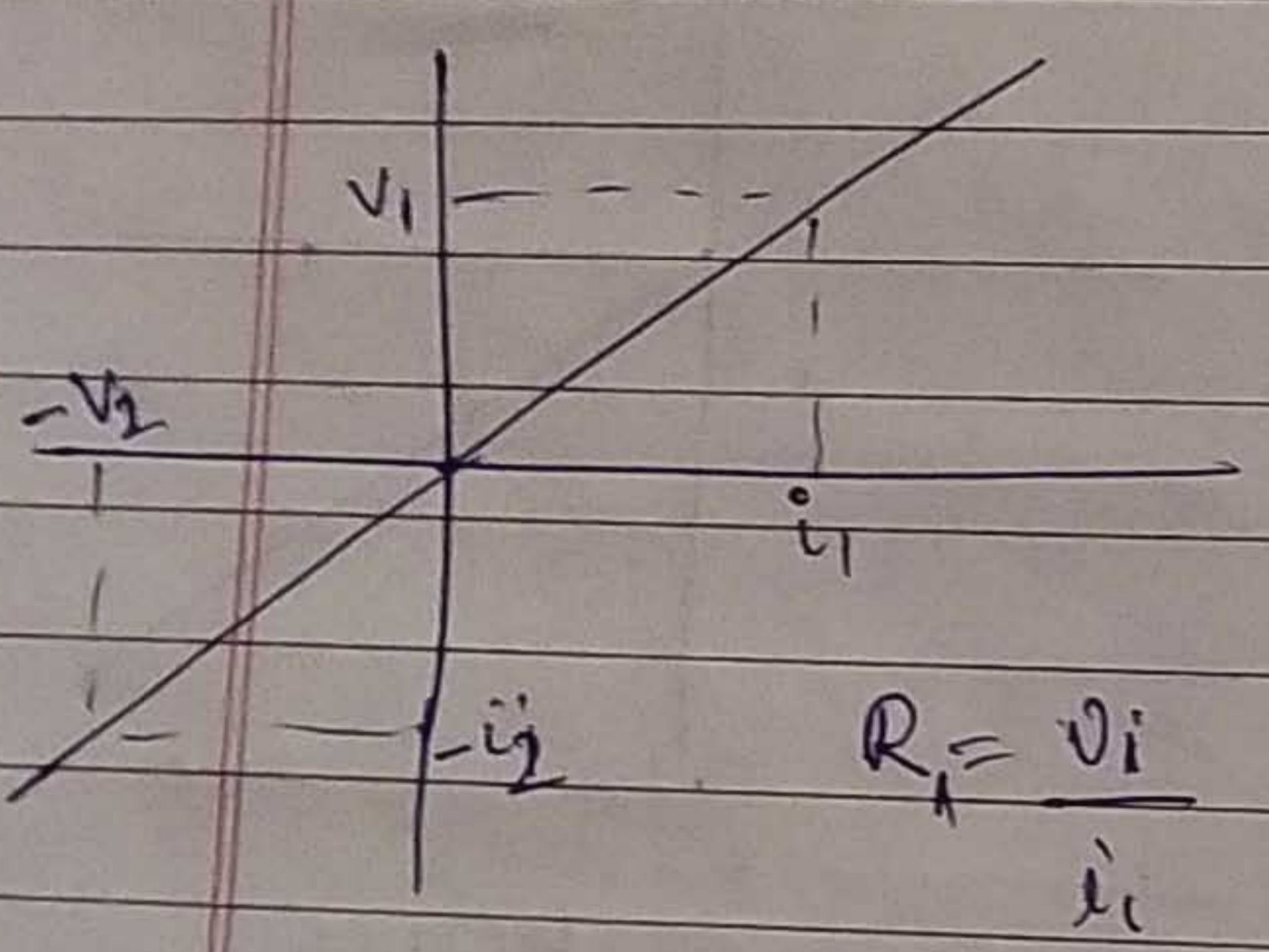
### # Unilateral & Bilateral Elements :->




$$R_1 = \frac{v_1}{i_1}$$

$$R_2 = \frac{v_2}{i_2}$$

Bilateral Ele  
(Resistor)

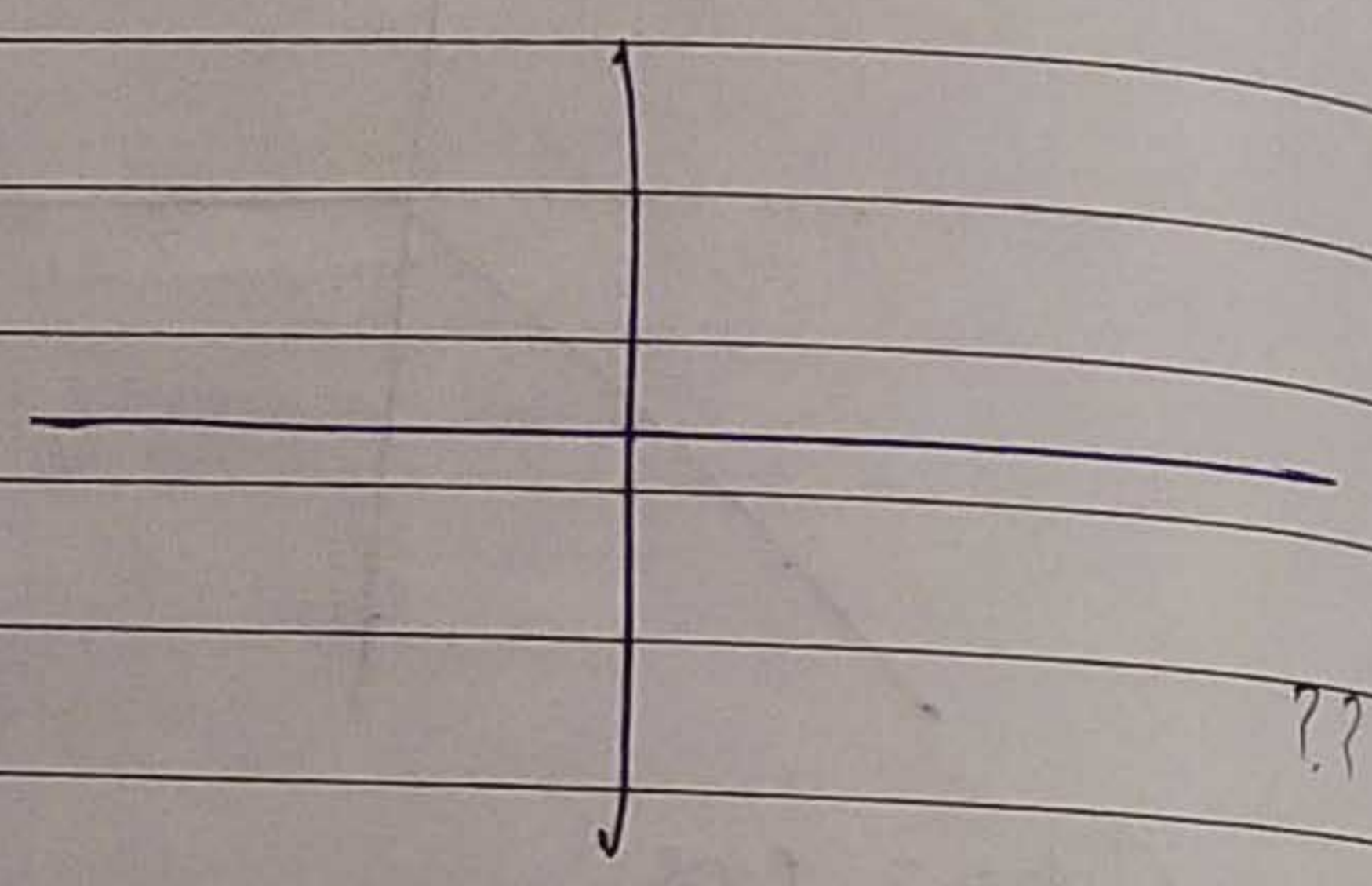


→ (diode)  
Unilateral

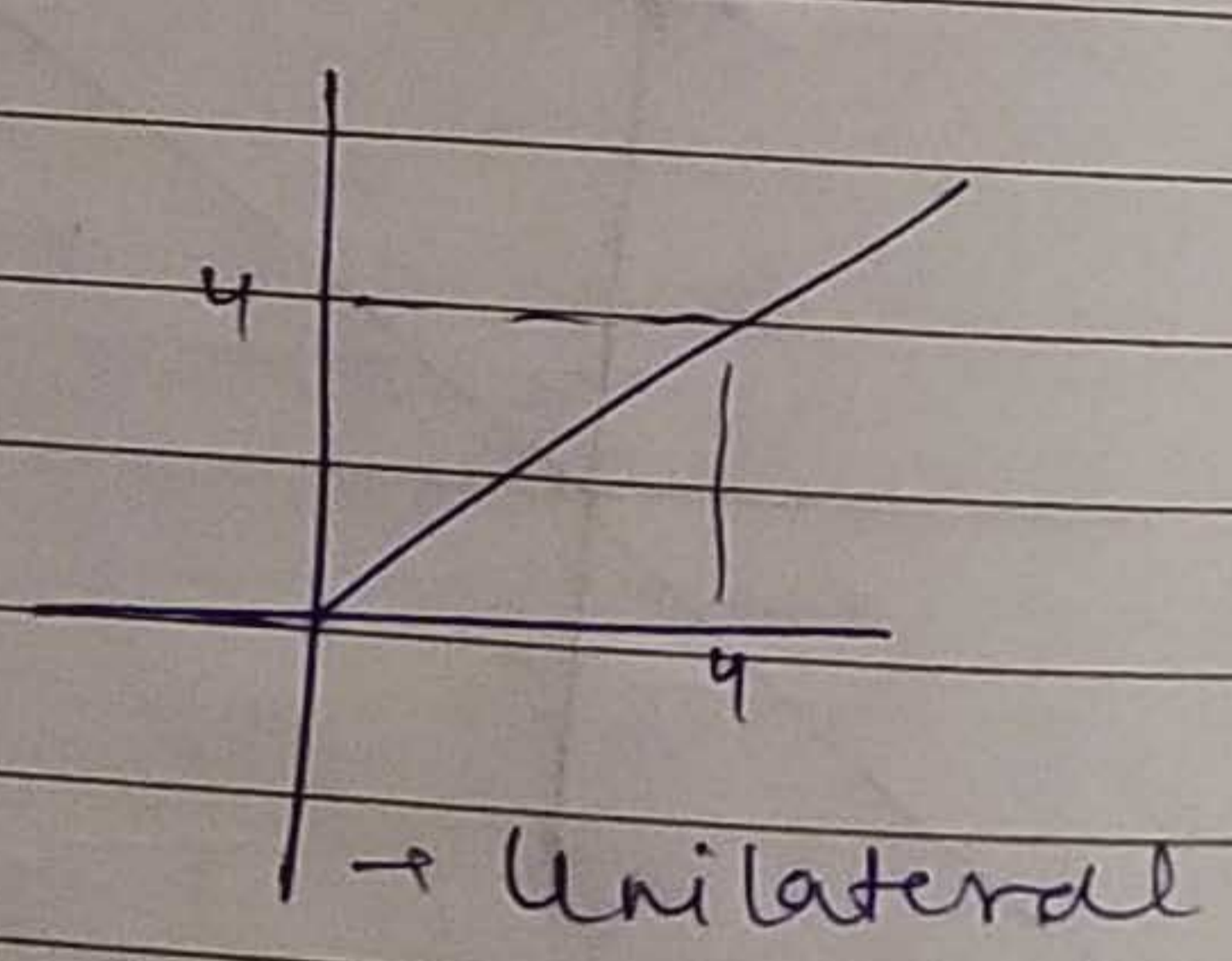

→ Unilateral

⊛ Every ~~linear~~ linear element is Bilateral  
but vice-versa is not  $\downarrow$  true.  
always.

## # Time-Varying and Time-Invariant:-

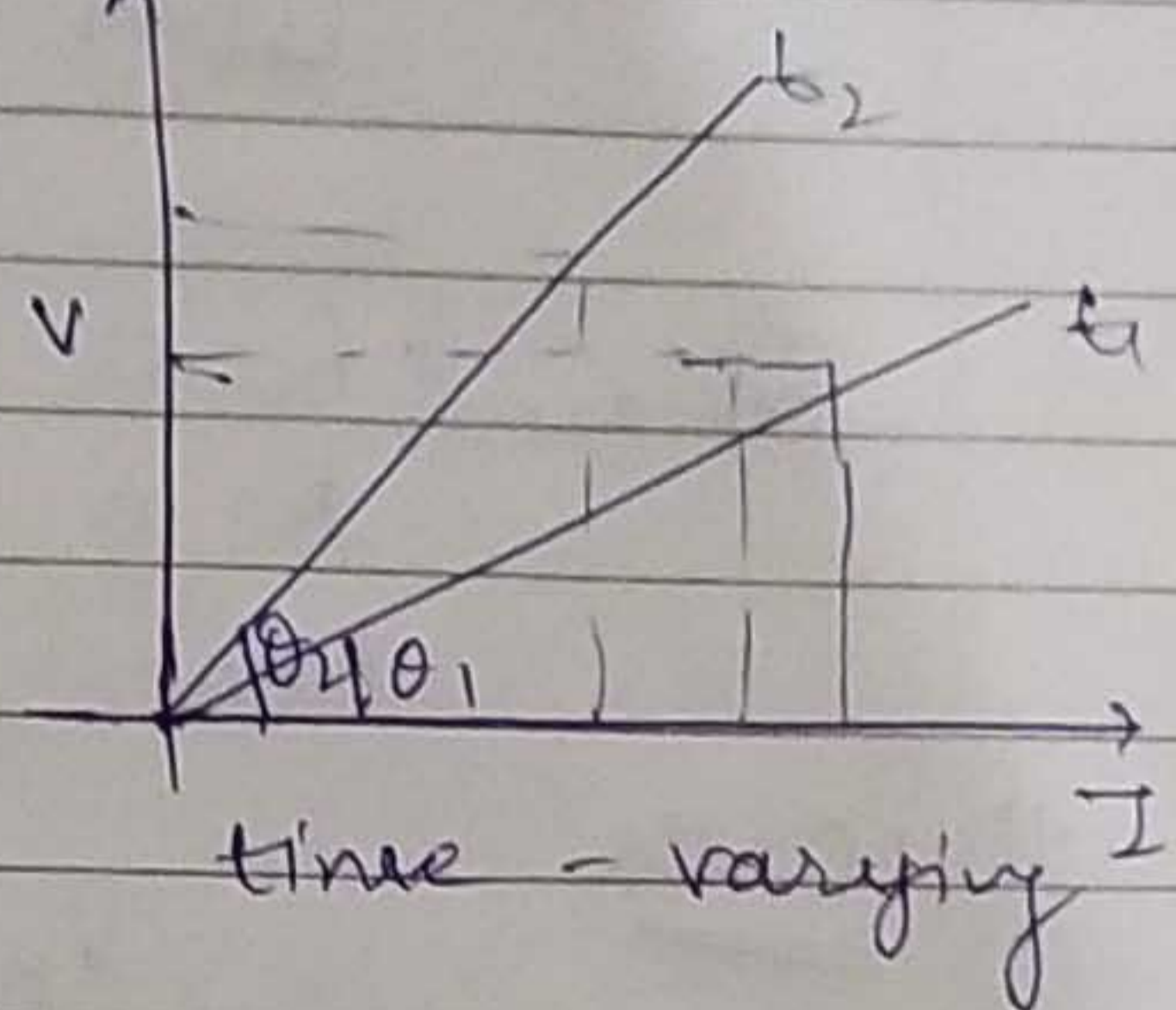


### Example

①  $A + P = \text{Active}$

L or NL  $\rightarrow$  NL

Active or Passive  $\rightarrow$  Active

U or BL  $\rightarrow$  Unilateral

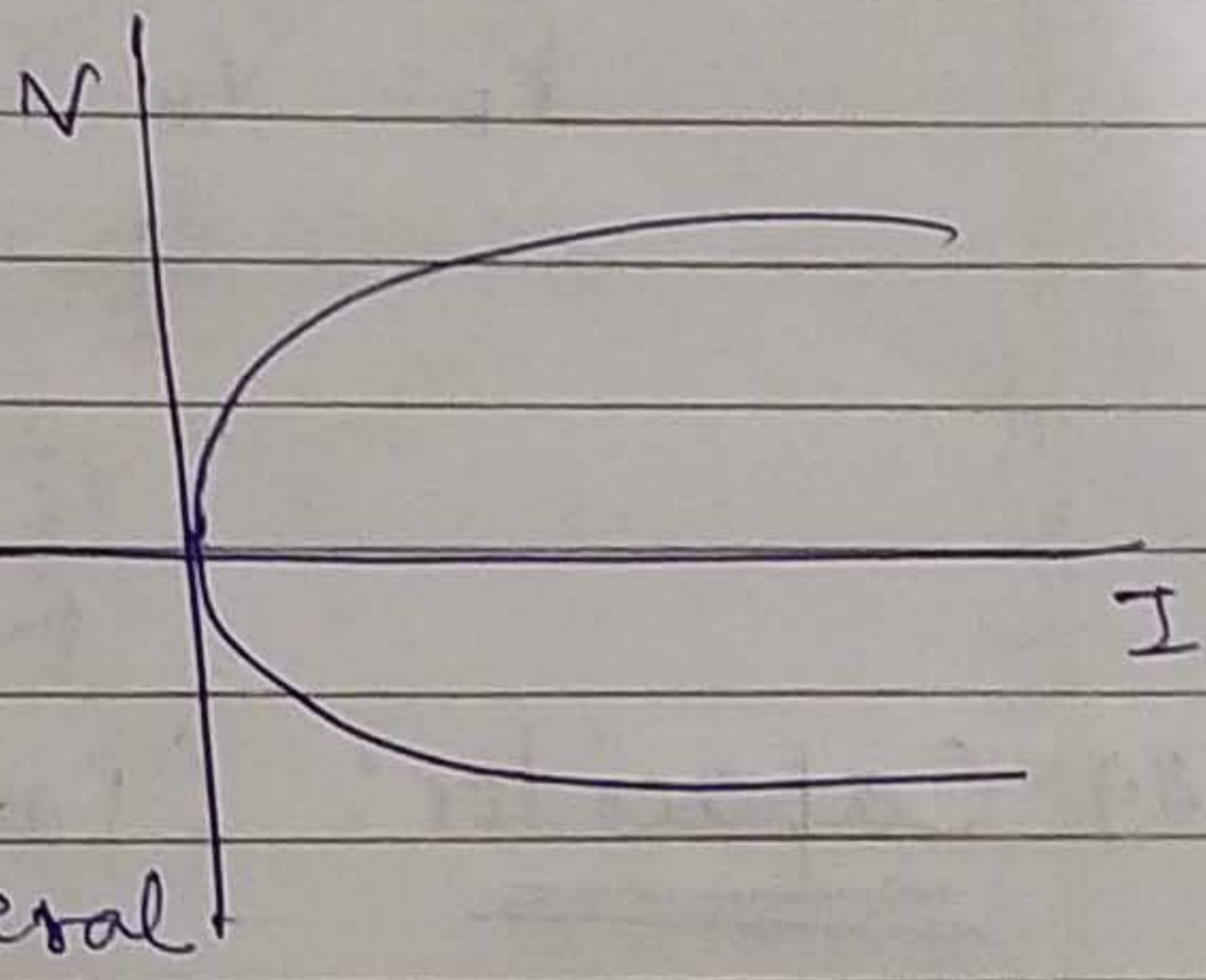


## # Basic Circuit Elements:

### 1.) Resistors:

$\rightarrow$  static element

$$R = \frac{l}{a}$$

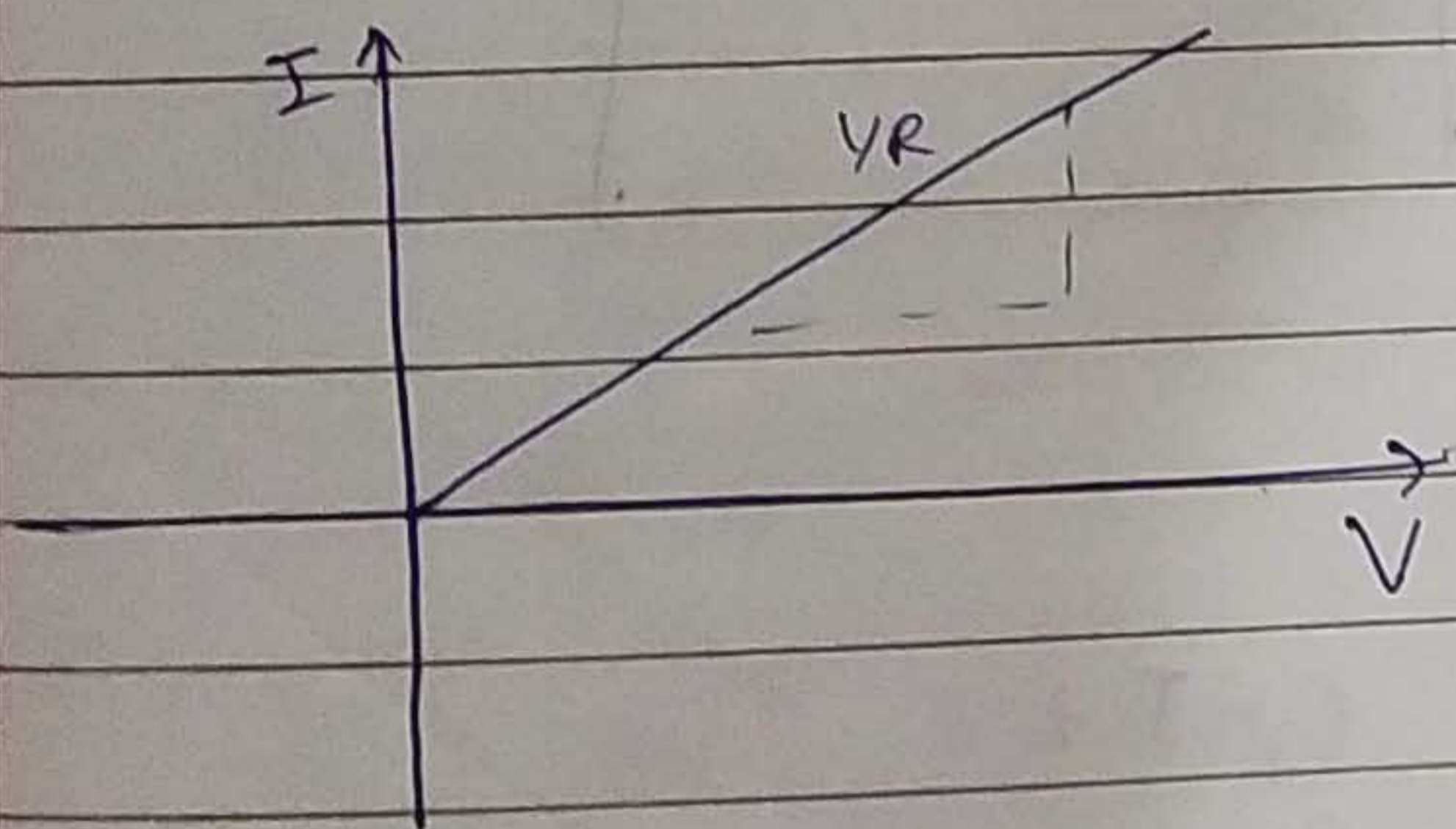$\rightarrow$  dissipated element in which energy is lost as heat



Ohm's law:

$$V \times \frac{1}{R} = I$$

$$\frac{1}{R} = G$$

$R \rightarrow \Omega$

$G \rightarrow \text{Siemen } \Sigma$

$$J = \sigma E \quad \text{Volt/unit length}$$

↓  
conductivity  
↓  
( $\Omega m$ )<sup>-1</sup> or  $\frac{1}{\Omega m}$

If,  $R=0 \rightarrow$  Short circuit (Current will be max & Volt = 0)  
 $R=\infty \rightarrow$  Open circuit (I=0 & Volt = max)

# Power:

$$P_R = V_R \cdot I_R$$


$$= \frac{I_R \cdot I_R}{R} = \frac{I_R^2}{R}$$

$$= \frac{V_R^2}{R}$$

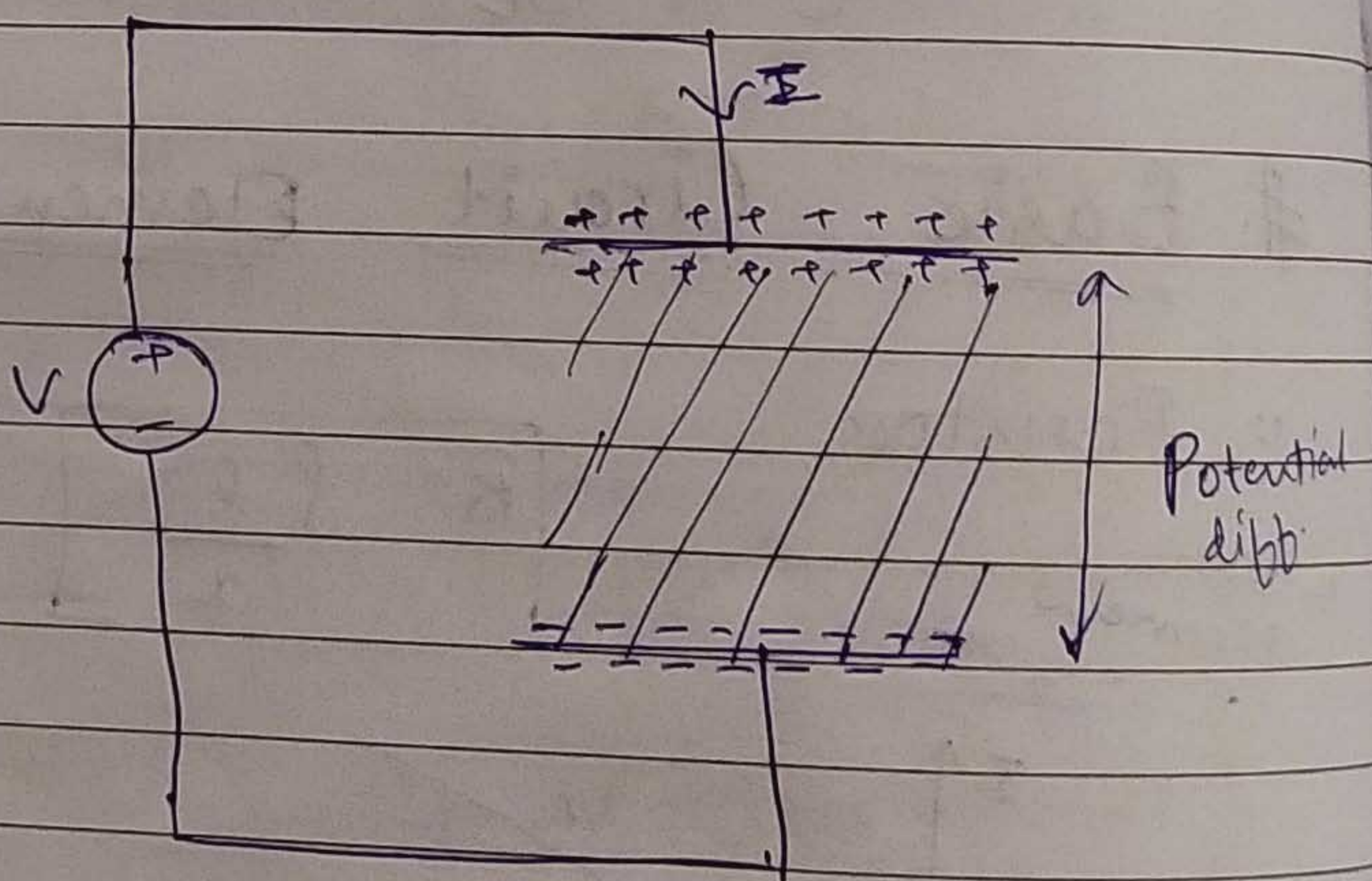2.) Capacitor: (farad)

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

↑ permittivity  
 → Area of metal plate  
 ↓ distance b/w two



→ dynamic elements

# Steady State:

$$Q = I \cdot t$$

$$Q = C \cdot V$$

$$i = C \frac{dV}{dt} \Rightarrow \int i dt = C \Delta V$$

$$\frac{1}{C} \int_{-\infty}^t i dt = \int_{V_0}^{V_t} dV$$

$$\frac{1}{C} \int_{-\infty}^t i dt = (V_t - V_0)$$

Power:  $P = Vi$   
 $= V \cdot C \cdot \frac{dV}{dt}$

$$\int P dt = \int C V \cdot dV$$

$$E = \frac{CV^2}{2} \rightarrow \text{Energy of a capacitor.}$$

3) Inductors:  $\rightarrow$  (Henry)  $\rightarrow$   $\mu H, mH$ .  
 $\rightarrow$  dynamic compo

$$\text{emf } (e) = N \frac{d\phi}{dt} \quad \text{--- (1)}$$


$$e = i \frac{di}{dt} \quad \text{--- (2)}$$

$N\phi = Li$   
 $\frac{N\phi}{i} = L \rightarrow$  Inductance

$$\phi = \frac{Ni}{\frac{l}{\mu A}} = \frac{Ni \mu A}{l}$$

$$L = \frac{N}{i} \cdot \frac{Ni \mu A}{l}$$

$$L = \frac{N^2 \mu A}{l}$$

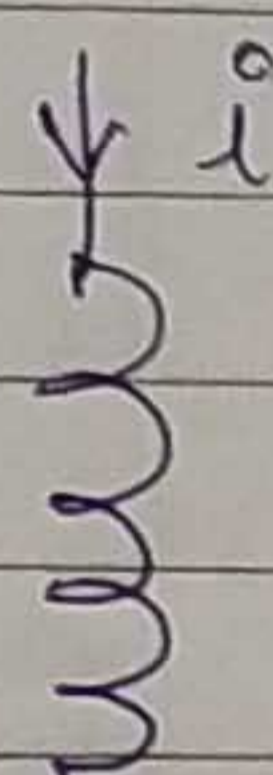

In Magnetic Circuits

$$\phi = \frac{\text{mmf}}{\downarrow \text{magnetic motive force}}$$

$$\phi = \frac{\text{mmf}}{\downarrow \text{Magnetic reluctance}}$$

$$\phi = \frac{\text{mmf}}{\frac{l}{\mu A}}$$

$$V = L \frac{di}{dt}$$

$$\frac{1}{L} \int V dt = \int_{i_0}^{i_t} di$$

$$\boxed{\frac{1}{L} \int V dt = (i_t - i_0)}$$

→ Non-linear element  
→ In case if initial current is zero then only it is linear element.

$$P = v \cdot i$$

$$= \frac{d}{dt} \int v \cdot i dt$$

$$= L \cdot \frac{di}{dt} \cdot i$$

$$\int \frac{P}{L} dt = \int i di$$

$$E = \frac{L \cdot i^2}{2}$$

$$\boxed{E = \frac{1}{2} Li^2}$$

→ Energy stored in inductor

## # CLASSIFICATION OF SOURCES →

Independent

Dependent

Practical

Ideal

Practical

Ideal


→ Voltage Controlled Volt-source

→ Current controlled Volt source

→ Voltage controlled Current source

→ Current controlled Current source

⊕ Independent Voltage sources: →

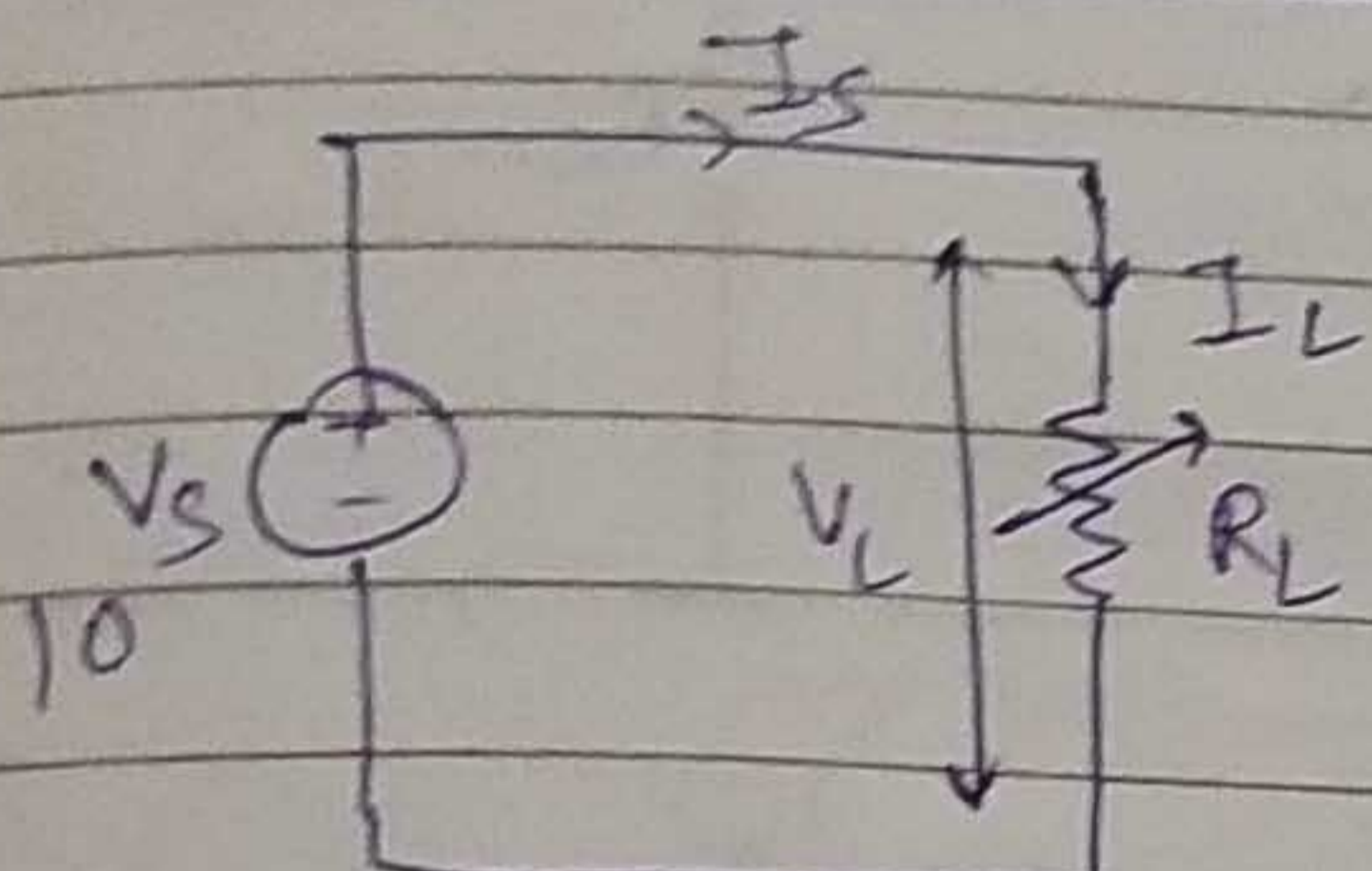


Ideal Voltage source

$R_L$	$I_L$	$V_L$
1	10	10
2	5	10


$V = IR$

$I = \frac{V}{R}$

$V_L = IR = 10$

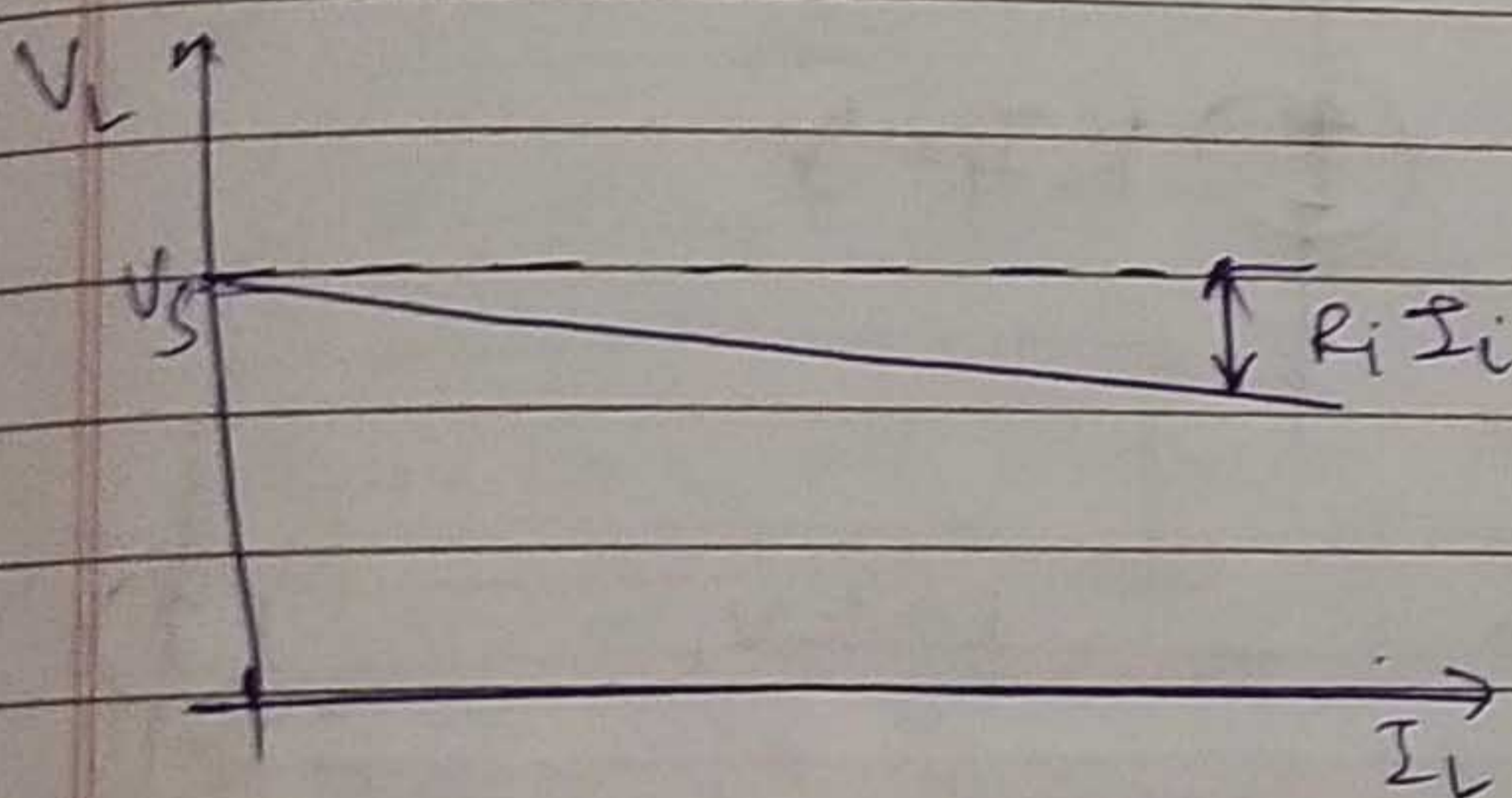

$V_L = V_s - R_i I_L$


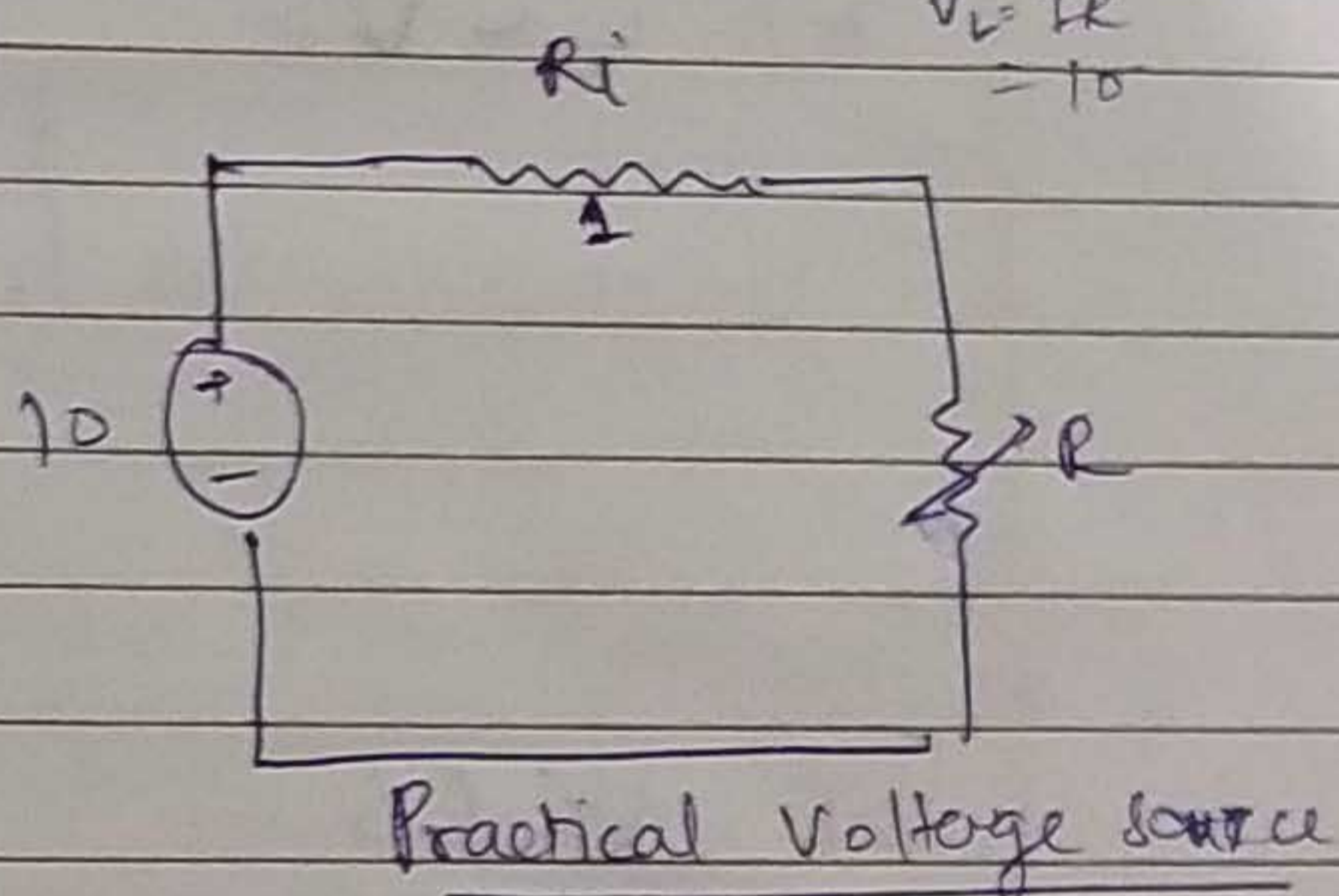


Practical Voltage source


~~$V_L = I_L R_L$~~   $V_L = V_s - I_L R_L$

$\frac{10}{R_i + R_L} = I_L$

⊕ Current Sources: →

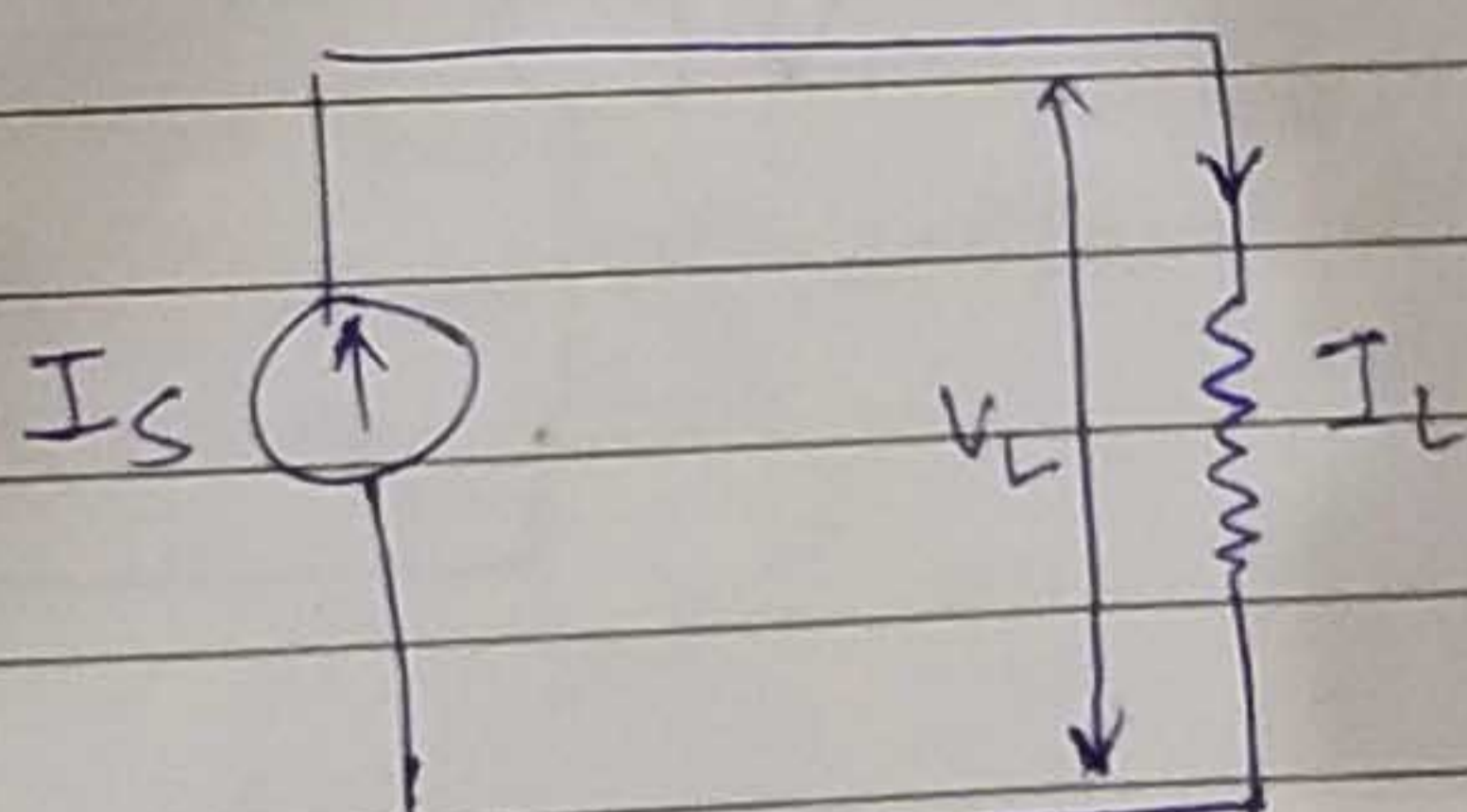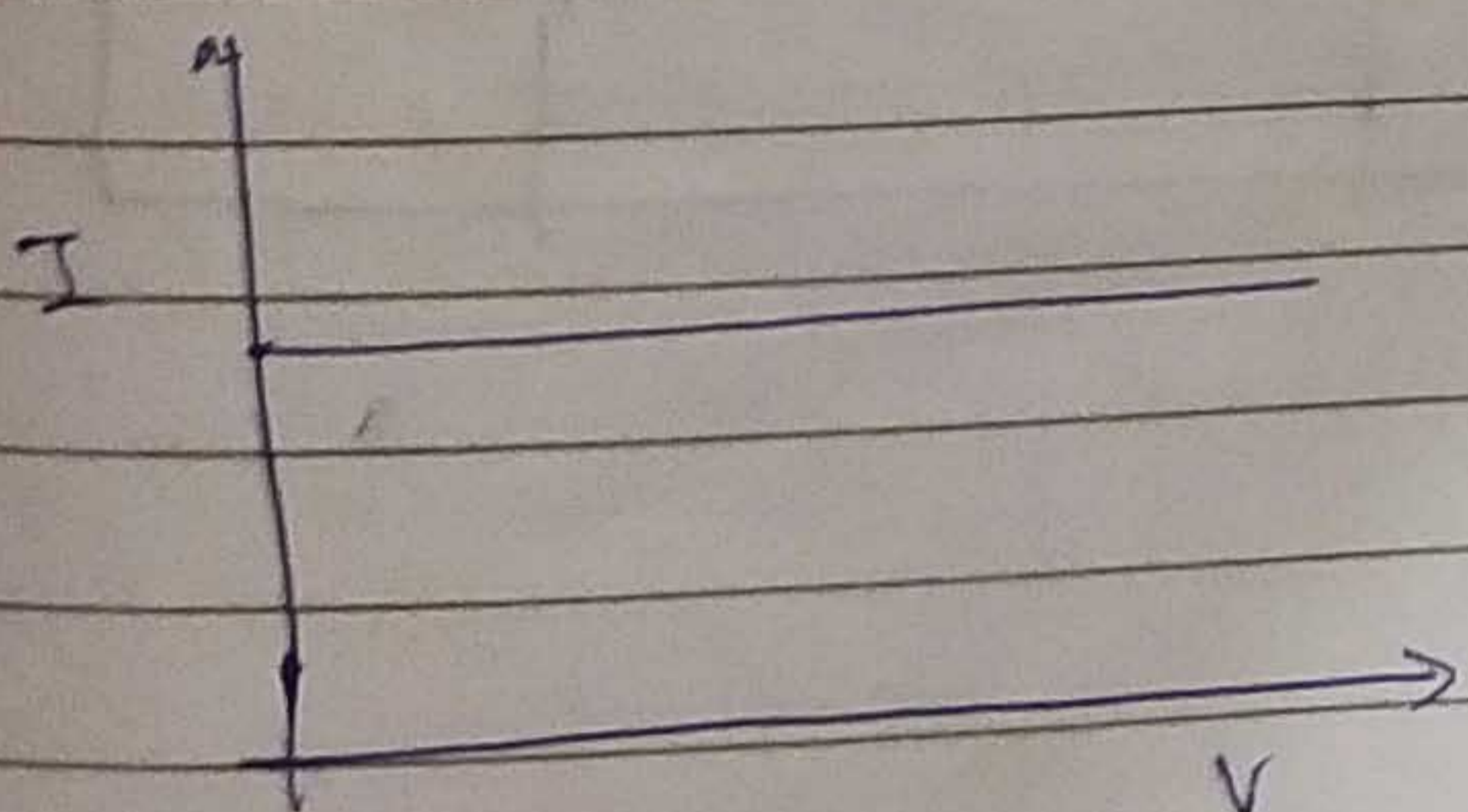


Ideal Current source

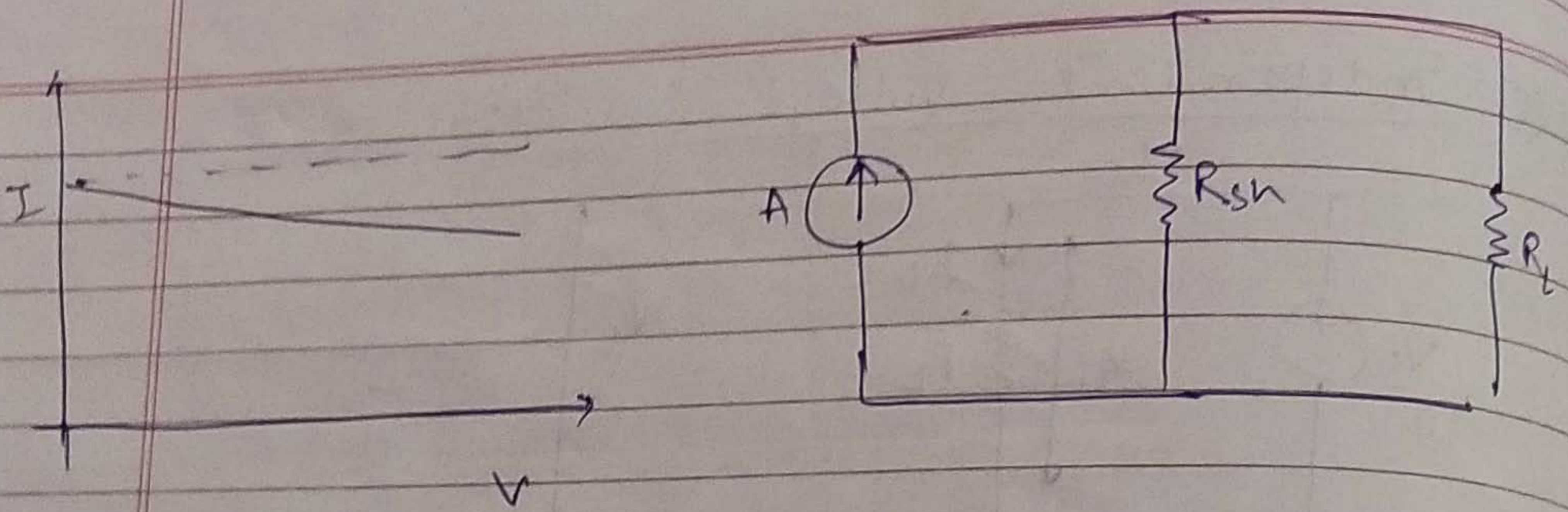

# Dependent Sources:

1.) VCVS


2.) CCVS

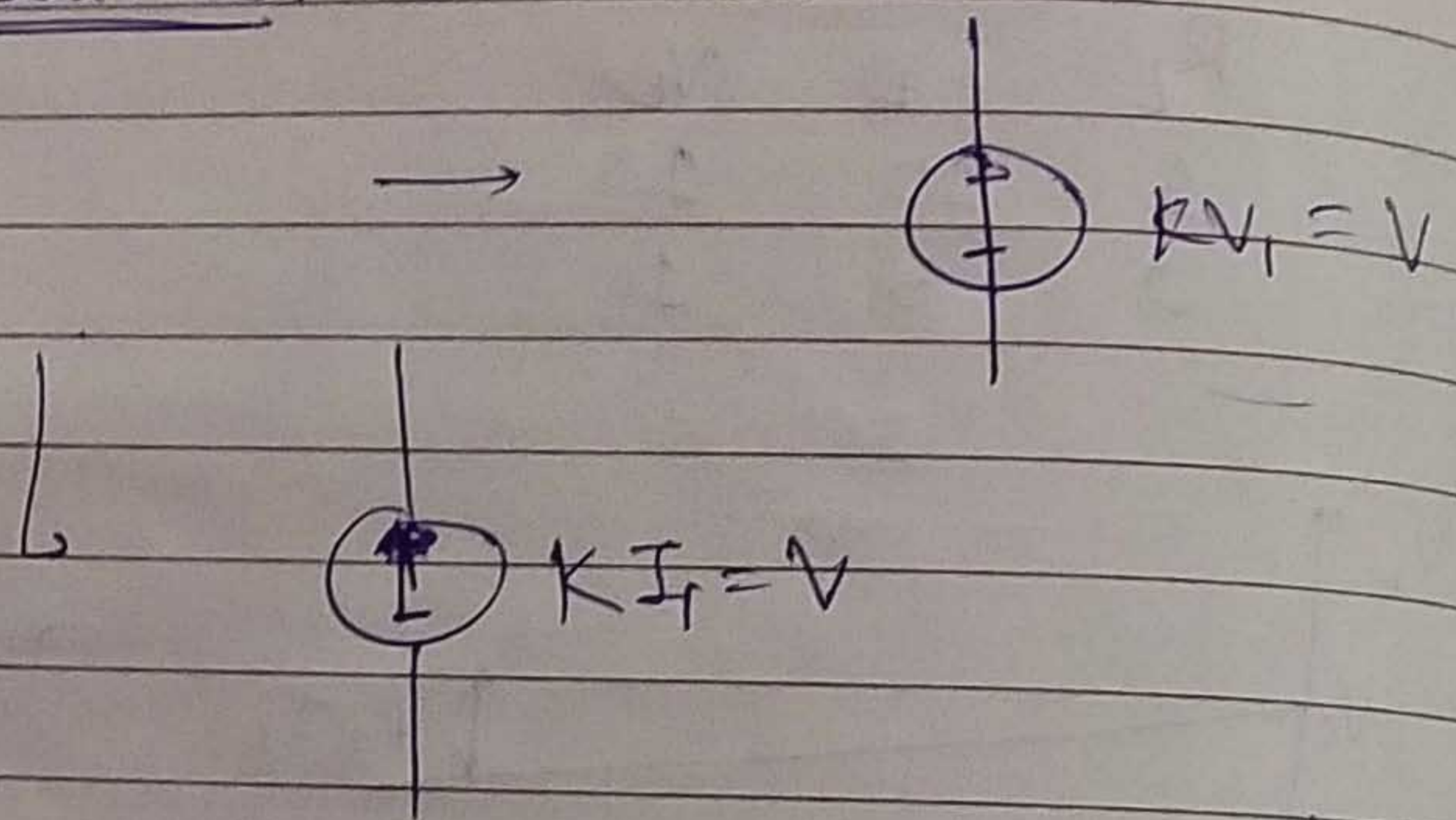


3.) VCCS

4.) CCCS

$I = kI_1$

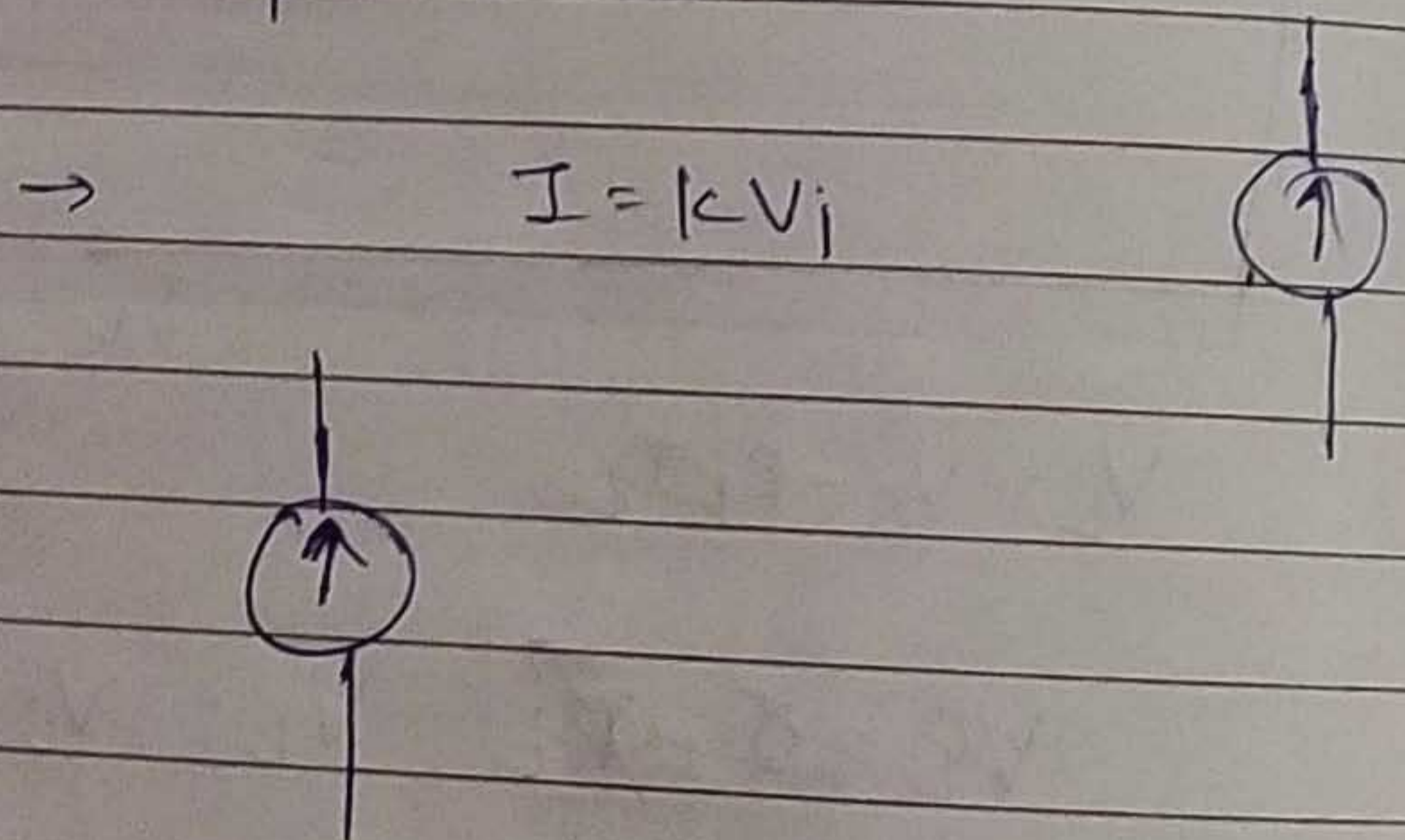


Example 1

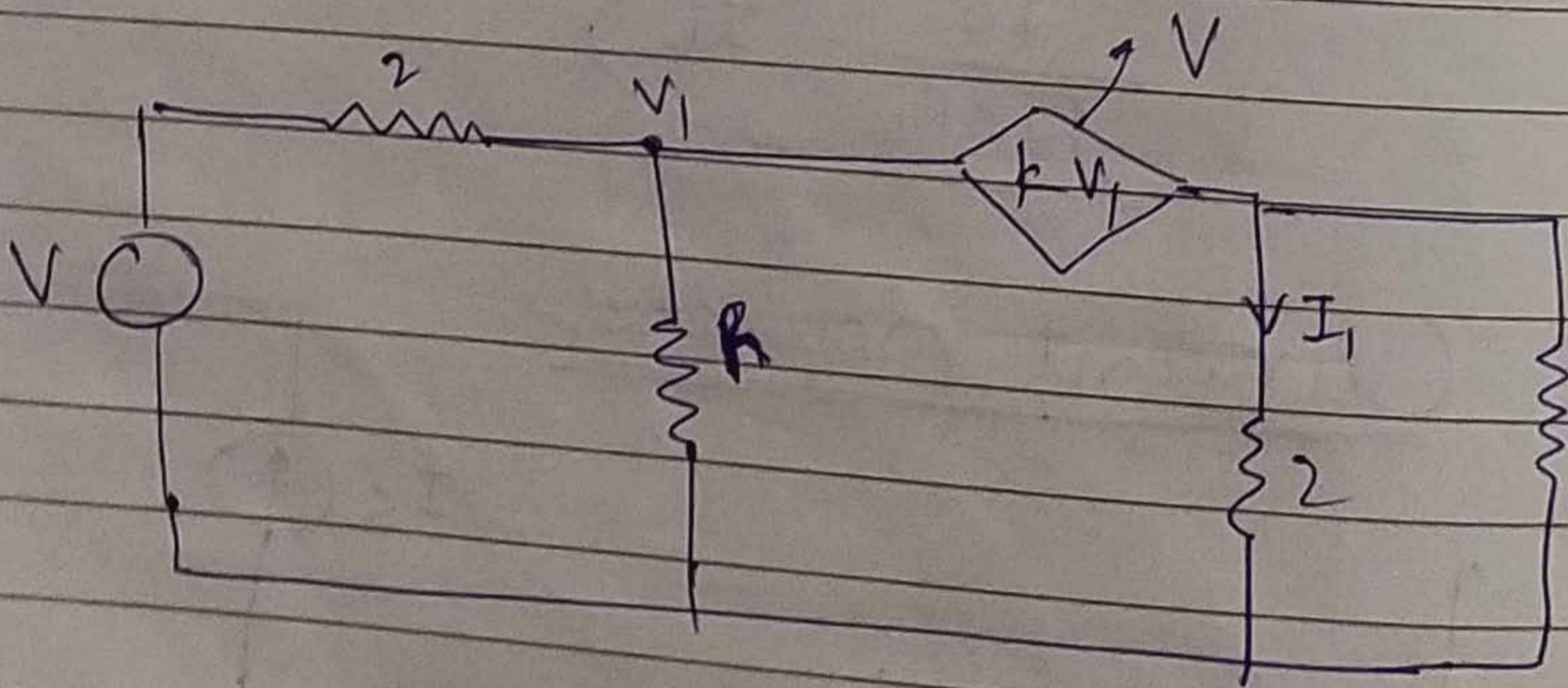

## # Kirchoff's Laws:->

1) KCL

2) KVL

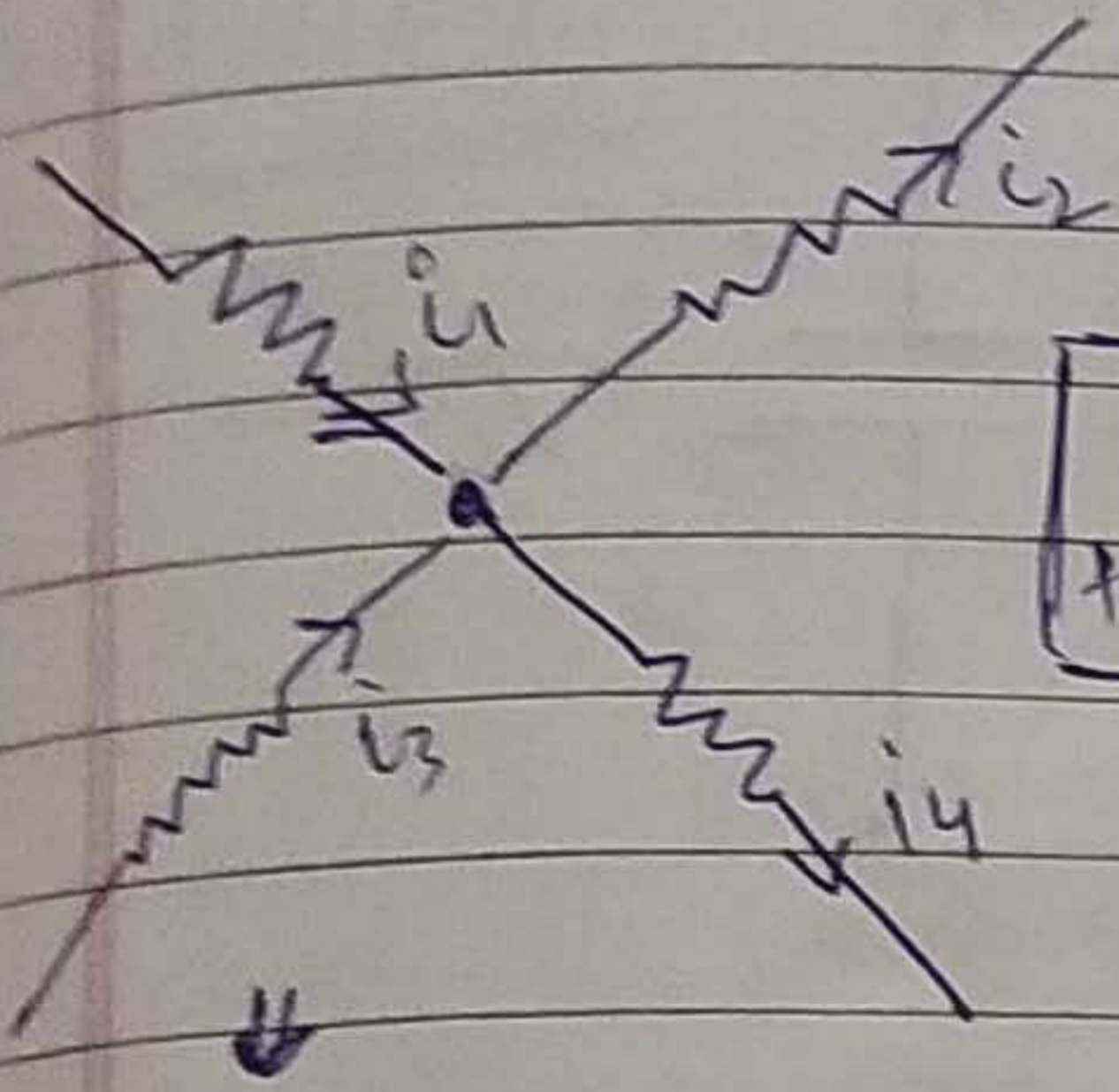

$$\sum_{\text{for all } k} i_k = 0$$

Incoming  $\rightarrow$  -ve  
Outgoing  $\rightarrow$  +ve

$$-i_1 - i_3 + i_4 + i_2 = 0$$

$$i_1 + i_3 = i_4 + i_2$$

$$\sum i_{\text{incoming}} = \sum i_{\text{outgoing}}$$

Also;  $i = \frac{dq}{dt}$


$$\therefore \frac{dq_1}{dt} + \frac{dq_3}{dt} = \frac{dq_2}{dt} + \frac{dq_4}{dt}$$

$$\Rightarrow q_1 + q_3 = q_2 + q_4$$

$\rightarrow$  Thus, it follows law of conservation of charge.

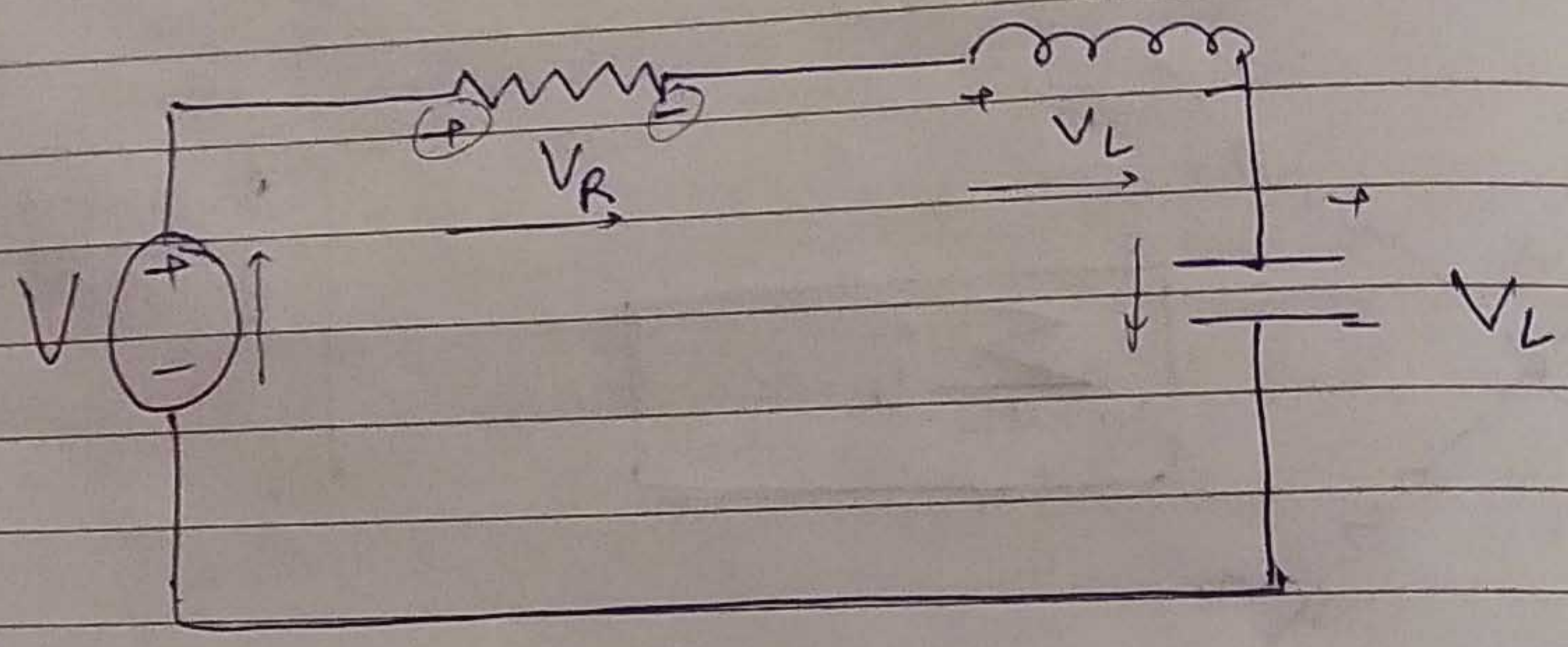2) KVL  $\rightarrow$  sum of voltage in a loop is zero

$\Rightarrow \sum_{\text{for all } k} V_k = 0 \rightarrow$  in a loop



Sign convention  
- to +  $\rightarrow$  +ve  
+ to -  $\rightarrow$  -ve

$V - V_R - V_L - V_C = 0$

$V = V_R + V_L + V_C$

$\sum \text{Voltage rise} = \sum \text{Voltage drops}$


Also,  $V = \frac{dW}{dq}$

$\therefore \frac{dW}{dq} = \frac{dW_R}{dq} + \frac{dW_L}{dq} + \frac{dW_C}{dq}$

$\Rightarrow W = W_R + W_L + W_C$

$\Rightarrow$  KVL follows law of conservation of energy  
 $\rightarrow$  applicable to lumped networks.

Example:

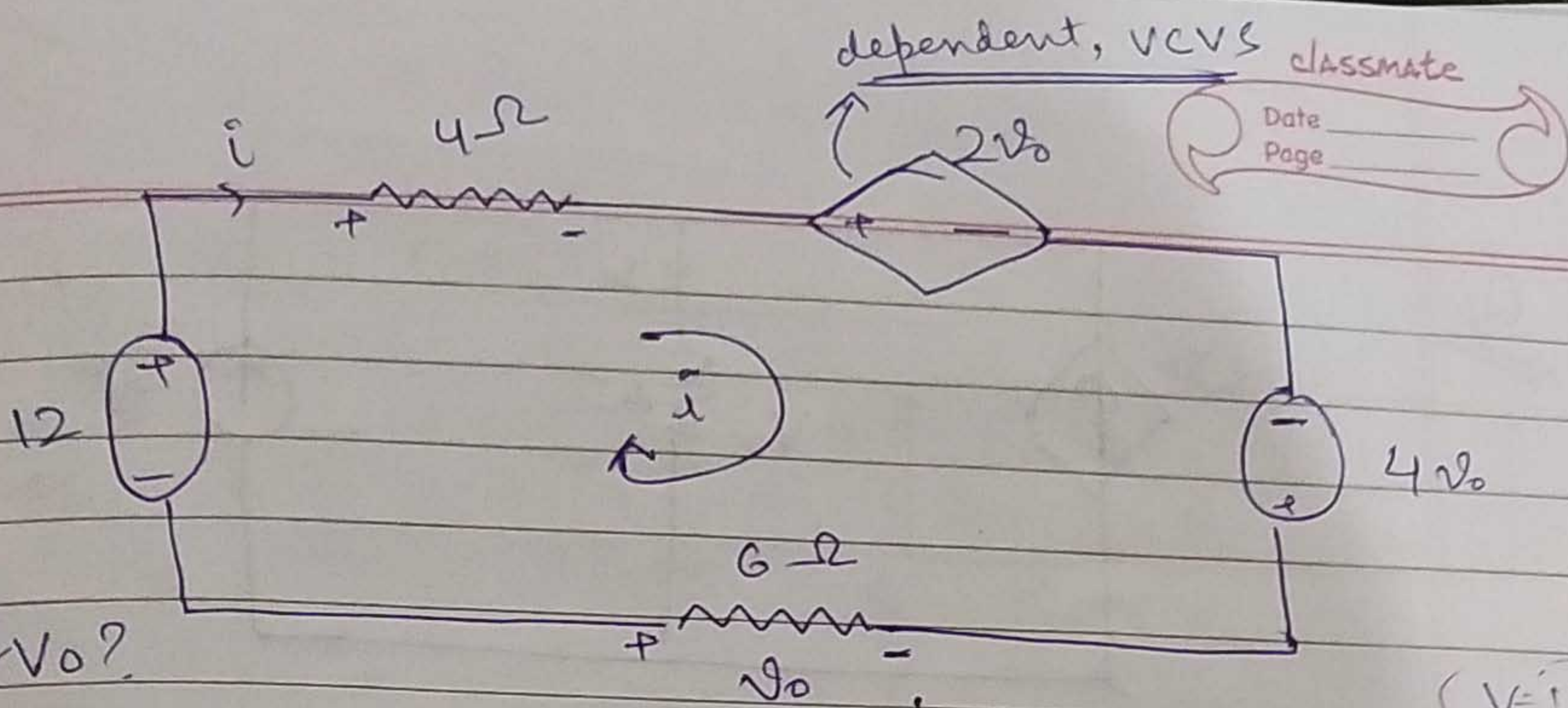

Find  $i$  &  $v_o$ ?

Applying KVL;

$$12 - 4i - 2v_o + 4v_o + v_o = 0$$

$$12 - 4i - 2v_o + 4v_o + v_o = 0$$

$$16 - 4i = v_o = 0$$

$$16 + 4i + 6i = 0$$


$$16 + 2i = 0$$

$$-16 = i$$

$$i = -8A$$

$$v_o = 48V$$

Example:

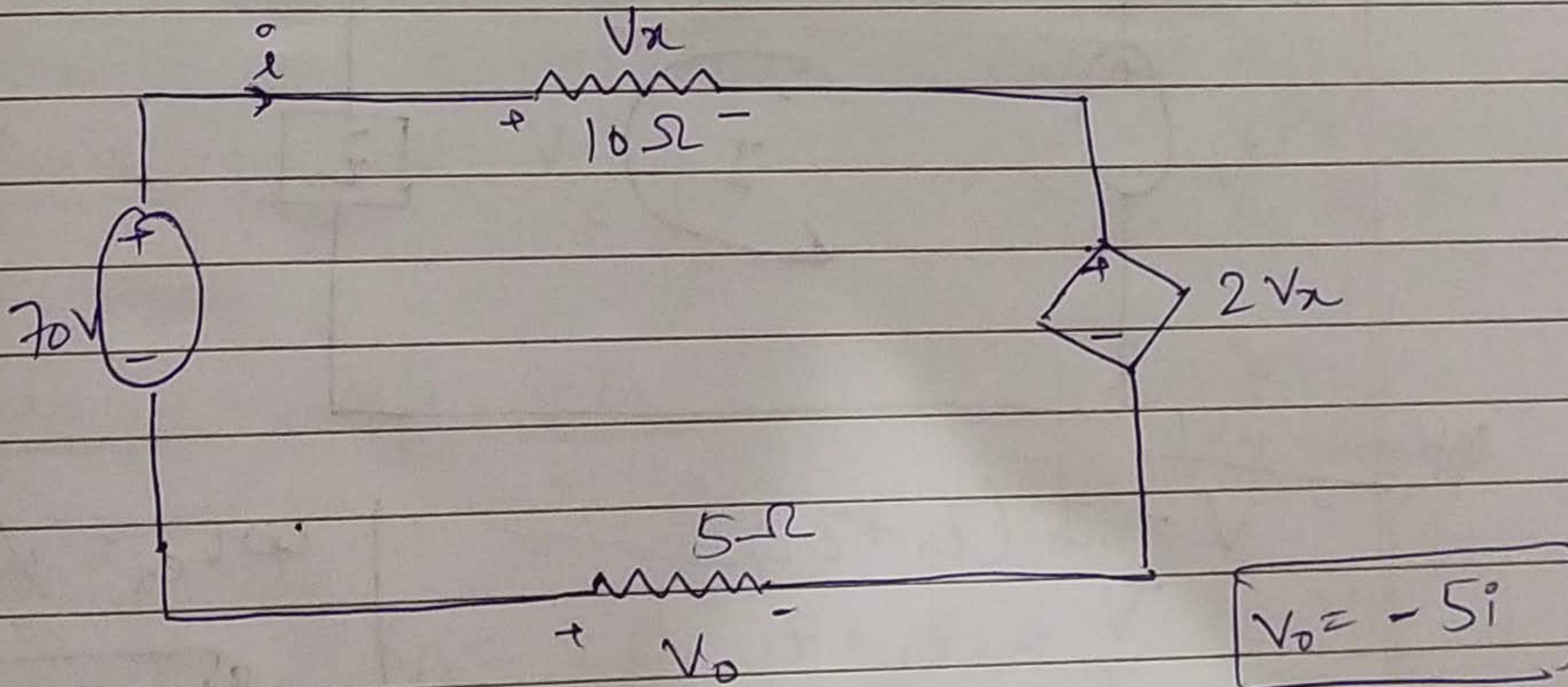

Find  $v_o$  &  $v_x$ ?

$$v_o = -5i$$

$$v_x = -10i$$


$$70 - v_x - 2v_x + v_o = 0$$

$$70 - 3v_x - 5i = 0$$

$$70 + 30i - 5i = 0$$

$$70 + 25i = 0$$

$$i = -\frac{70}{25} = -2.8$$

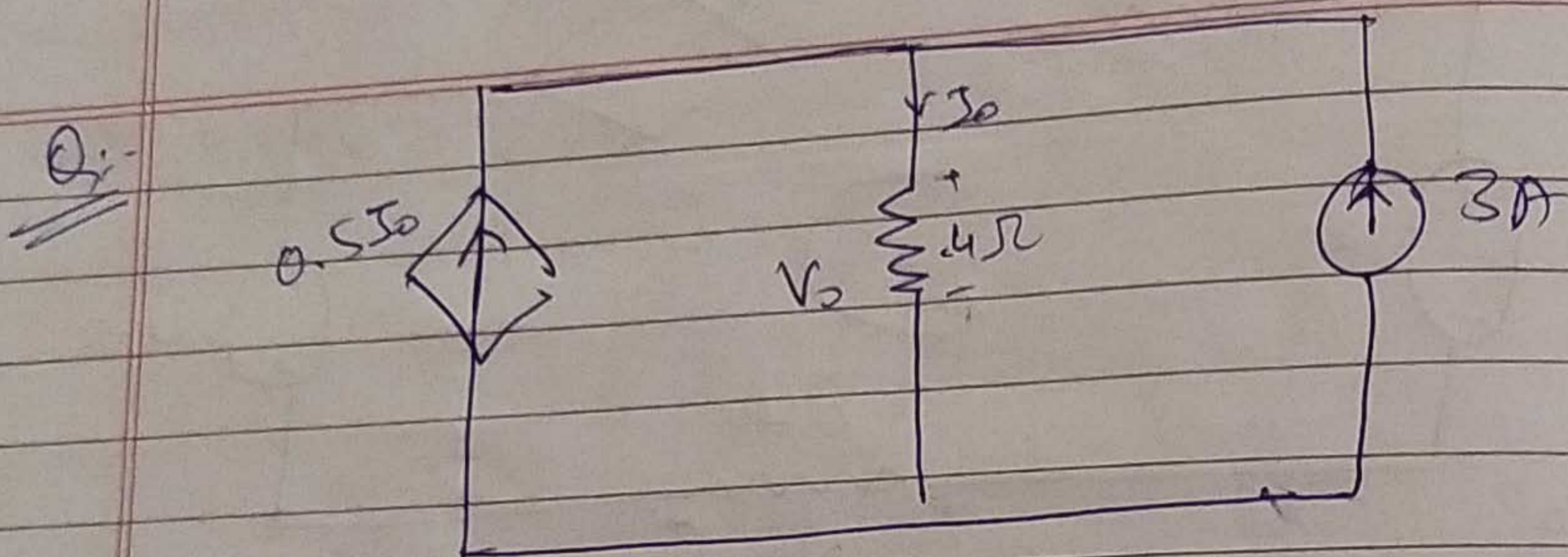

Find  $V_0$  &  $I_0$ ?

Sol:  $0.5I_0 + 3 = I_0$

$$3 = 0.5I_0$$


$$3 \times \frac{2}{1} = I_0$$

$$I_0 = 6$$

$$V_0 = 4I_0$$

$$V_0 = 24V$$

### # SERIES CONNECTION $\Rightarrow$

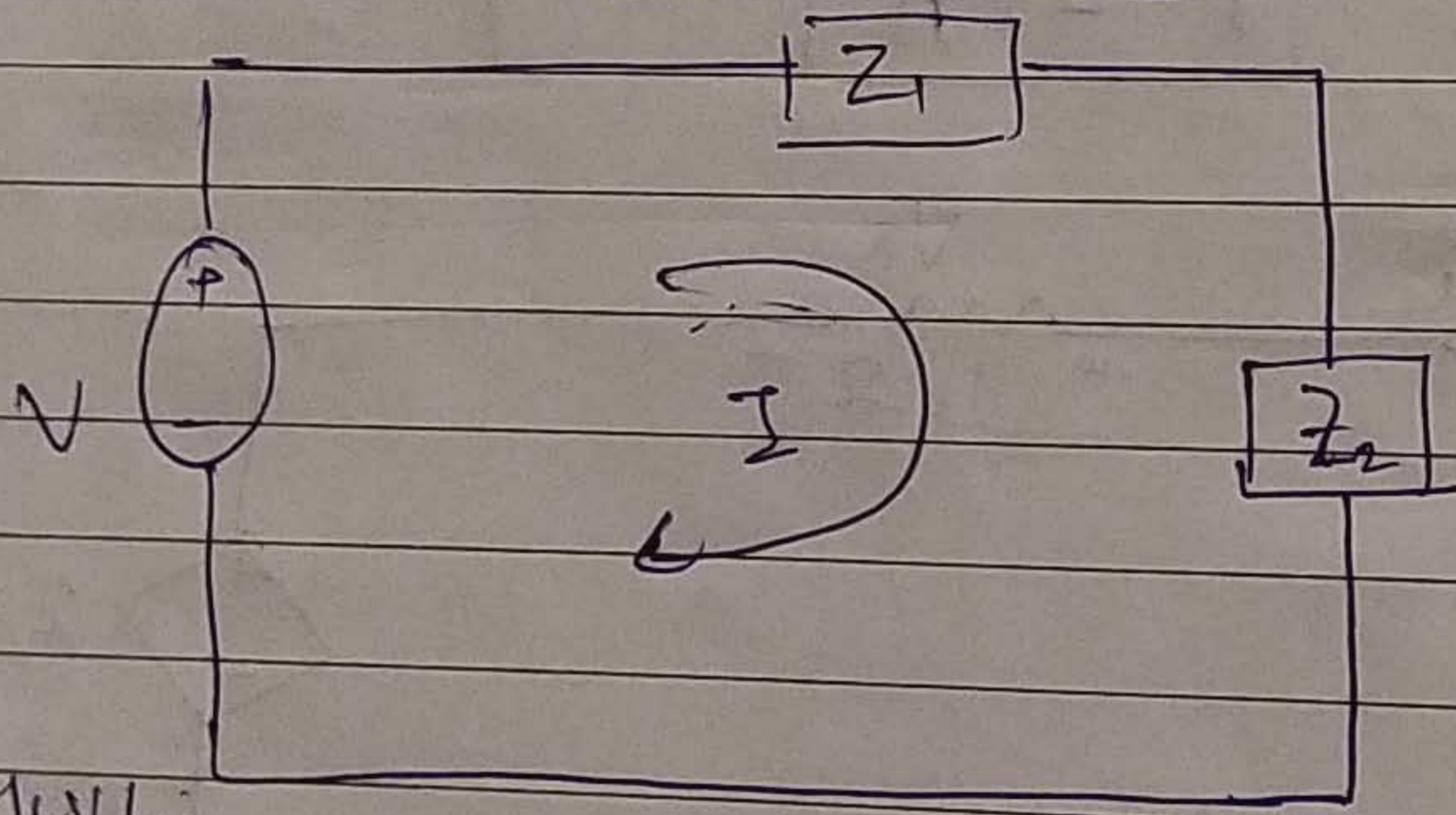

Applying KVL,

$$V = I(Z_1 + Z_2)$$

$$\frac{V}{I} = Z_1 + Z_2$$

$$Z_{eq} = Z_1 + Z_2$$

$$R_{eq} = R_1 + R_2$$

$$X_{Leq} = \omega L_1 + \omega L_2$$

$$X_{Leq} = \omega(L_1 + L_2)$$

$$\omega L_{eq} = \omega(L_1 + L_2)$$

$$L_{eq} = L_1 + L_2$$

$$X_{Ceq} = X_{C1} + X_{C2}$$

$$\frac{1}{\omega C_{eq}} = \frac{1}{\omega C_1} + \frac{1}{\omega C_2}$$

$$\Rightarrow \boxed{\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}}$$

$$Q = CV$$

$$\frac{Q}{C} = V$$

$$V = V_1 + V_2$$

$$\frac{Q}{C_{eq}} = \frac{Q}{C_1} + \frac{Q}{C_2}$$

$$\textcircled{\#} \quad \boxed{I = \frac{V}{Z_1 + Z_2}}$$

$$\therefore V_1 = I Z_1 \Rightarrow$$

$$\boxed{V_1 = \frac{V \cdot Z_1}{(Z_1 + Z_2)}}$$

Voltage  
division  
Rule

$$V_2 = I Z_2 \Rightarrow$$

$$\boxed{V_2 = \frac{V \cdot Z_2}{(Z_1 + Z_2)}}$$

for Resistor;  $V_1 = \frac{V R_1}{R_1 + R_2}$  ,  $V_2 = \frac{V R_2}{R_1 + R_2}$


for Inductor:  $V_1 = \frac{V L_1}{L_1 + L_2}$  ,  $V_2 = \frac{V L_2}{L_1 + L_2}$

for Capacitor:  $V_1 = \frac{V C_2}{C_1 + C_2}$  ,  $V_2 = \frac{V C_1}{C_1 + C_2}$

↓  
Inverse Relation

#  $C_{eq} = C_1 + C_2$

# Parallel Connection :->

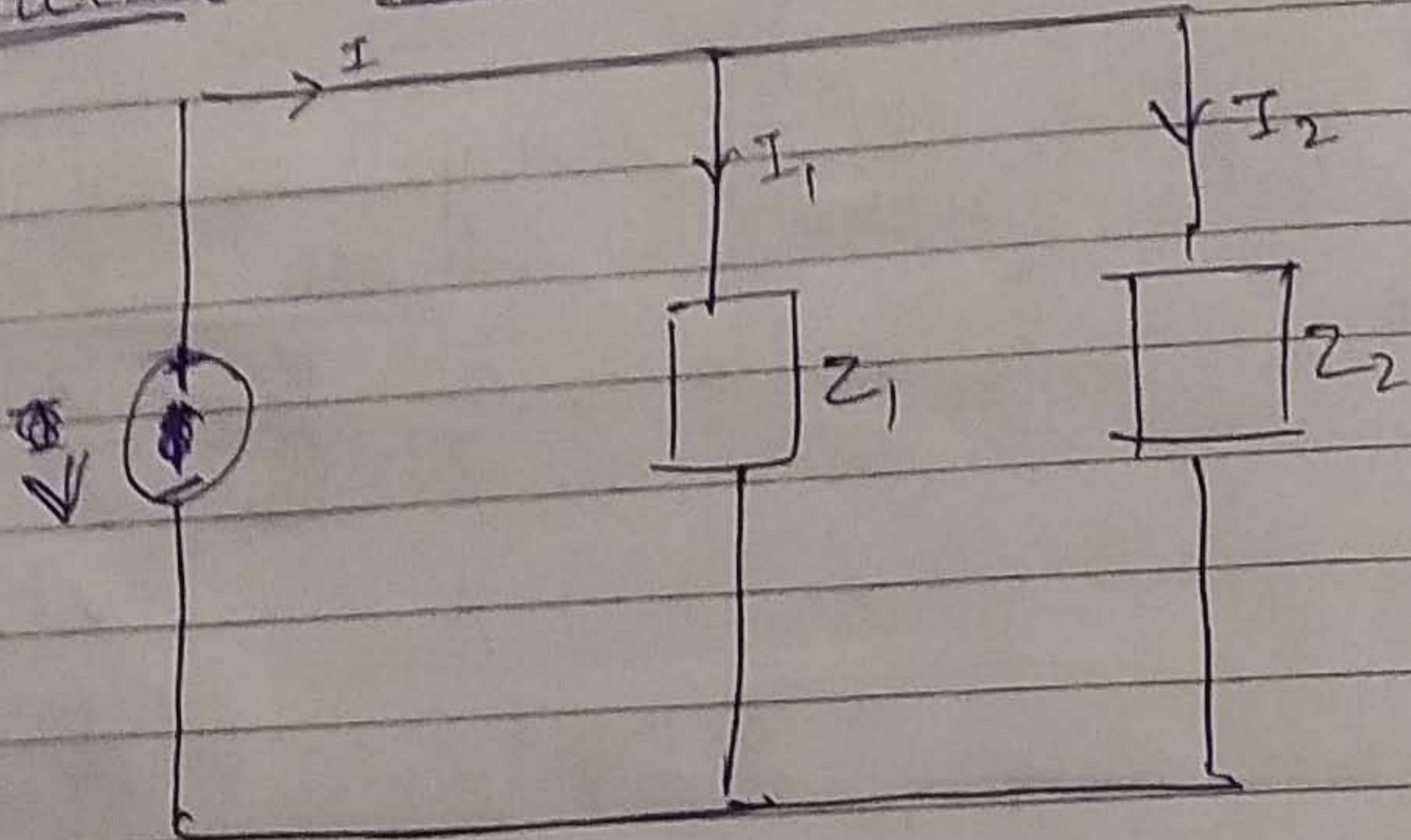

KCL:  $I = I_1 + I_2$

$$\frac{V}{Z_{eq}} = \frac{V}{Z_1} + \frac{V}{Z_2}$$

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

for R;

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

for L;

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

for C;

$$C_{eq} = C_1 + C_2$$

$V = IR$   
 $I = \frac{V}{R_{eq}}$

$$I_1 = \frac{V}{Z_{eq}}$$

$$I_1 = \frac{I Z_{eq}}{Z_1}$$

$$\frac{1}{Z} = \frac{Z_1 + Z_2}{Z_1 Z_2}$$

$$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$I_1 = I \cdot \left( \frac{Z_2}{Z_1 + Z_2} \right)$$

$$I_2 = I \cdot \left( \frac{Z_1}{Z_1 + Z_2} \right)$$

Current division Rule

$I_1 Z = R_1$ 

$$I_1 = \frac{I \cdot R_2}{R_1 + R_2}$$

$$I_2 = \frac{I \cdot R_1}{R_1 + R_2}$$

 $I_1 Z = L_1$ 

$$I_1 = \frac{I \cdot L_2}{L_1 + L_2}$$


$$I_2 = \frac{I \cdot L_1}{L_1 + L_2}$$

 $I_1 Z = C_1$ 

$$I_1 = \frac{I \cdot C_2}{C_1 + C_2}$$

$$I_2 = \frac{I \cdot C_1}{C_1 + C_2}$$
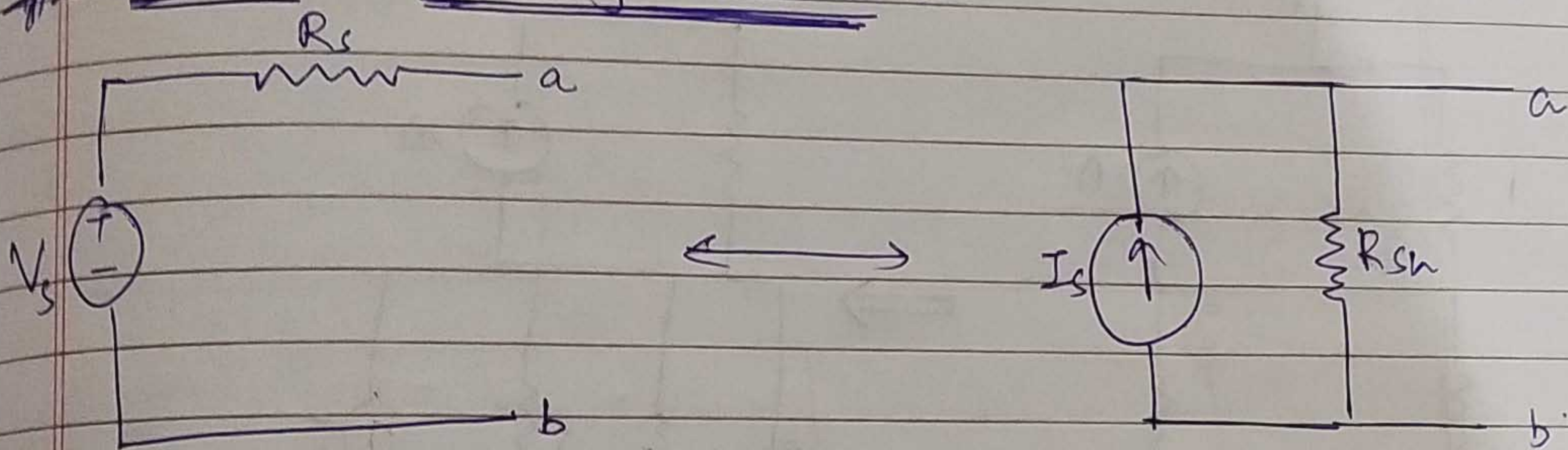
### # Source Transformation $\Rightarrow$



$$I_s = \frac{V_s}{R_{sh}}$$

$$R_{sh} = R_s$$

We can convert voltage source into current source by adding a shunt resistance parallel to it.






KVL

$$\sum_{\#k} V_k = 0$$



KCL

$$\sum_{\#k} i_k = 0$$

Examples

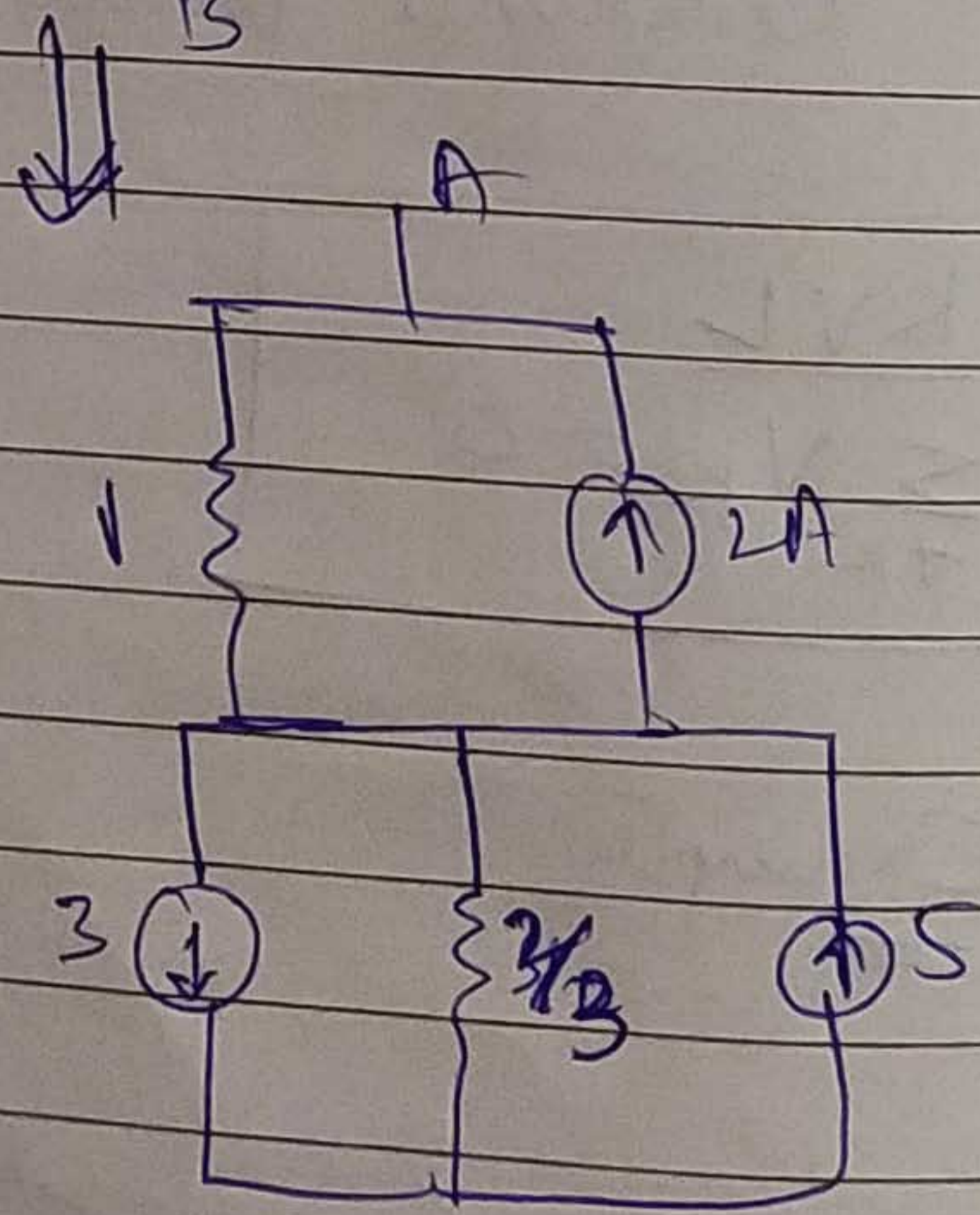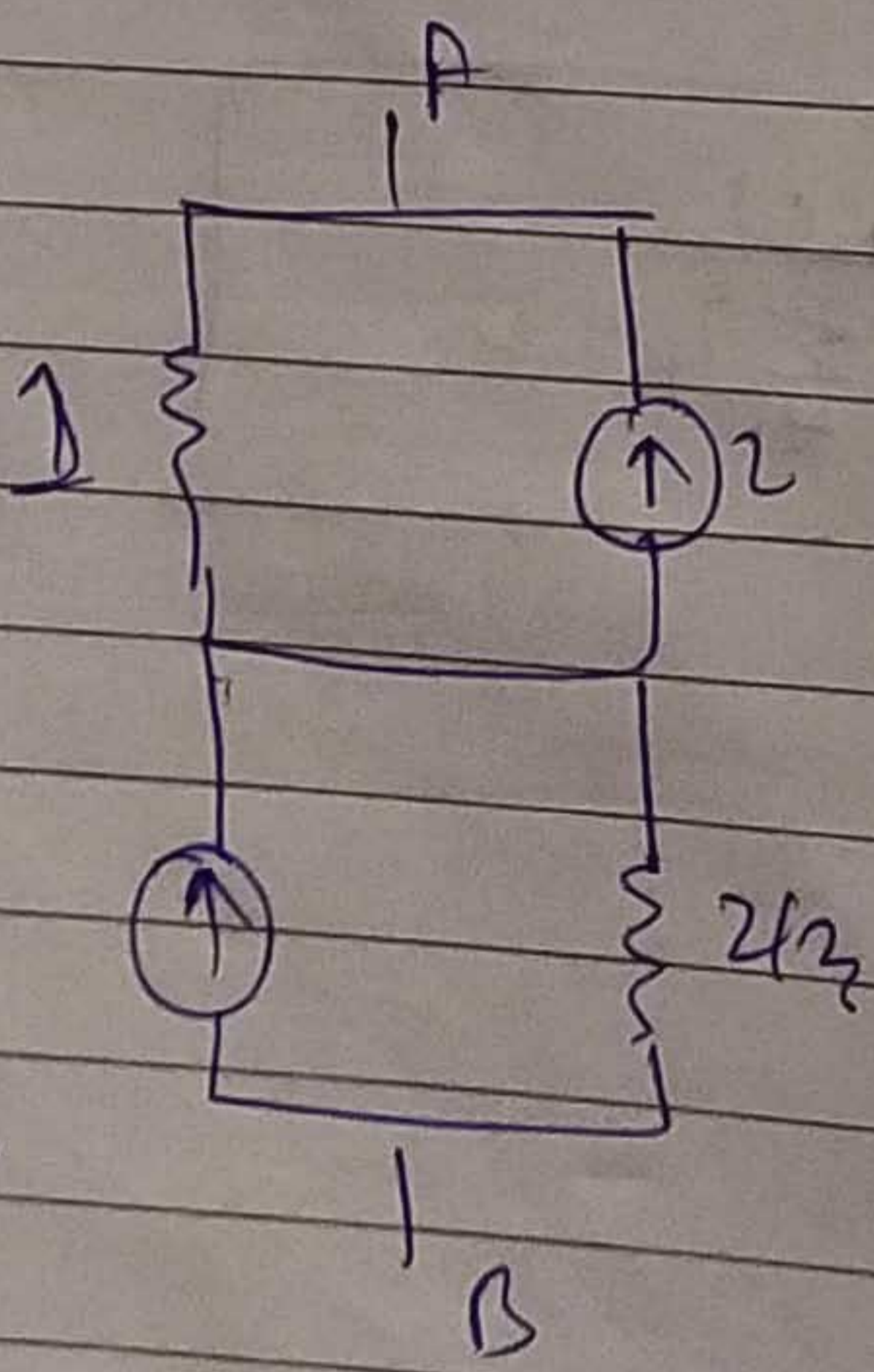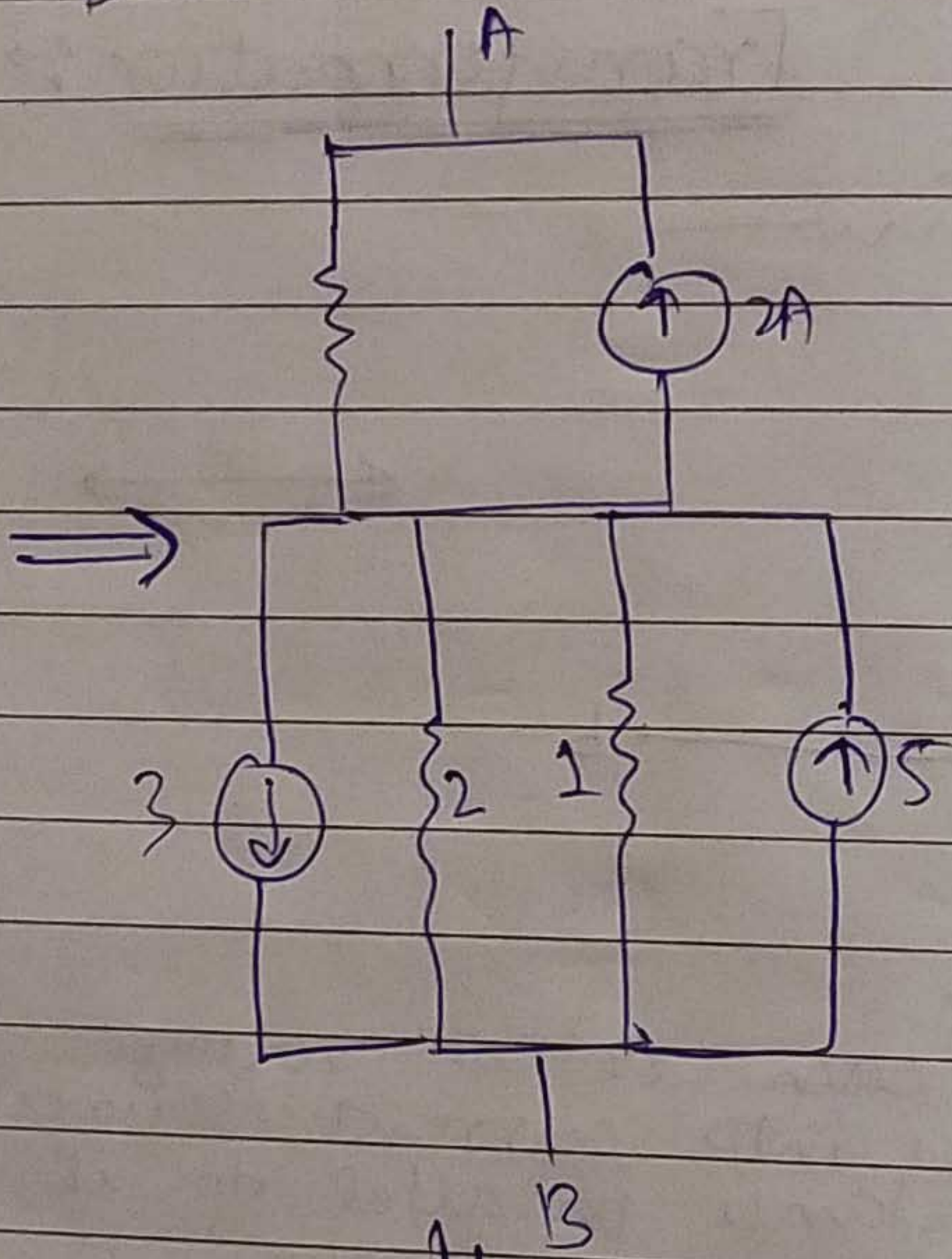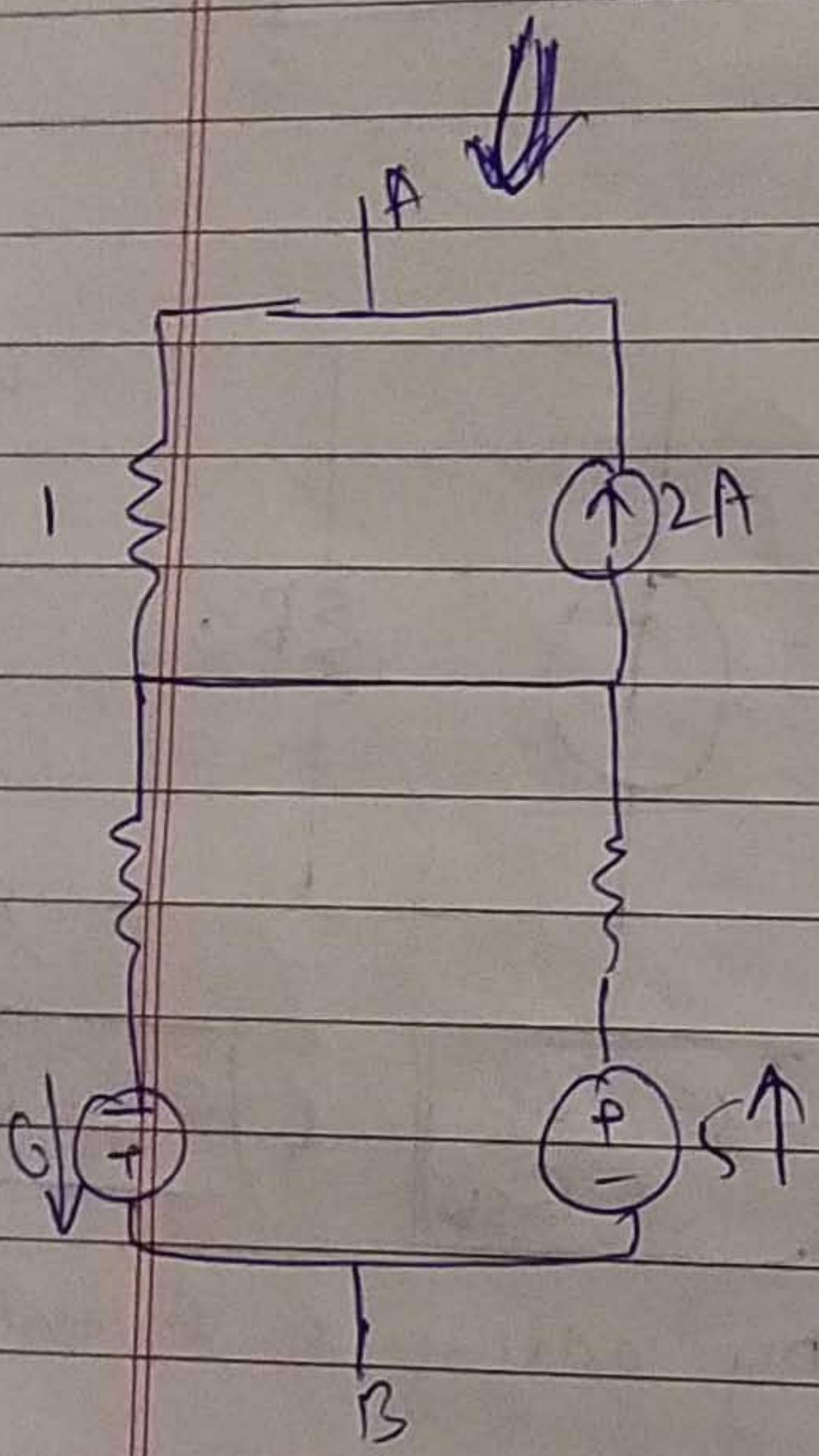
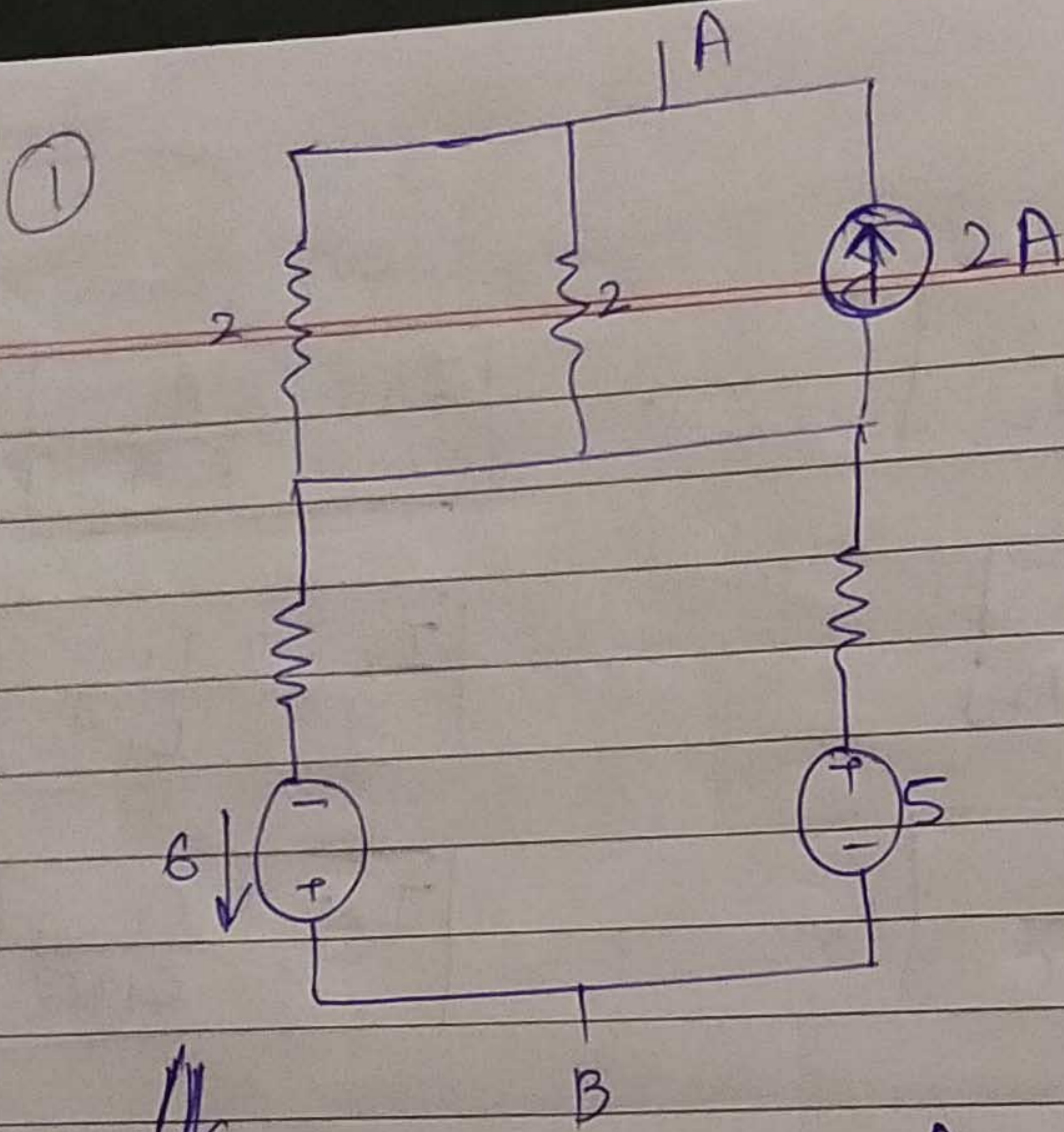


PTD

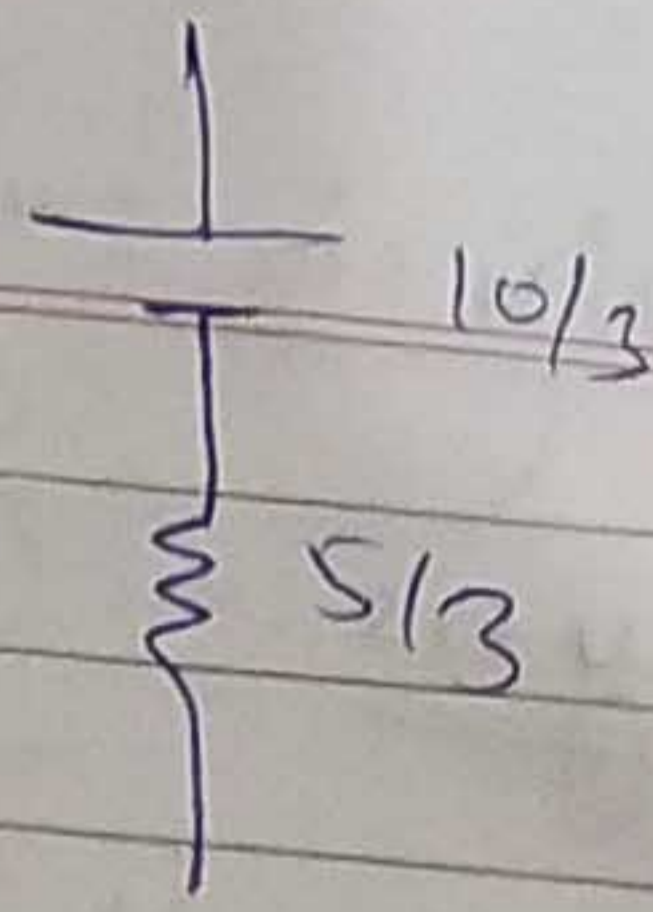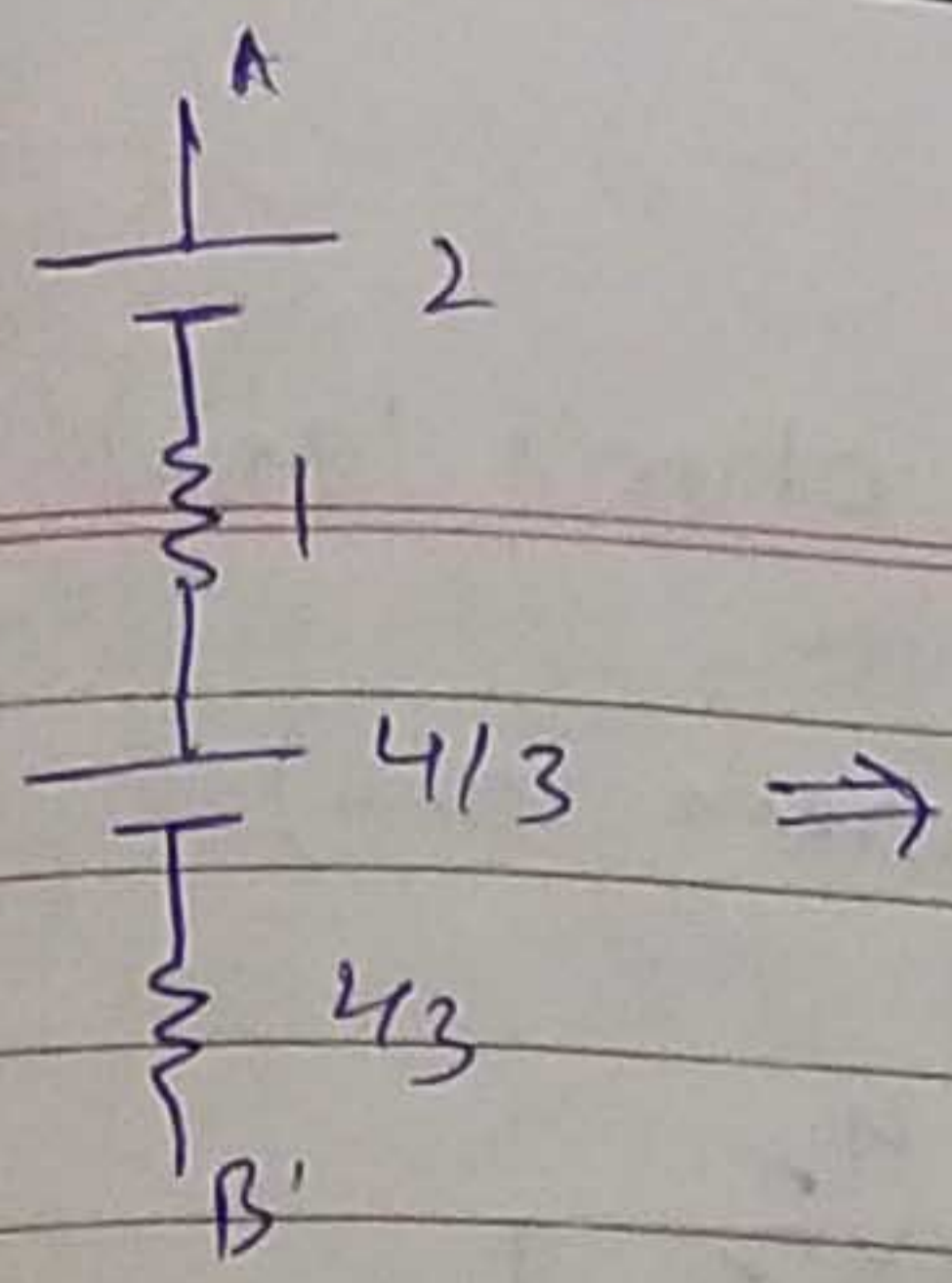



classmate  
Date \_\_\_\_\_  
Page \_\_\_\_\_

Concept:

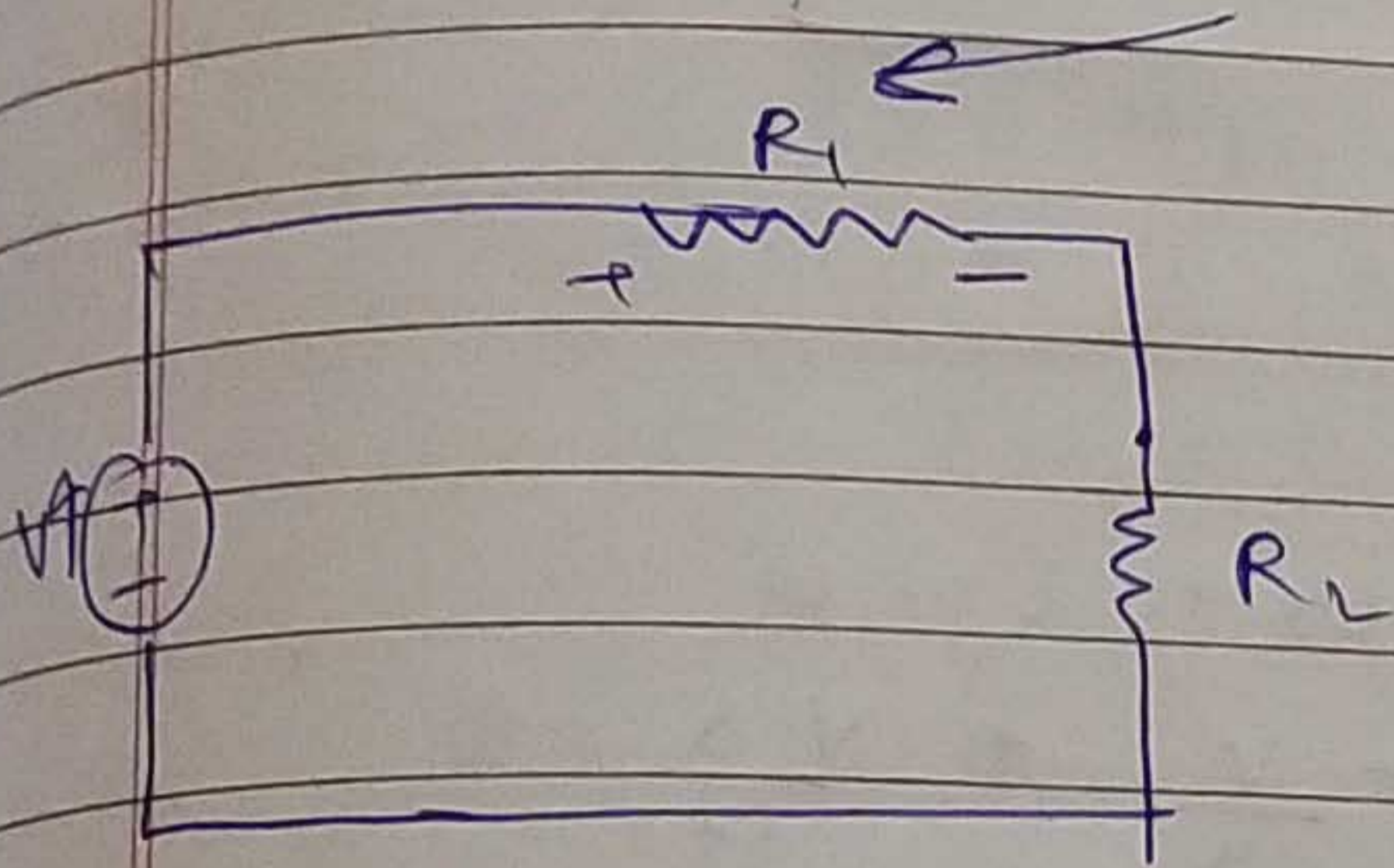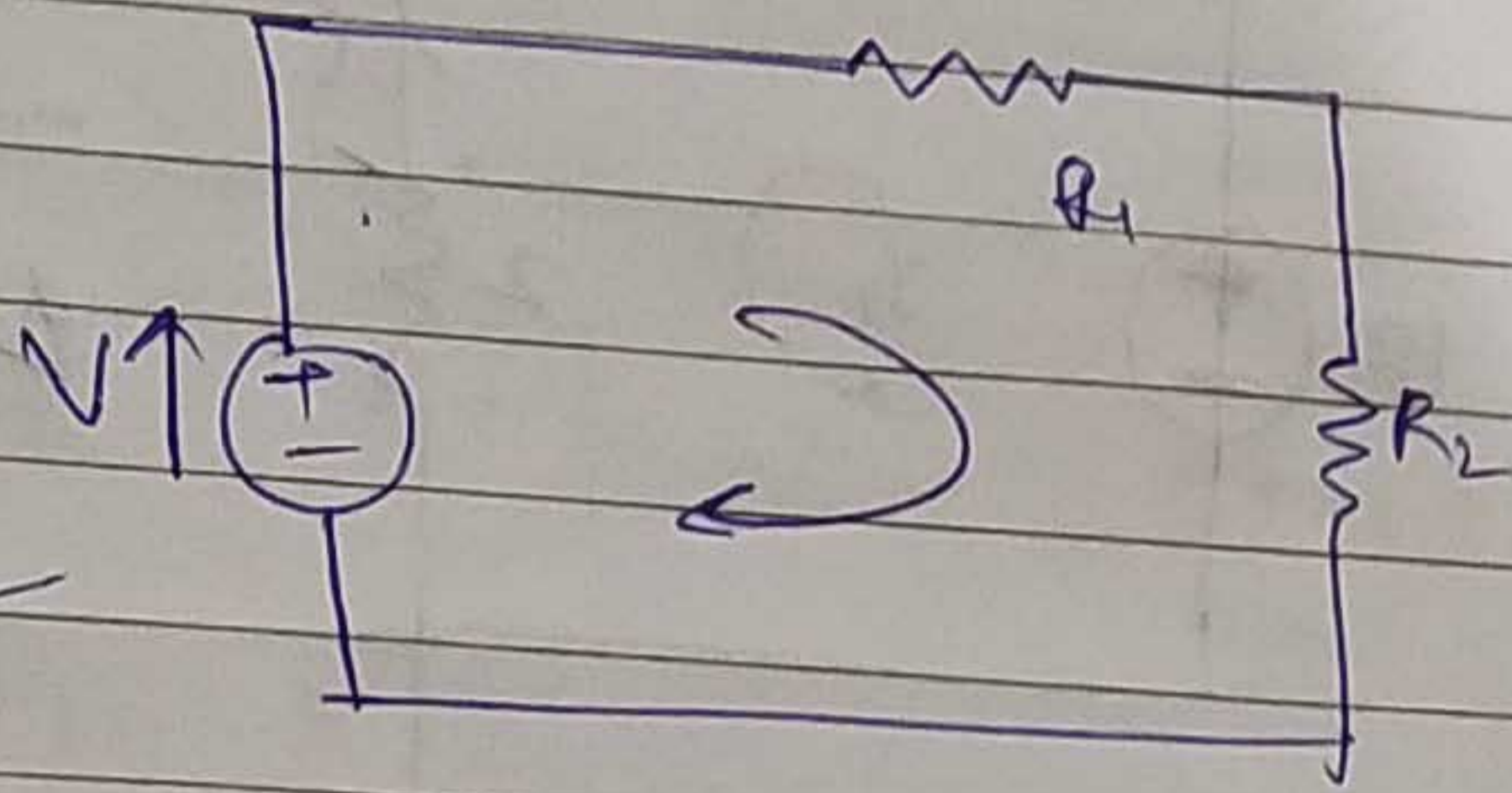


$2+2 \neq 0$   
KCL violated


Questions:

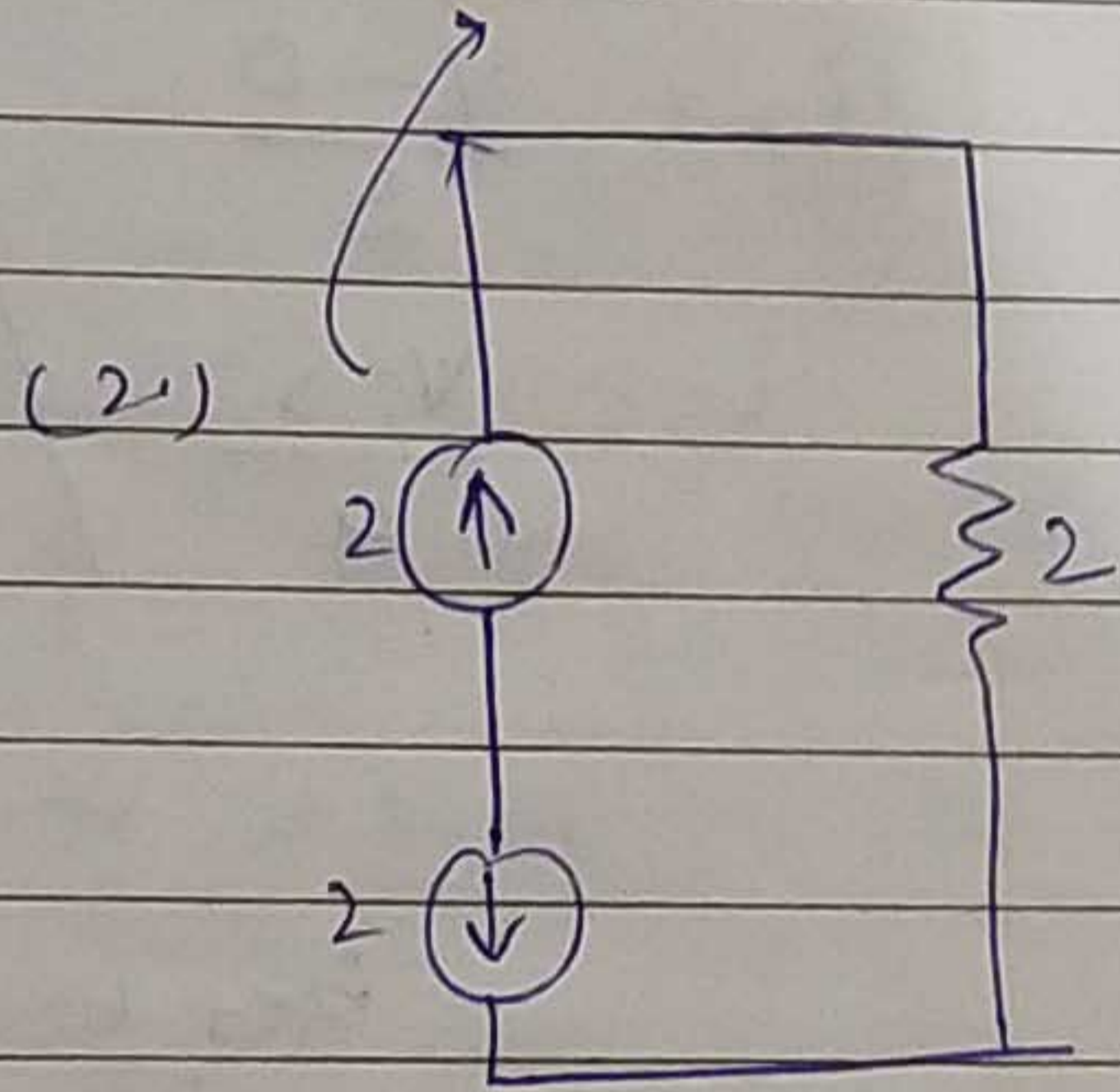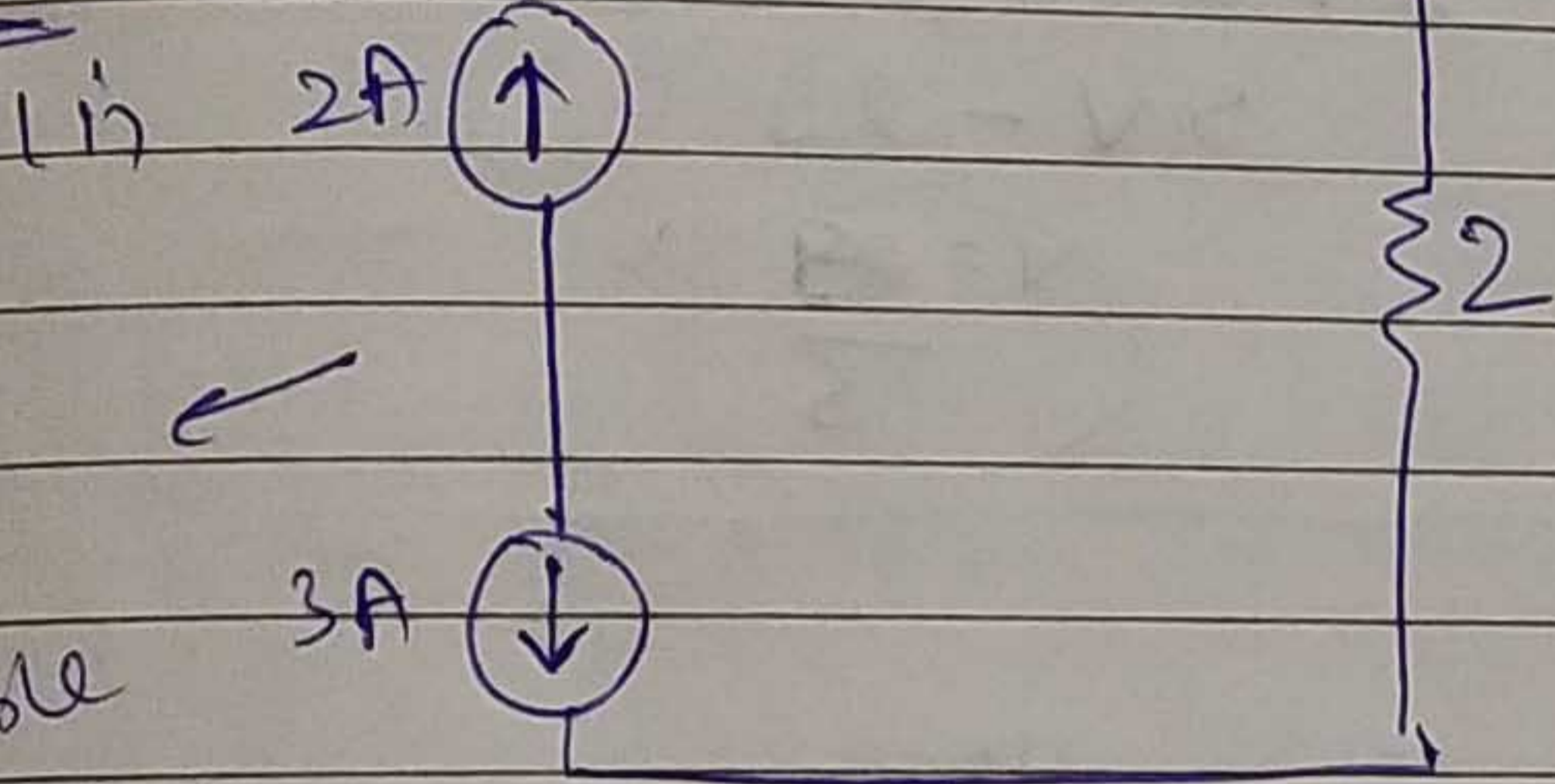

3)

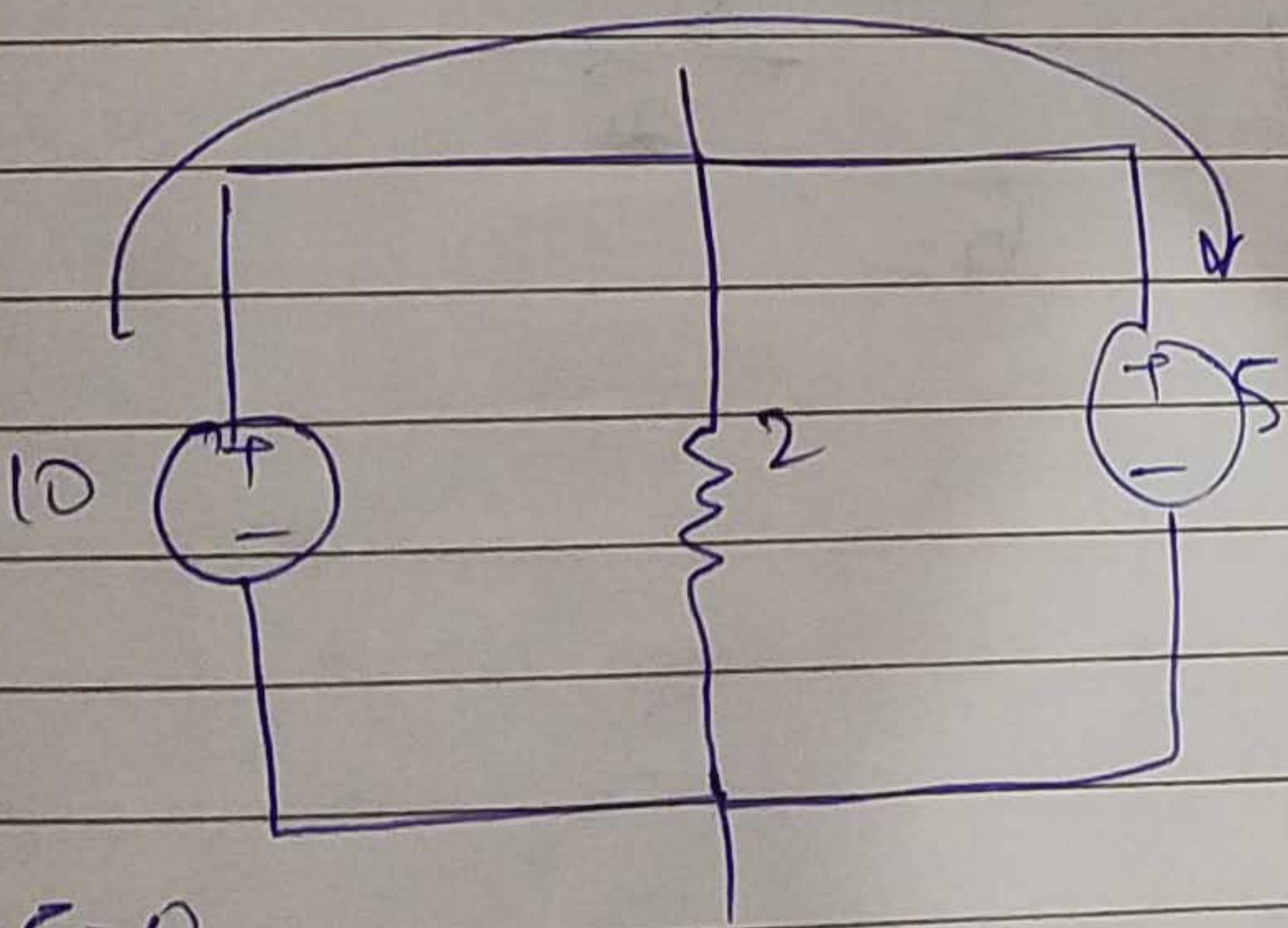


$10-5=0$   
↓  
KVL violated

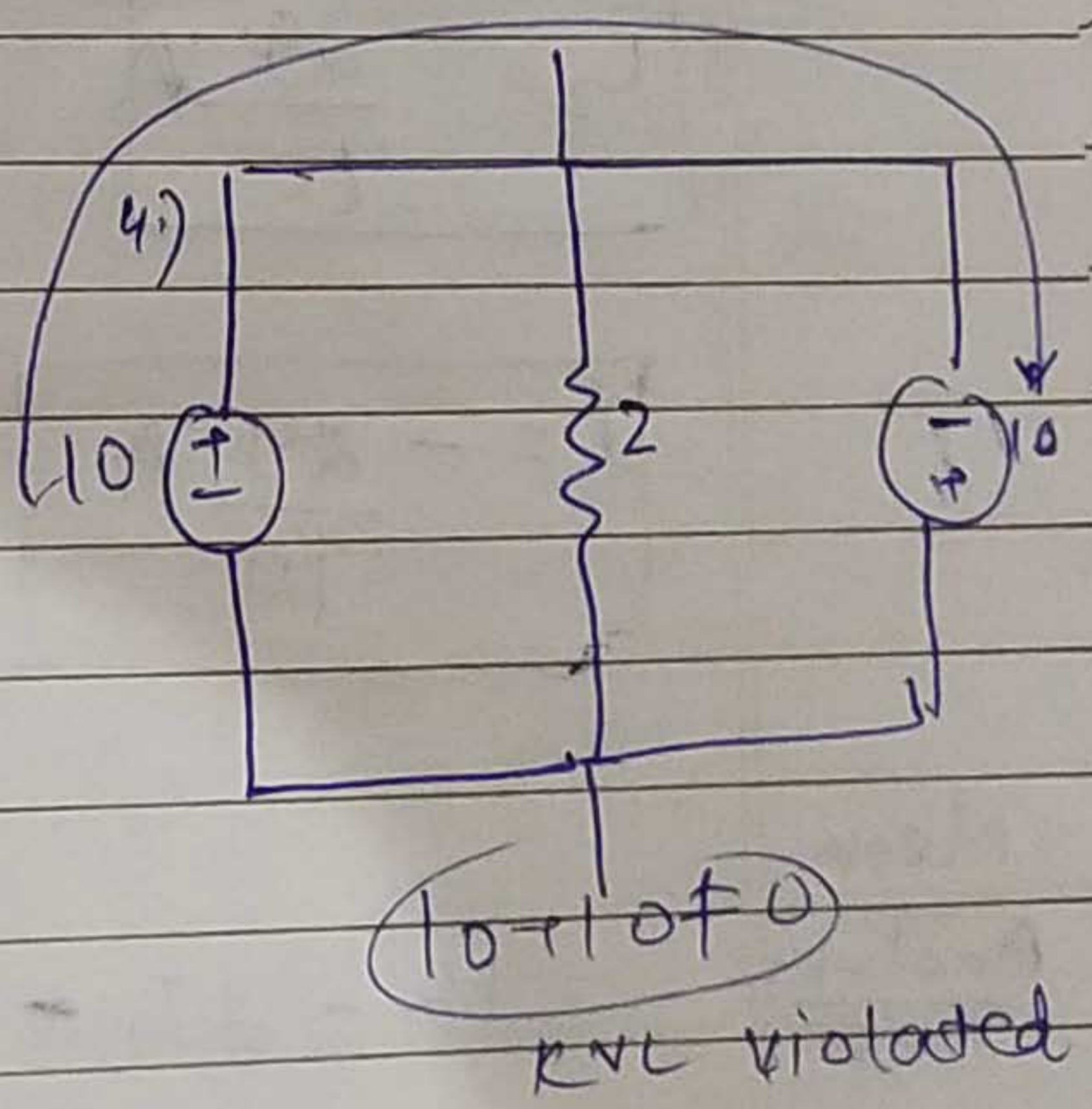

$(10-10=0)$   
KVL violated
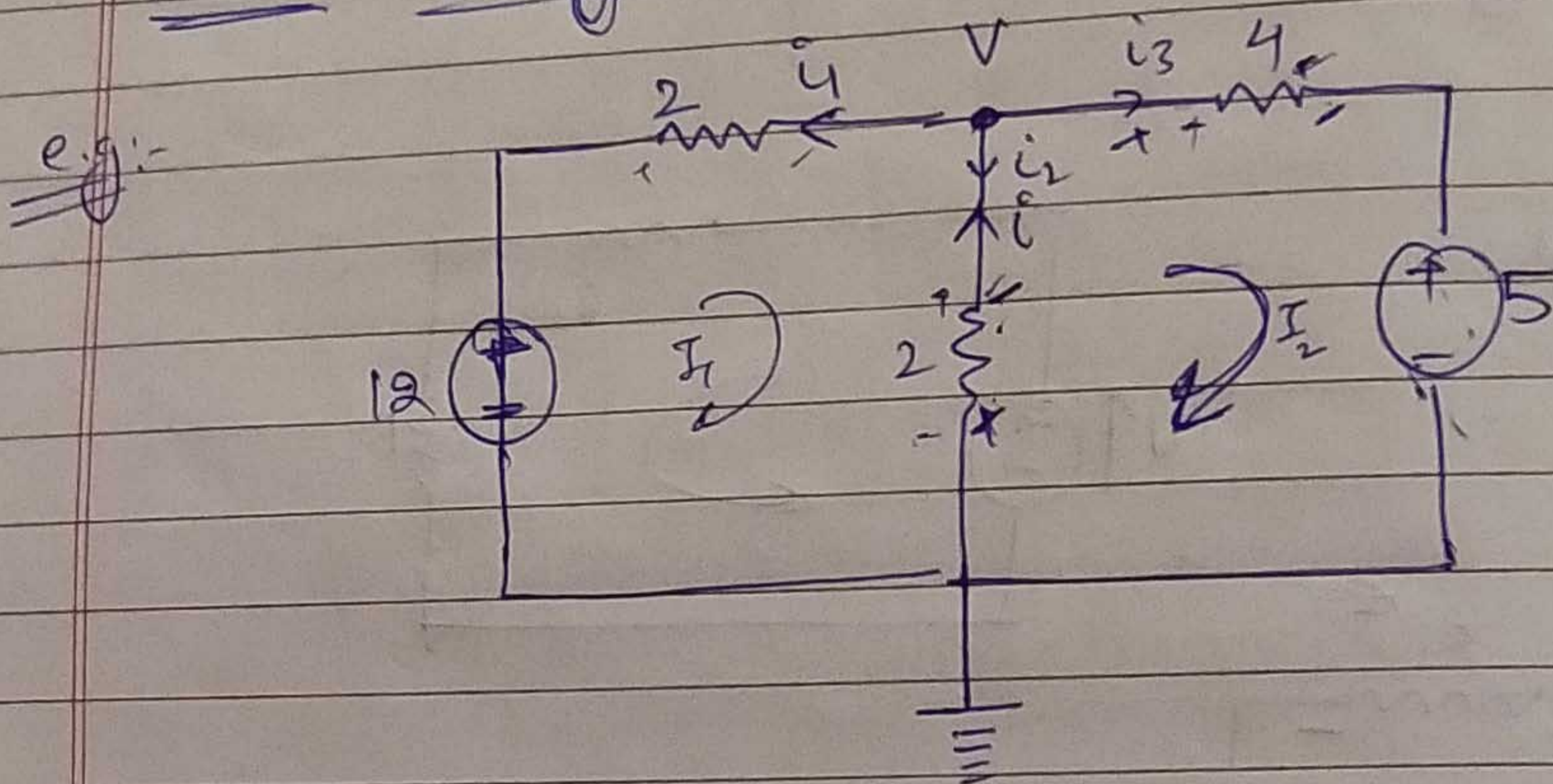
#. Nodal Analysis  $\Rightarrow$  (KCL + ohm's law)

Mesh Analysis  $\Rightarrow$  (KVL + ohm's law)



Nodal

Analysis:

$$i_1 = \frac{V-12}{2}$$

$$i_2 = \frac{V-0}{2}$$

$$i_3 = \frac{V-5}{4}$$

$$i_1 + i_2 + i_3 = 0$$

$$\frac{V-12}{2} + \frac{V}{2} + \frac{V-5}{4} = 0$$

$$2V-24 + 2V + V-5 = 0$$

$$5V - 29 = 0$$

$$V = \frac{29}{5} \text{ V}$$

$$i_1 + i_2 = i_3$$

$$i_2 = \frac{29}{10} \text{ V}$$

$$i_1 = \frac{29}{5} \text{ A}$$

$$i_3 =$$

$$I_1 = -\frac{29}{10} \text{ A}$$

Mesh  
Analysis

$$12 - 2I_1 + 2(I_1 - I_2) = 0$$

$$12 - 2I_1 + 2I_1 + 2I_2 = 0$$

$$12 - 4I_1 + 2I_2 = 0$$

$$-4i_2 - 5 \Rightarrow 2(i_2)$$

class 12  
Date \_\_\_\_\_  
Page \_\_\_\_\_

$$\begin{aligned} -5 + 2(I_2 - I_1) + 4I_2 &= 0 \\ -5 + 2I_2 - 2I_1 + 4I_2 &= 0 \\ -5 - 2I_1 + 6I_2 &= 0 \end{aligned}$$

$$\begin{aligned} 4i_2 + 5 + 2(i_2 - 4) &= 0 \\ 6i_2 + 2i_1 + 5 &= 0 \end{aligned}$$

$$12 = 4I_1 - 2I_2$$

$$-5 = -2I_1 + 6I_2$$

$$\begin{aligned} 12 &= 4I_1 - 2I_2 \\ -10 &= -2I_1 + 6I_2 \end{aligned}$$

$$2 = 10I_2$$

$$I_2 = \frac{1}{5} \text{ A}$$

$$12 + \frac{2}{5} = 4I_1$$

$$\frac{31}{10}$$

$$4I_1 = \frac{62}{5}$$


$$I_1 = \frac{31}{10} \text{ A}$$

$$I = I_2 - I_1$$

$$= \frac{1}{5} - \frac{31}{10}$$


$$I = -\frac{29}{10} \text{ A}$$

Ques

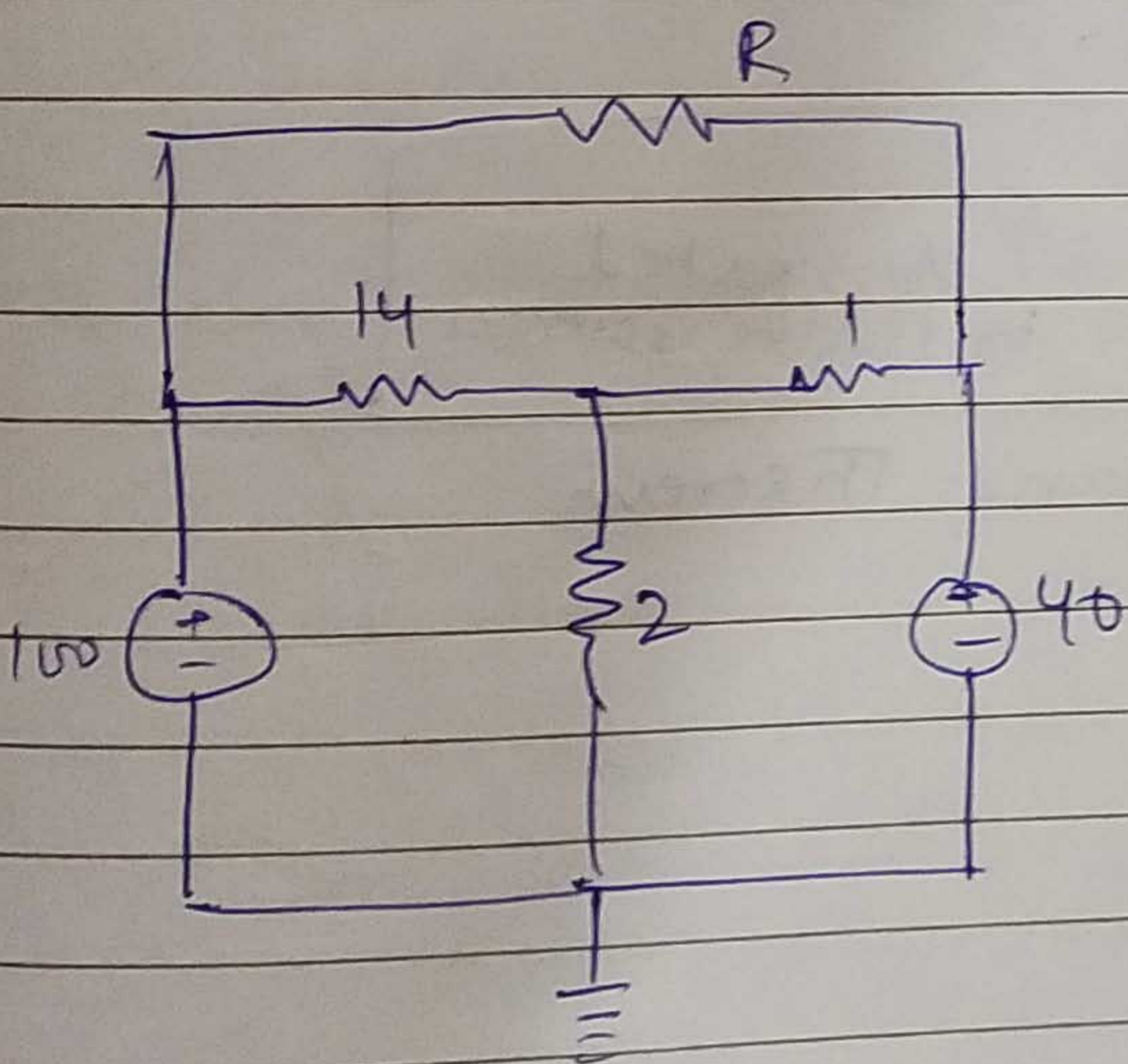

R = ?

Ques.

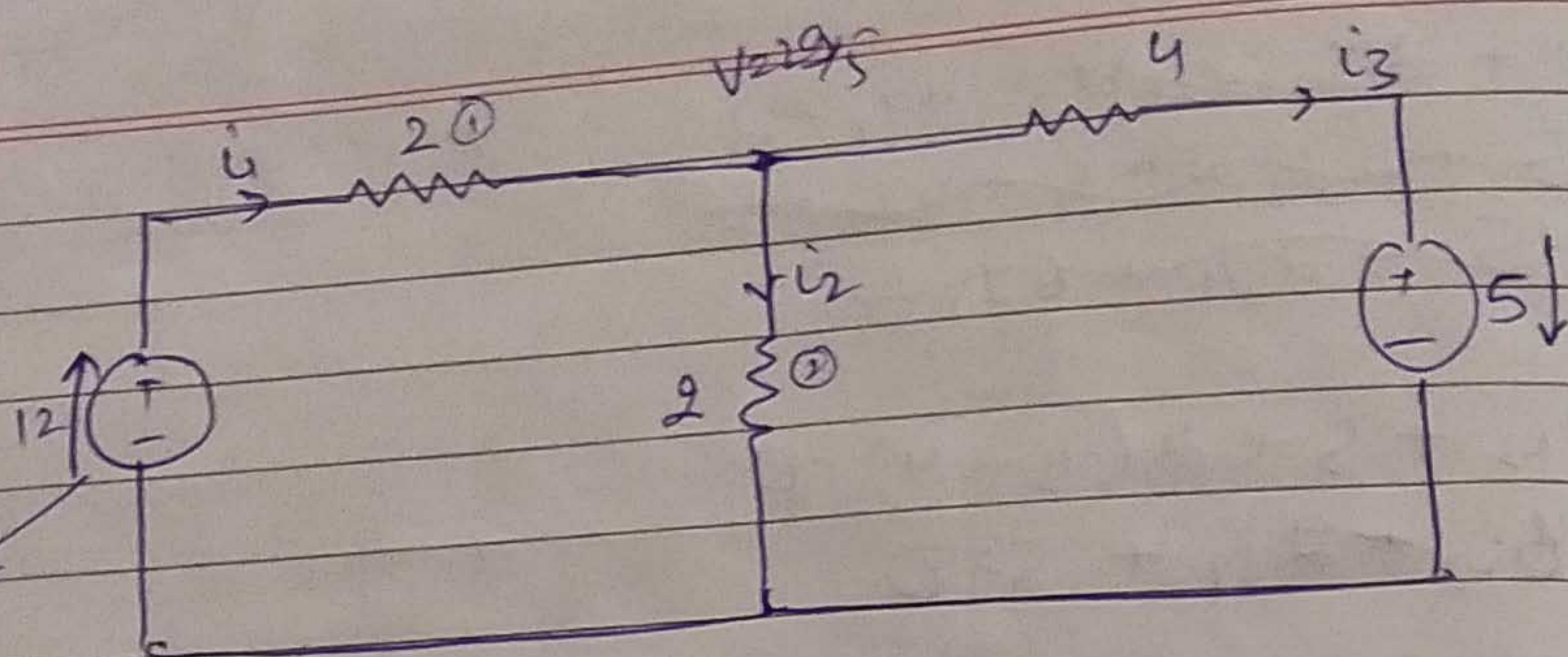

$$P = 12 \times 3.1 = 37.2 \text{ W}$$

$$i_1 = \frac{12 - 5.8}{2} = 3.1$$

$$i_2 = \frac{5.8 - 0}{2} = 2.9$$

$$i_3 = \frac{5.8 - 5}{4} = 0.2$$

$$\begin{aligned} \textcircled{1} P_{2\Omega} &= i_1^2 R \\ &= (3.1)^2 \cdot 2 \\ &= 19.22 \text{ W} \end{aligned}$$

$$\begin{aligned} P_{4\Omega} &= 0.2^2 \times 4 \\ &= 0.16 \text{ W} \end{aligned}$$

$$\begin{aligned} \textcircled{2} P_{2\Omega} &= 2.9^2 \times 2 \\ &= 16.82 \text{ W} \end{aligned}$$


$$P_{5V} = 5 \times 0.2 = 1$$

$$P_T = 37.2 \text{ W}$$

$$P_{\text{delivered by active source}} = P_{\text{dissipated by passive sources}}$$


↳ Tellegen's Theorem

Ques

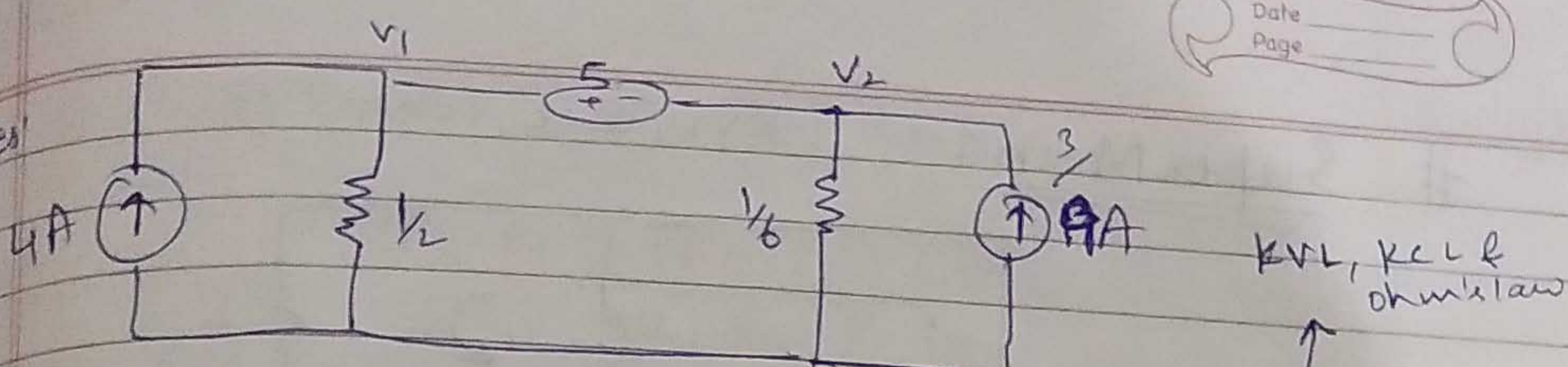Find  $V_1$  &  $V_2 = ?$ KVL, KCL & Ohm's law  
↳ (Super node)

$$V_1 - 5 = V_2$$

$$\boxed{V_1 - V_2 = 5 \text{ V}}$$

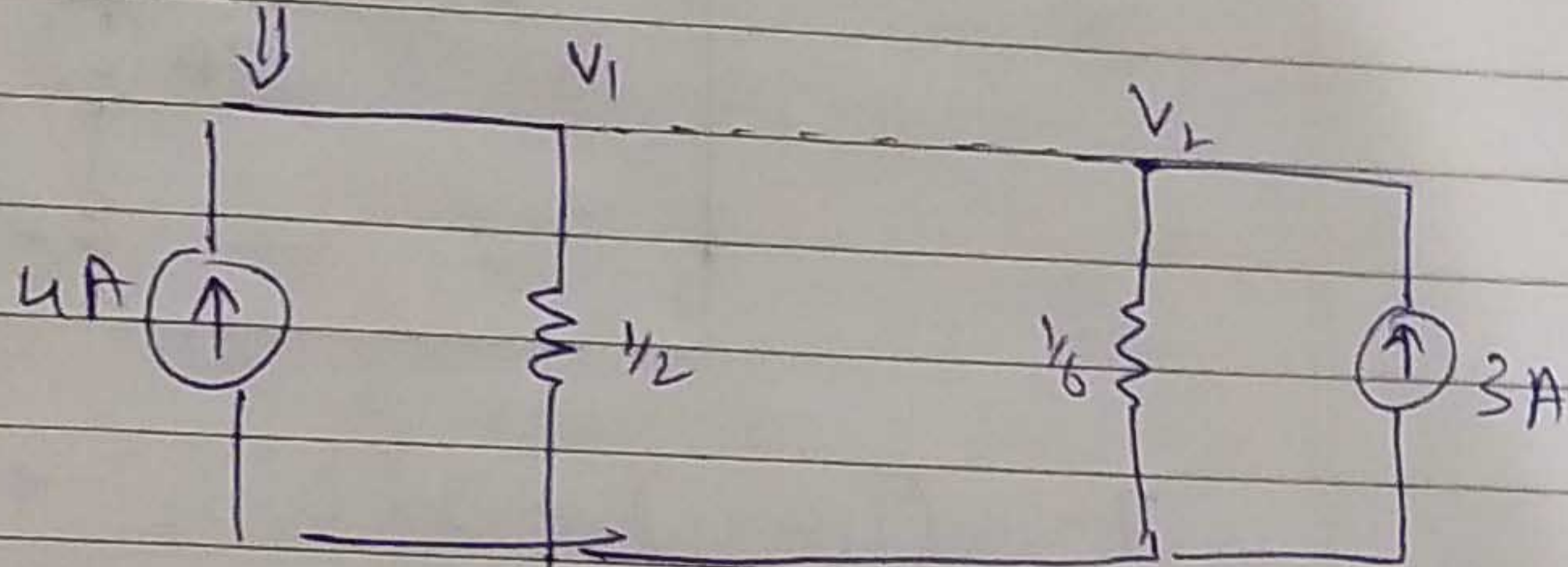

$$4 = \frac{V_1}{1/2} + \frac{V_2}{1/6} - 3$$

$$\boxed{7 = 2V_1 + 6V_2}$$

$$6V_1 - 6V_2 = 30$$

$$2V_1 + 6V_2 = 7$$

$$8V_1 = 31$$

$$\boxed{V_1 = \frac{31}{8} \text{ V}}$$

$$V_2 = \frac{31}{8} - 5$$

$$\boxed{V_2 = -\frac{9}{8} \text{ V}}$$

$$13 = 2V_1 + 6V_2$$

$$30 = 6V_1 - 6V_2$$

$$43 = 8V_1$$


$$\boxed{V_1 = \frac{43}{8} \text{ V}}$$

$$V_2 = \frac{43}{8} - 5$$

$$\boxed{V_2 = \frac{3}{8} \text{ V}}$$

7/11/2019  
#

Super Mesh → (KVL, KCL, ohm's law)

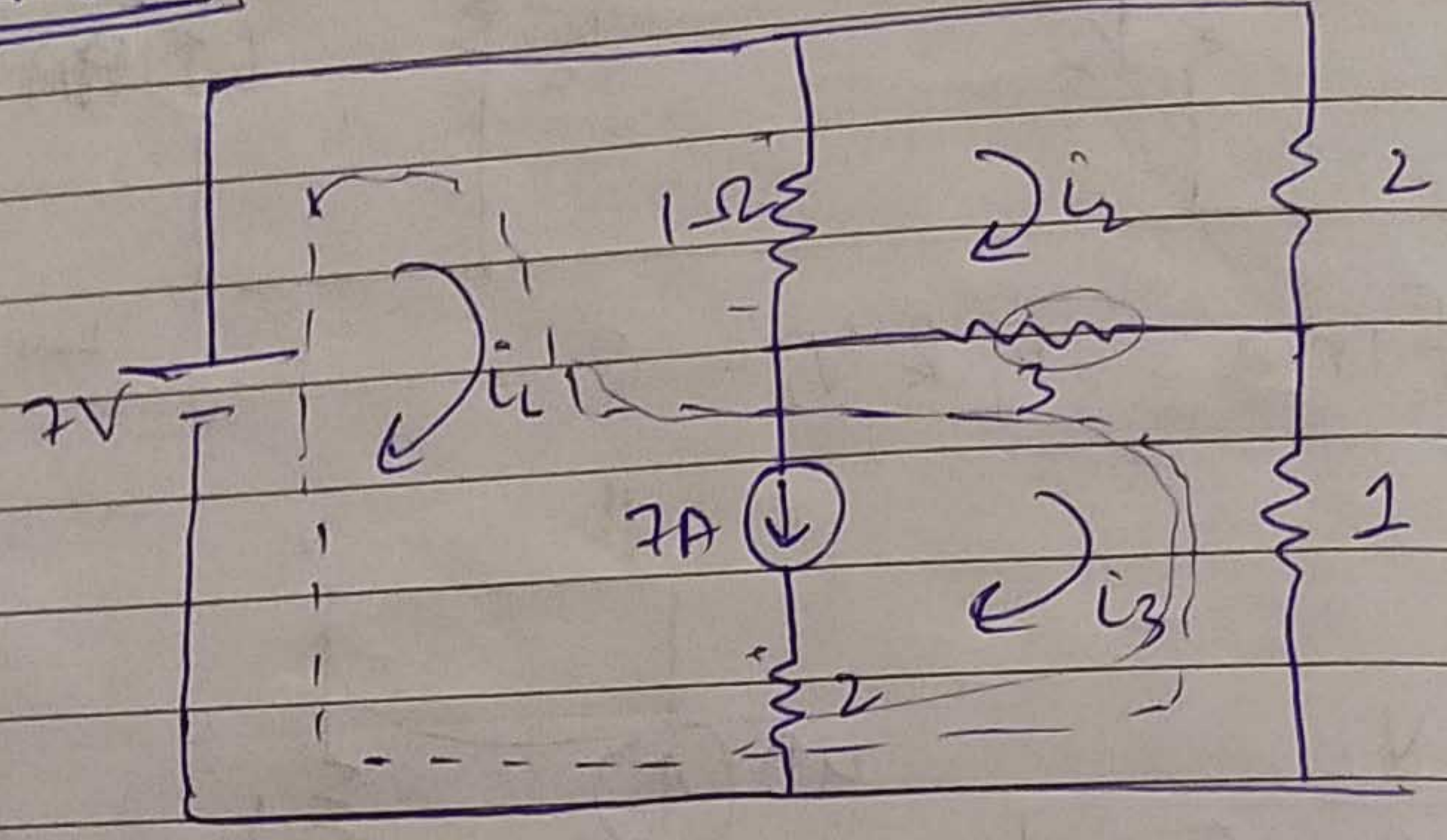


$$7 = (i_1 - i_2) + 3(i_3 - i_2) + i_3$$

$$i_1 - i_3 = 7A$$

$$2i_2 + 3(i_2 - i_3) + (i_2 - i_1) = 0$$

Eg:-

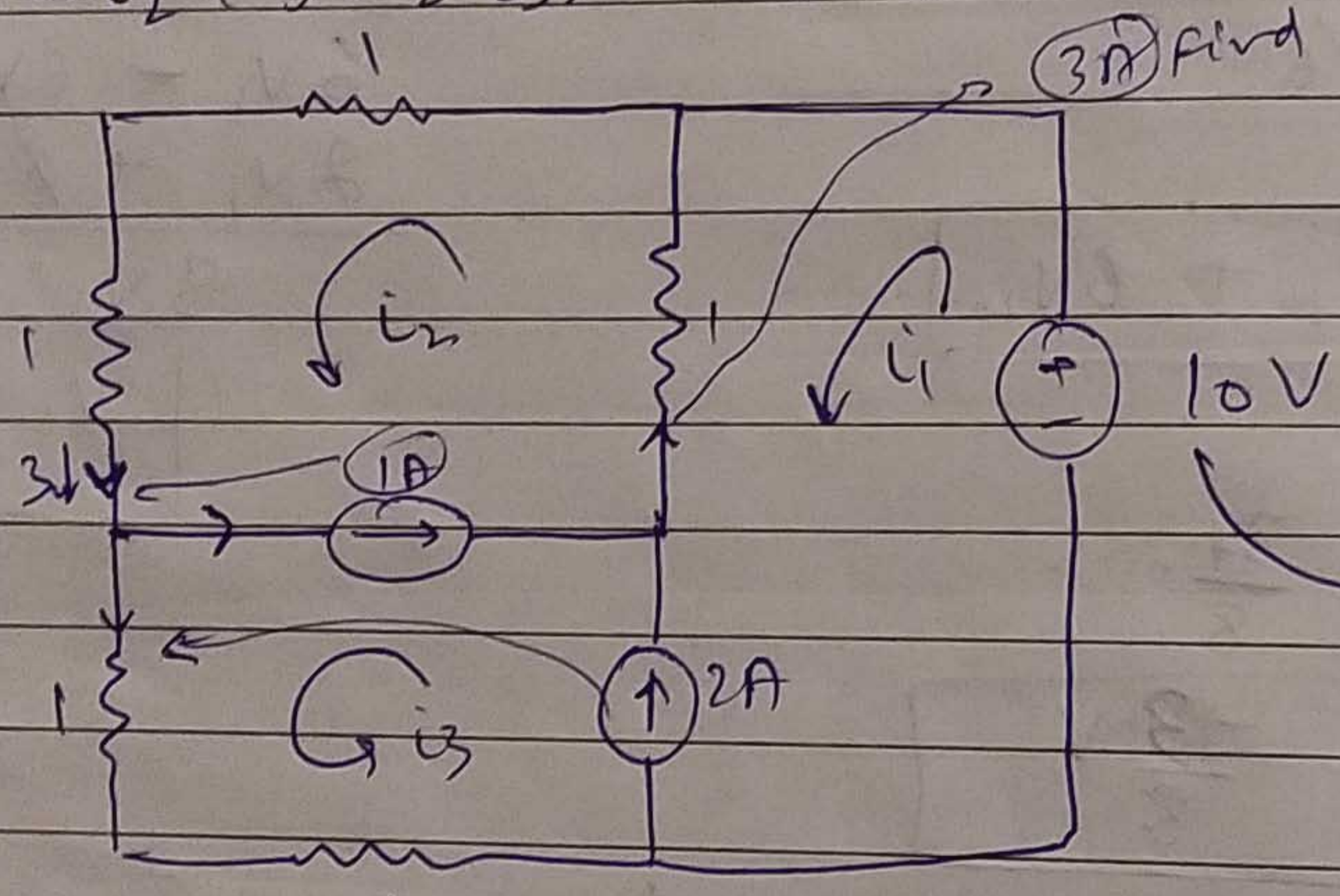


Find Power?

Wye - Delta


# Star - Delta Connection:

↑  
connection

Star form

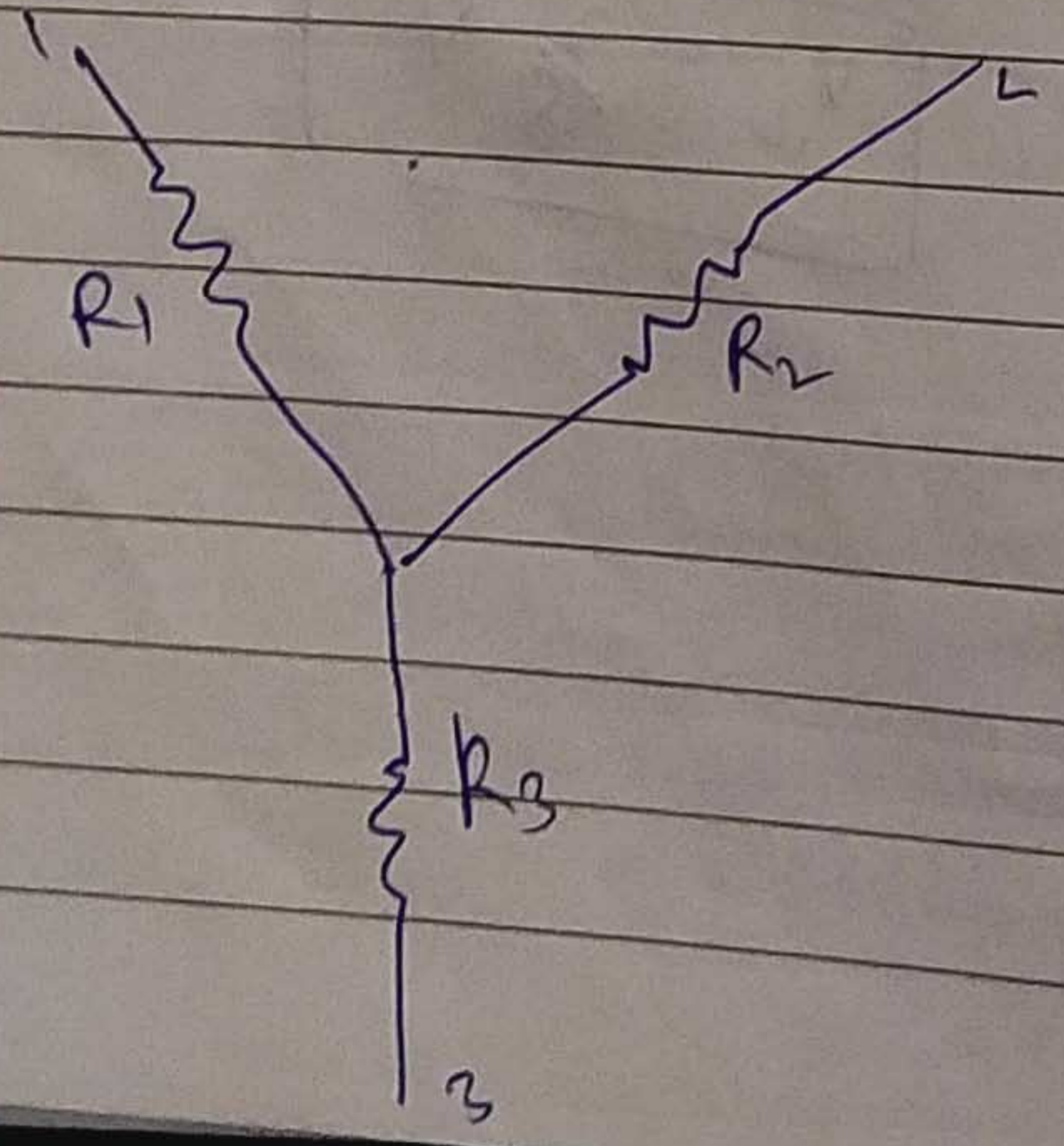

delta form

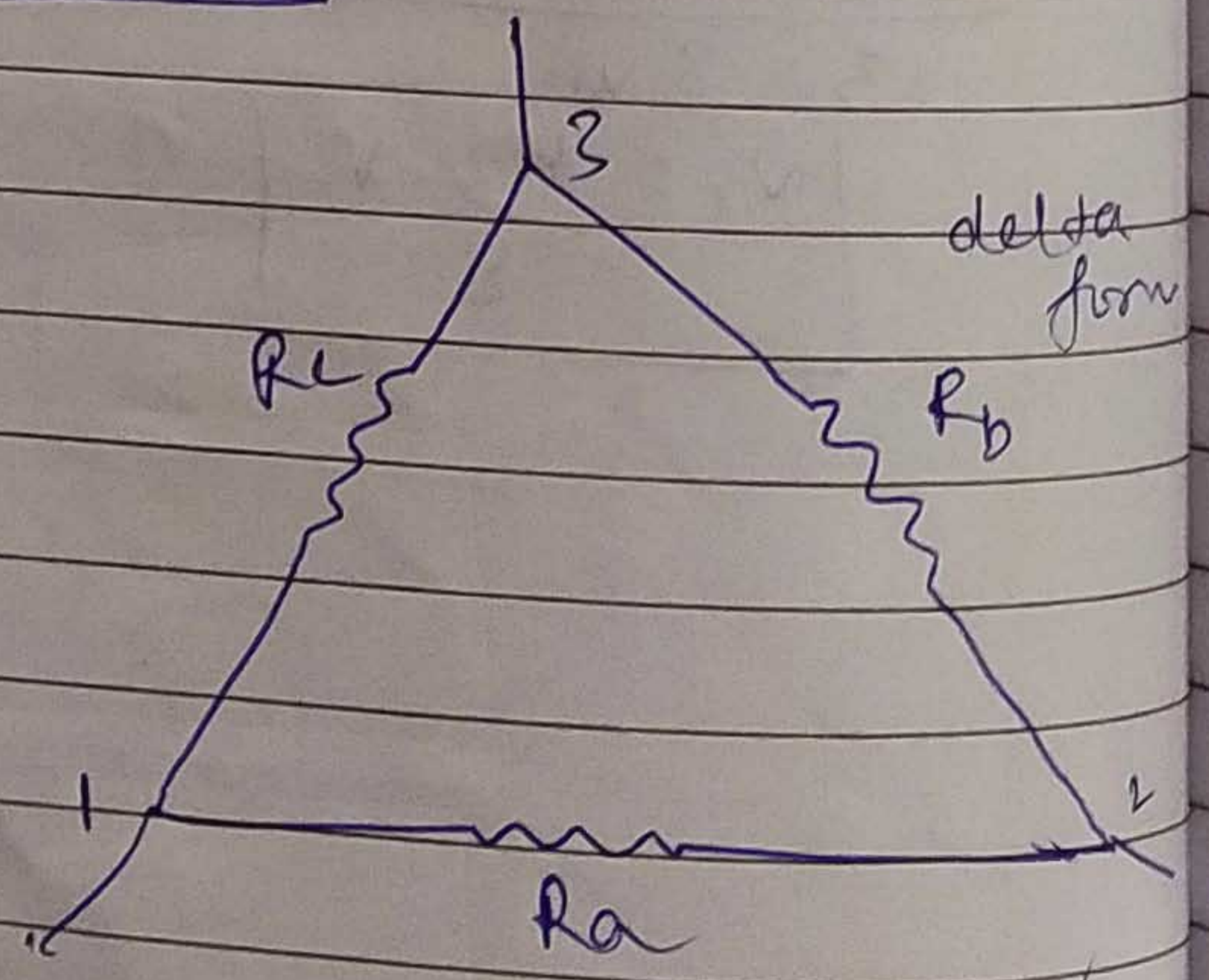

Δ/x connection

$$R_{12}(Y) = R_1 + R_2 \Rightarrow (R_c + R_b) \parallel R_a$$

$$R_1 + R_2 = \frac{(R_c + R_b) R_a}{R_a + R_b + R_c} \quad - \textcircled{1}$$

$$R_{23}(Y) = R_2 + R_3 \Rightarrow \frac{(R_a + R_c) R_b}{R_a + R_b + R_c} \quad - \textcircled{2}$$

$$R_{31}(Y) = R_3 + R_1 \Rightarrow \frac{(R_a + R_b) R_c}{R_a + R_b + R_c} \quad - \textcircled{3}$$

Subtract  $\textcircled{2}$  from  $\textcircled{1}$ ;

$$R_1 - R_3 = \frac{R_a R_c + R_a R_b}{R_a + R_b + R_c} - \frac{R_a R_b - R_b R_c}{R_a + R_b + R_c}$$

$$R_1 - R_3 = \frac{R_a R_c - R_b R_c}{R_a + R_b + R_c} \quad - \textcircled{4}$$


Add  $\textcircled{3}$  &  $\textcircled{4}$ ;

$$2R_1 = \frac{2R_a R_c}{R_a + R_b + R_c}$$

$$R_1 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_b}{R_a + R_b + R_c}$$
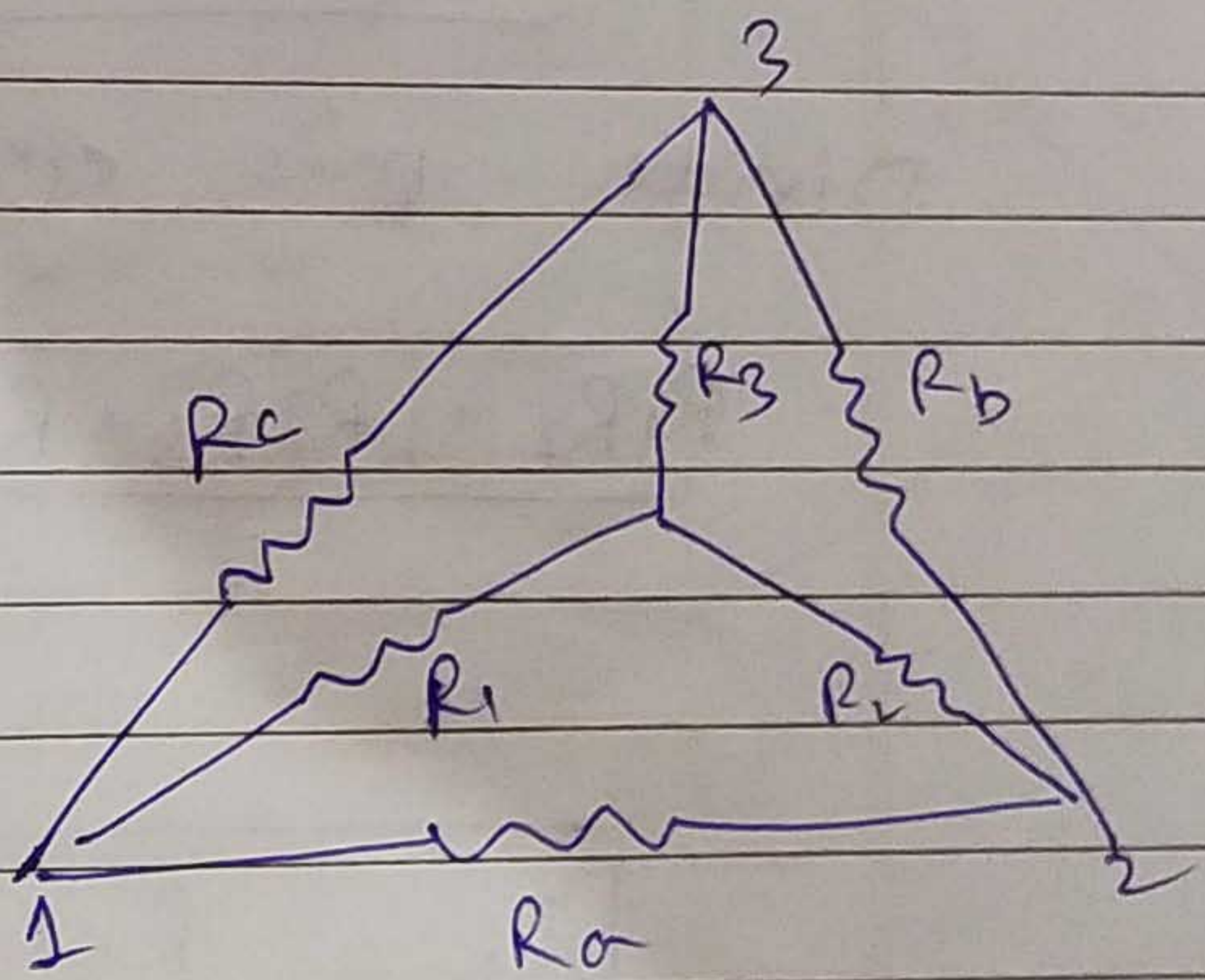
$$R_3 = \frac{R_b R_c}{R_a + R_b + R_c}$$



Now start to delta;

$$R_1 R_2 = \frac{R_a^2 R_b R_c}{(R_a + R_b + R_c)^2} \quad \text{--- (a)}$$

$$R_2 R_3 = \frac{R_b^2 R_a R_c}{(R_a + R_b + R_c)^2} \quad \text{--- (b)}$$

$$R_1 R_3 = \frac{R_c^2 R_a R_b}{(R_a + R_b + R_c)^2} \quad \text{--- (c)}$$

Add (a), (b) & (c);

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_a^2 R_b R_c + R_b^2 R_a R_c + R_c^2 R_a R_b}{(R_a + R_b + R_c)^2}$$

$$= \frac{(R_a R_b R_c) (\cancel{R_a + R_b + R_c})}{(R_a + R_b + R_c)^2}$$

$$\boxed{R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_a R_b R_c}{(R_a + R_b + R_c)}}$$

Divide this eqn. by  $R_1$

$$\frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{R_a R_b R_c}{(R_a + R_b + R_c) R_1}$$



$$\boxed{R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}}$$

$$\boxed{R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

\*  $R_0, R_1, R_2, R_3$  eliminate  
Date: / /  
Page: /  
 $R_1, R_2, R_3$

Ques

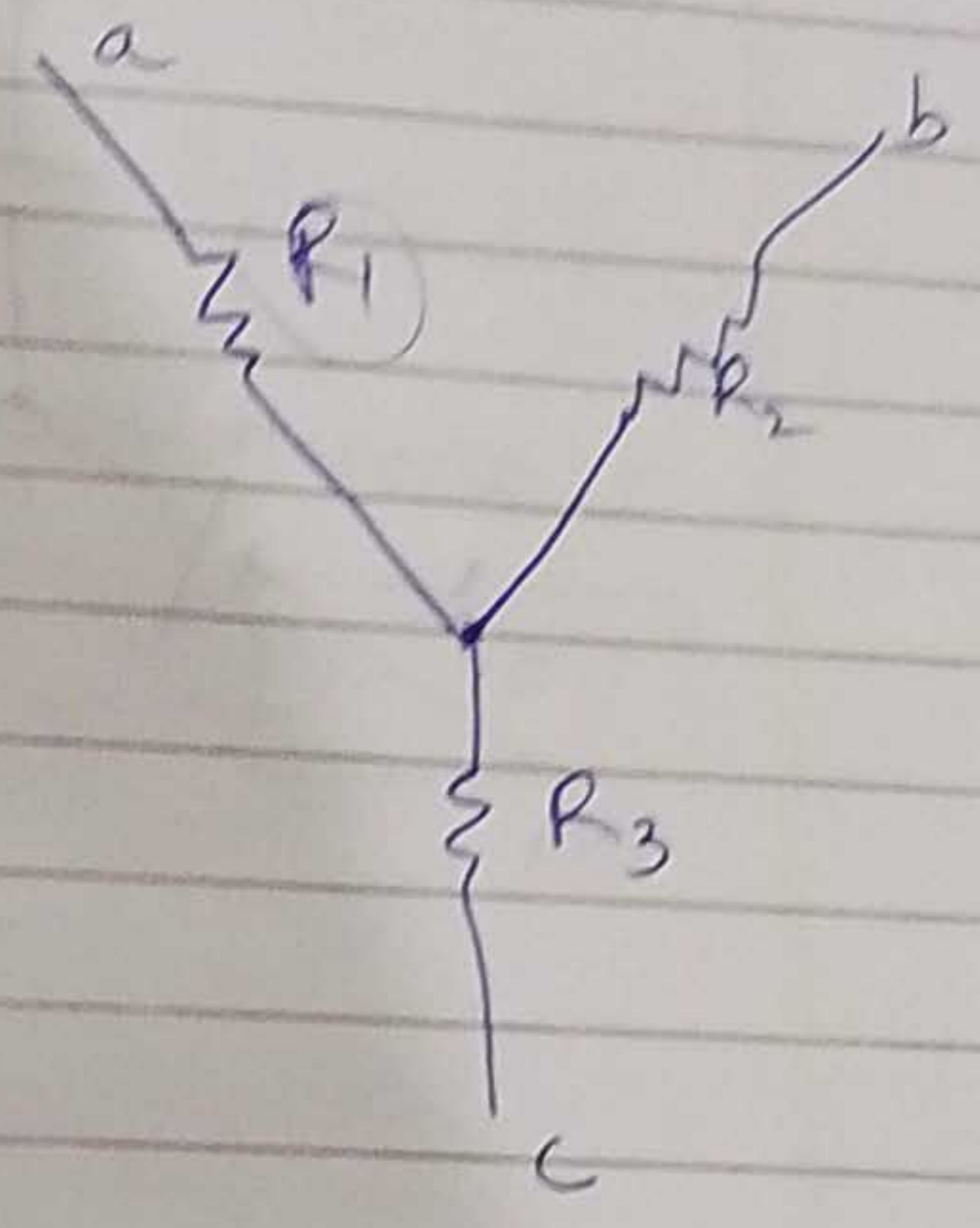
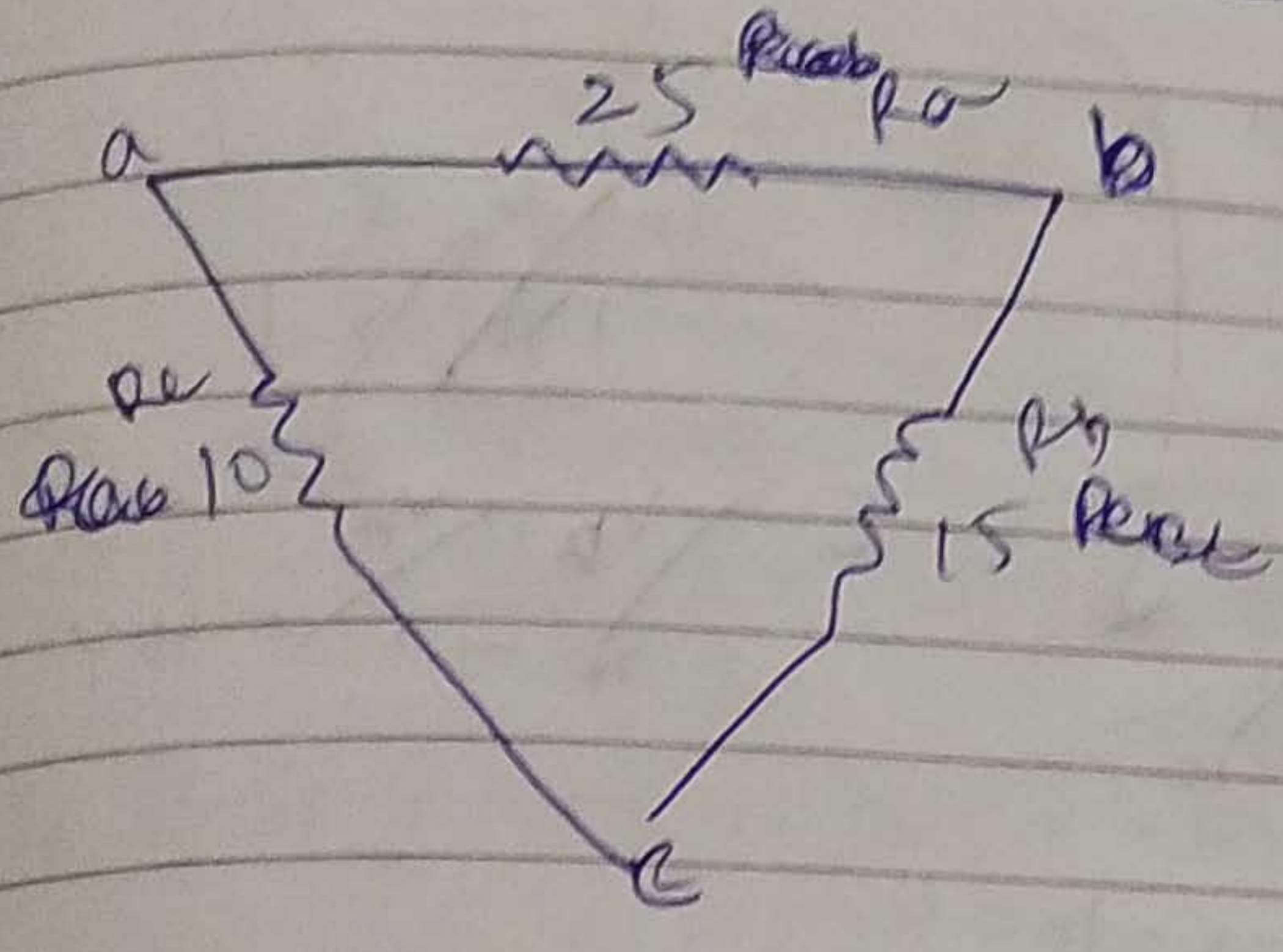


$$R_1 = \frac{10 \times 15}{50} = 3$$

$$R_2 = \frac{15 \times 25}{50} = \frac{375}{50} = 7.5 \Rightarrow \left(\frac{15}{2}\right)$$

$$R_3 = \frac{10 \times 15}{50}$$

Ques

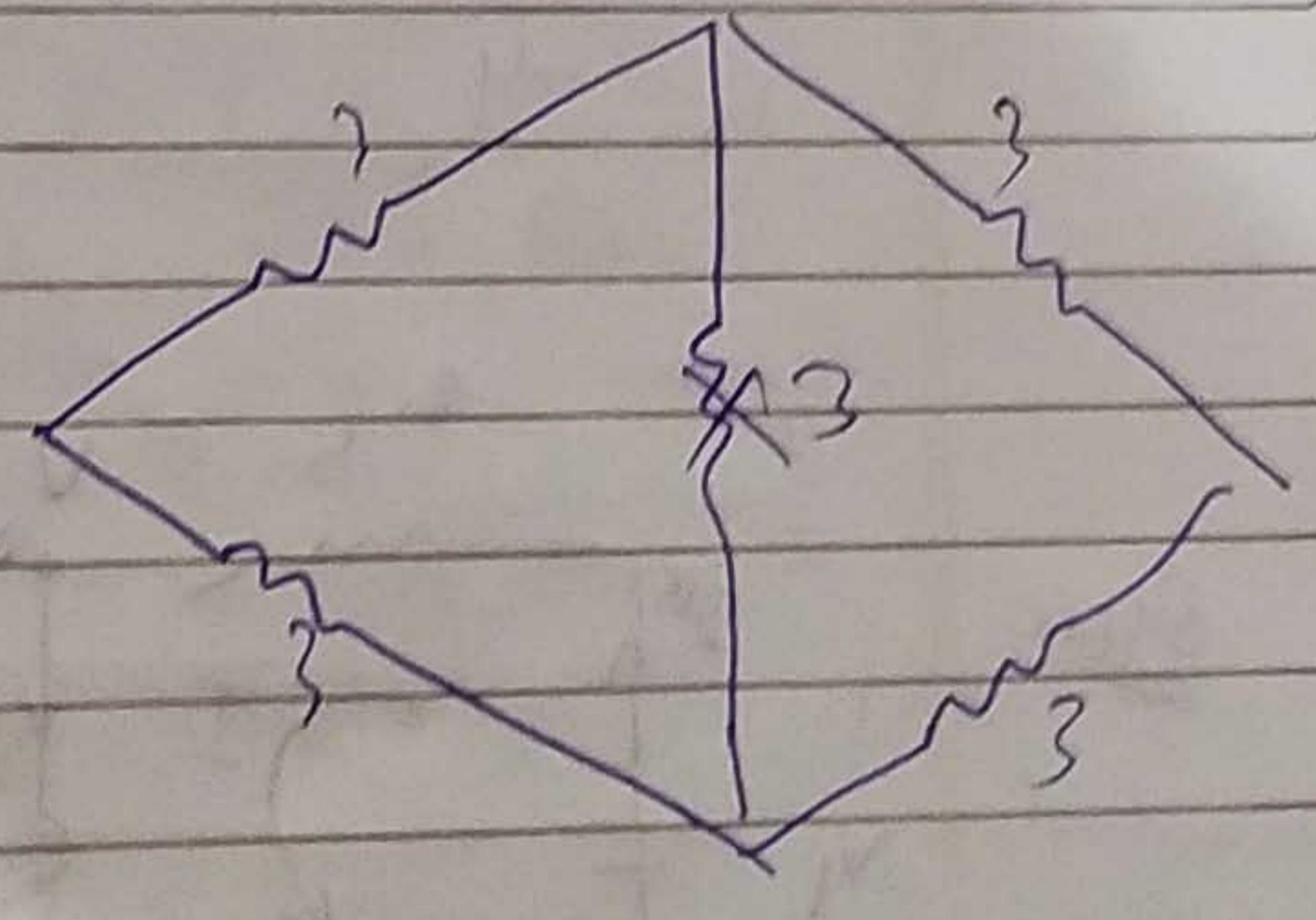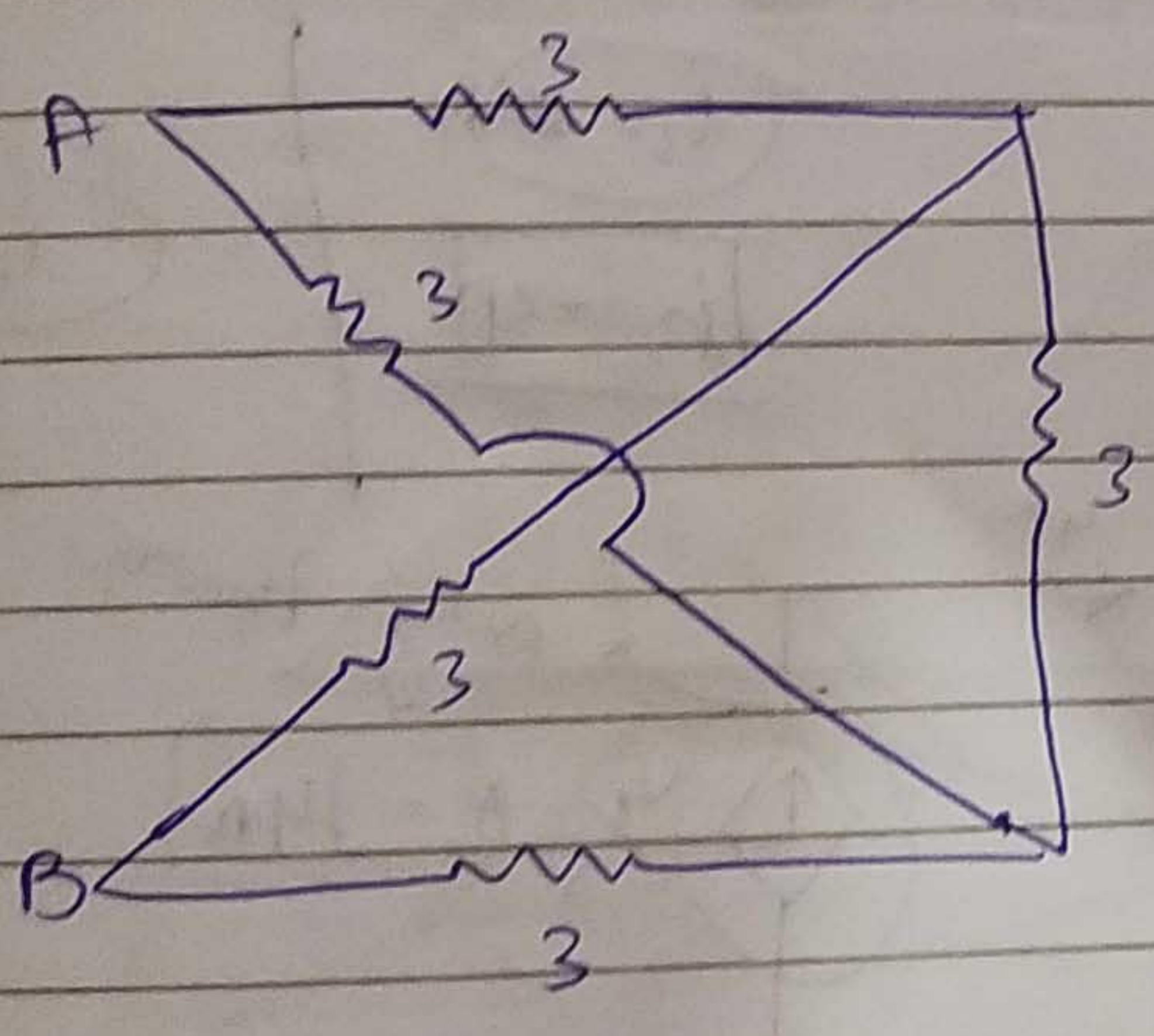

$$\frac{36}{12} = 3$$

$$\frac{6 \times 6}{12}$$



$R_{eq} = 10 \Omega$

$I_{net} = \frac{V_1}{R_{eq}} = \frac{20}{10} = 2A$

$P_{R_1} = I^2 R = (2)^2 \cdot 5 = 20W$

$P_{R_2} = I^2 R = (2)^2 \cdot 5 = 20W$

$P_{V_1} = VI = 20 \times 2 = 40W$

$\frac{V}{5} + \frac{V-V_1}{5} = \frac{V_1}{5}$

$\frac{2V}{5} = \frac{2V_1}{5}$

$V = V_1$

$V_1 = 20V$

KVL at a:


$\frac{V}{5} + \frac{V-V_1}{5} = \frac{V_1}{5}$

$\frac{V}{5} + V = \frac{2V_1}{5}$

$\frac{6V}{5} = \frac{2V_1}{5}$

$V = \frac{V_1}{3} = \frac{20}{3} = 6.67V$

Quest

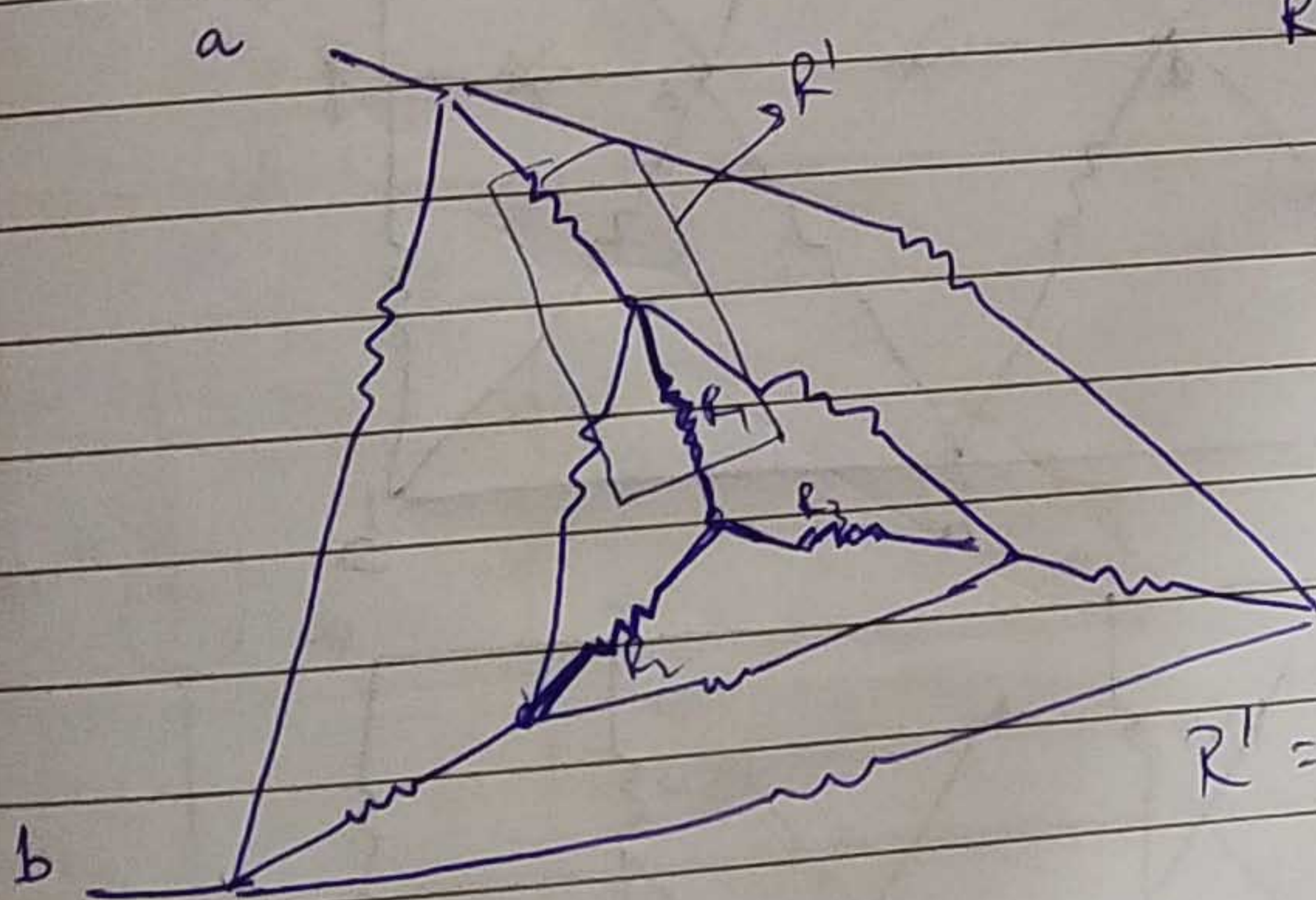

$R = 1 \Omega$

Find  $R_{ab}$ ?


$R_1 = \frac{1 \times 1}{3} = \frac{1}{3}$

$R_2 = \frac{1}{3} \quad | \quad R_3 = \frac{1}{3}$

$R' = 1 + \frac{1}{3} = \frac{4}{3} \Omega$



$R_a = \left( \frac{4}{3} \times \frac{4}{3} \right)^3 \Rightarrow \frac{16 \times 8}{81} = \frac{128}{81}$

$R_b = 4 \quad | \quad R_c = 4$

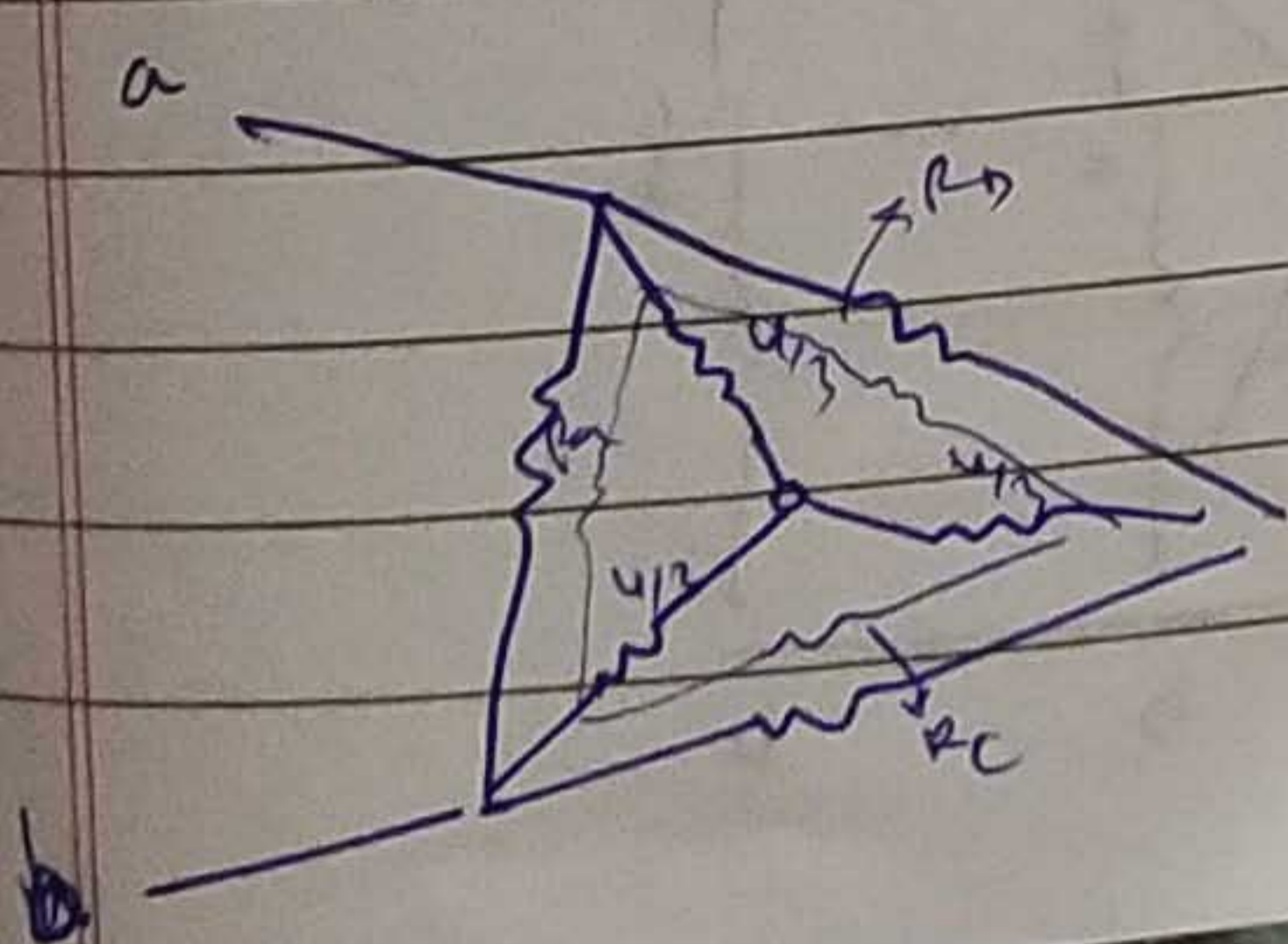


dent
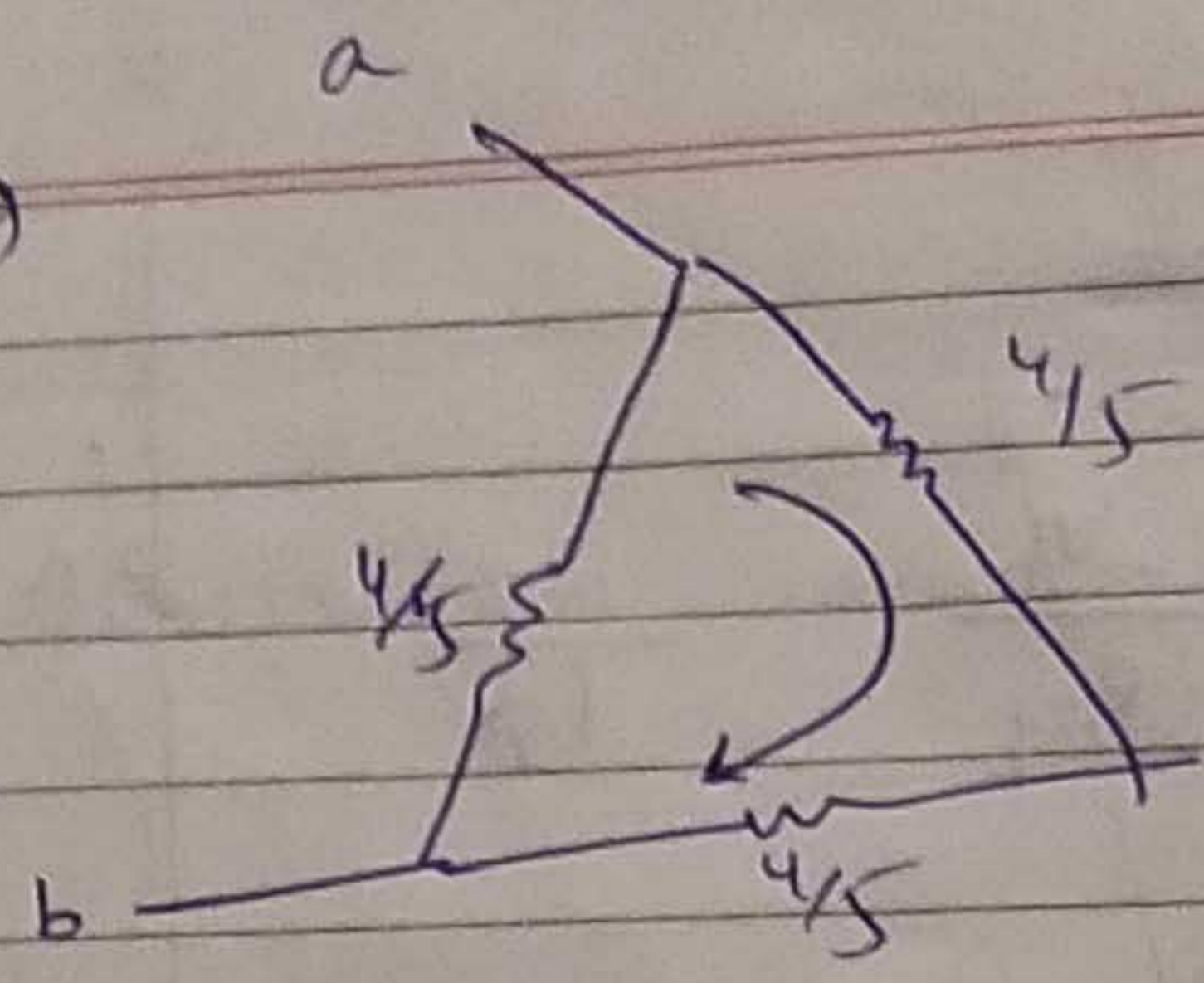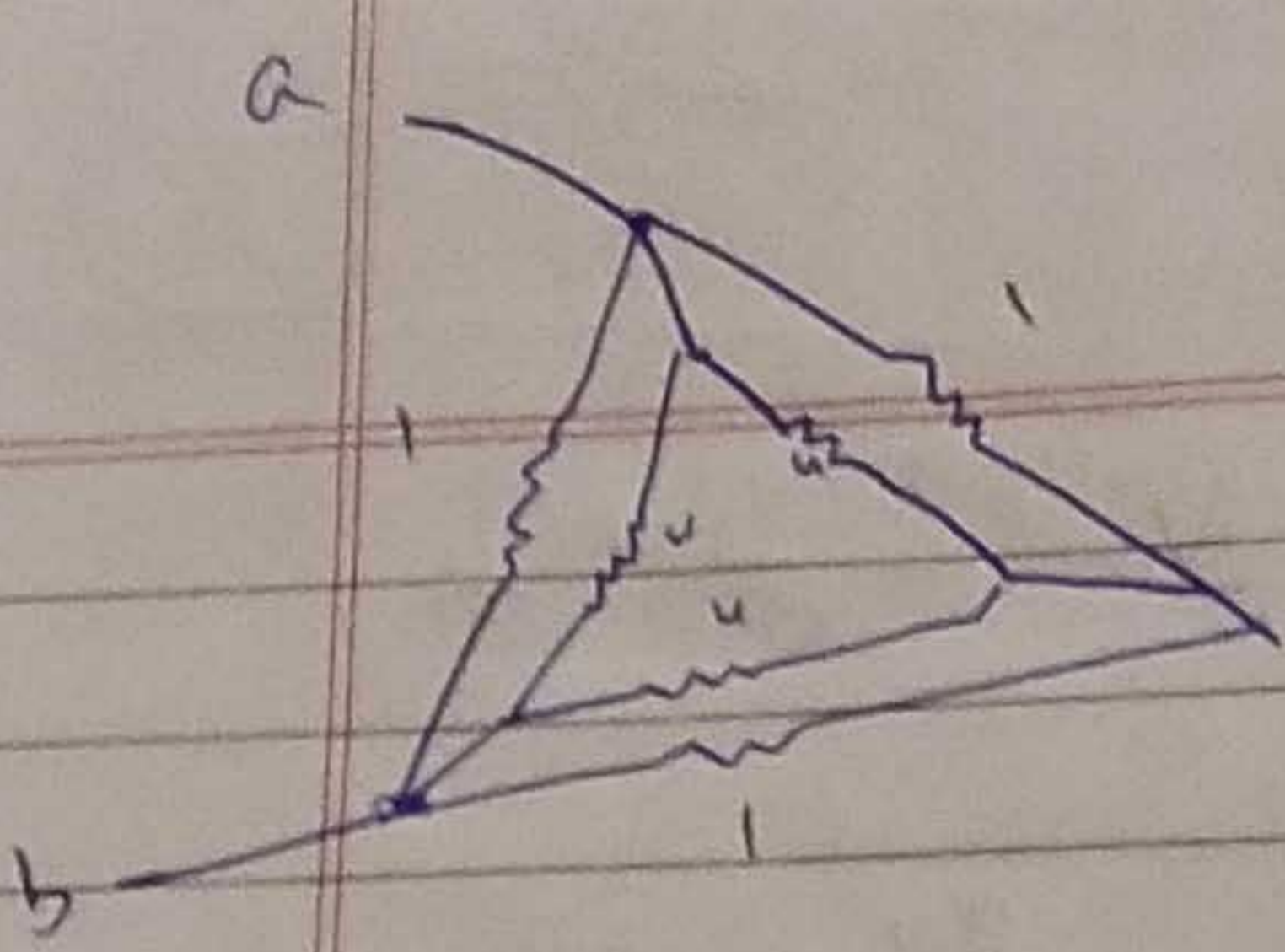
$$\frac{1 \times 4}{5} = \frac{4}{5} \Omega$$



$$\frac{4}{5} + \frac{4}{5}$$

$$\frac{8}{5}$$

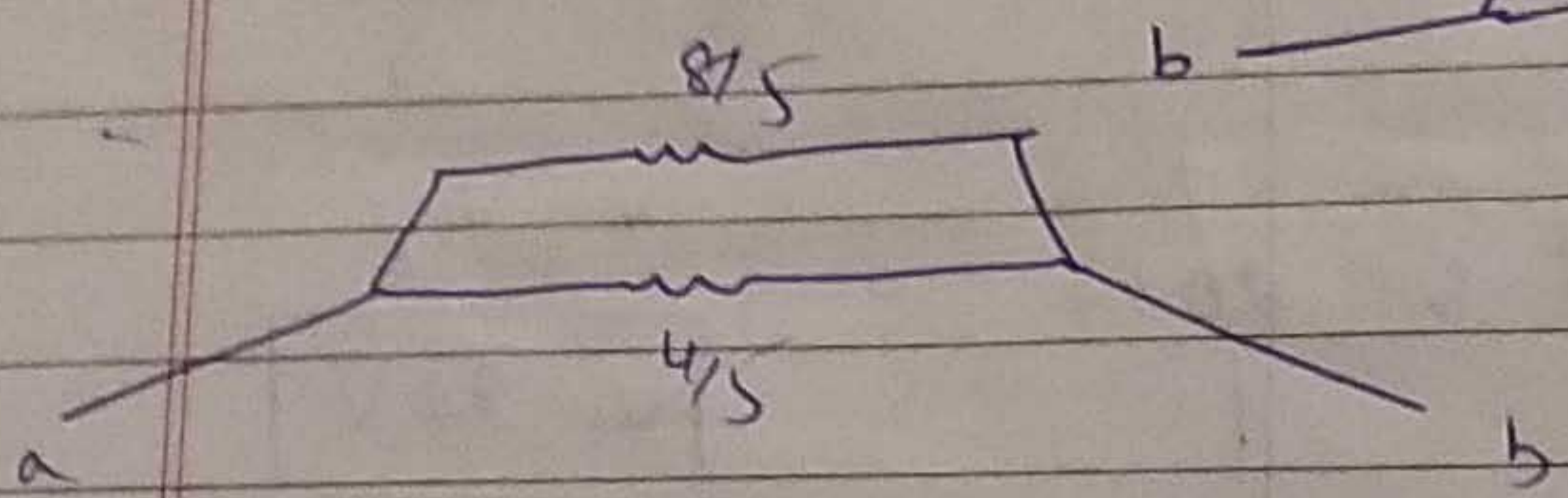

$$\frac{\frac{8}{5} \times \frac{4}{5}}{\frac{8}{5} + \frac{4}{5}}$$

$$\frac{\frac{32}{25}}{\frac{12}{5}}$$

$$\frac{32}{25} \times \frac{5}{12}$$

$$\Rightarrow \frac{32}{25} \times \frac{5}{12}$$

$$\Rightarrow \frac{32}{15} \times 12$$

$$\Rightarrow \frac{8}{15} \Omega$$

Ques:-  
R=30Ω  
Rab=?

$$\frac{50 \times 100}{200}$$

