


# Module - II

- Harmonics & Harmonic Filters
- HVDC Light/Plus
- Multi-Terminal HVDC Systems (MTDCs)

## Harmonic Analysis: Sources of Harmonics:

i) Generators: Due to non-uniform field windings  $\rightarrow$  Harmonics in generated voltage  $\rightarrow$  Smaller in amplitude & hence negligible

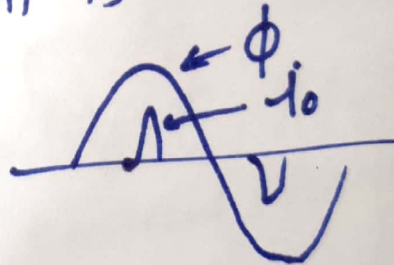ii) Converter Transformers: For sinusoidal flux, The excitation current is non-sinusoidal.  $I_0 \downarrow \downarrow \rightarrow$  negligible



iii) Converters:  $\alpha$

$I_s \rightarrow$  distorted


Characteristic harmonics,  $h = np \pm 1$   
 $n = 1, 2, 3, \dots$

Uncharacteristic harmonics  $p = 6, 12$


Causes: - Valves are not fixed at equal

$60^\circ$  intervals due to unbalanced

3- $\phi$  source.

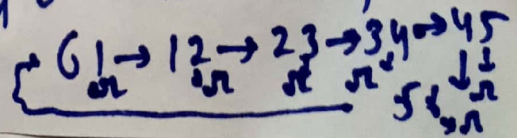

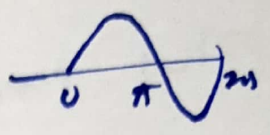- Due to jitter in electronic circuitry (Shift in ZC instants);
- Saturation of converters  
Xmers;
- Interaction of harmonics with ~~can~~ fundamental component in ~~the~~ non-linear elements of power system,
- Some control actions like CEA control
- Don't need separate filters for uncharacteristic harmonics



Effect of Harmonics:

- i) Ineffective operation of converter & sometimes instability of CC control
- ii) Maloperation of critical/sensitive equipments
- iii) Additional losses in AC motors
- iv) False tripping of relays
- v) EM Interference with nearby telephone lines
- vi) Shifting of ZCs;
- vii) OVs due to harmonic resonances
- viii) Blowing of fuses




$$\% \text{ THD} = \frac{\sqrt{I_s^2 - I_{s1}^2}}{I_{s1}} \times 100 \quad (3)$$

Variation of Harmonic current w.r.t  $\alpha$  and  $u$ :

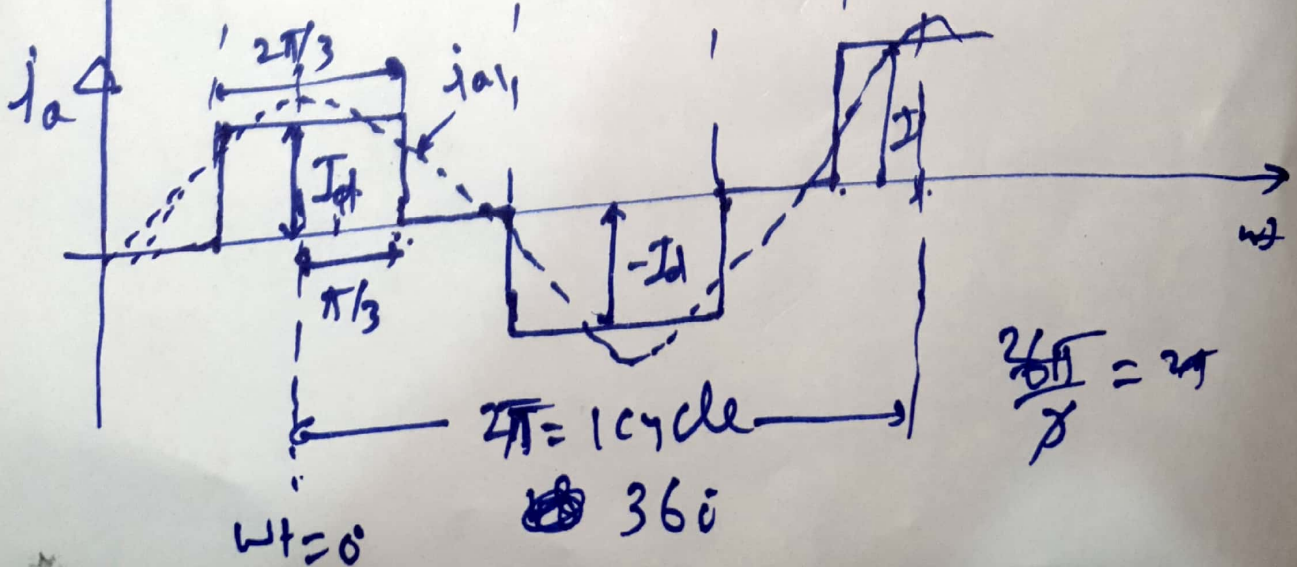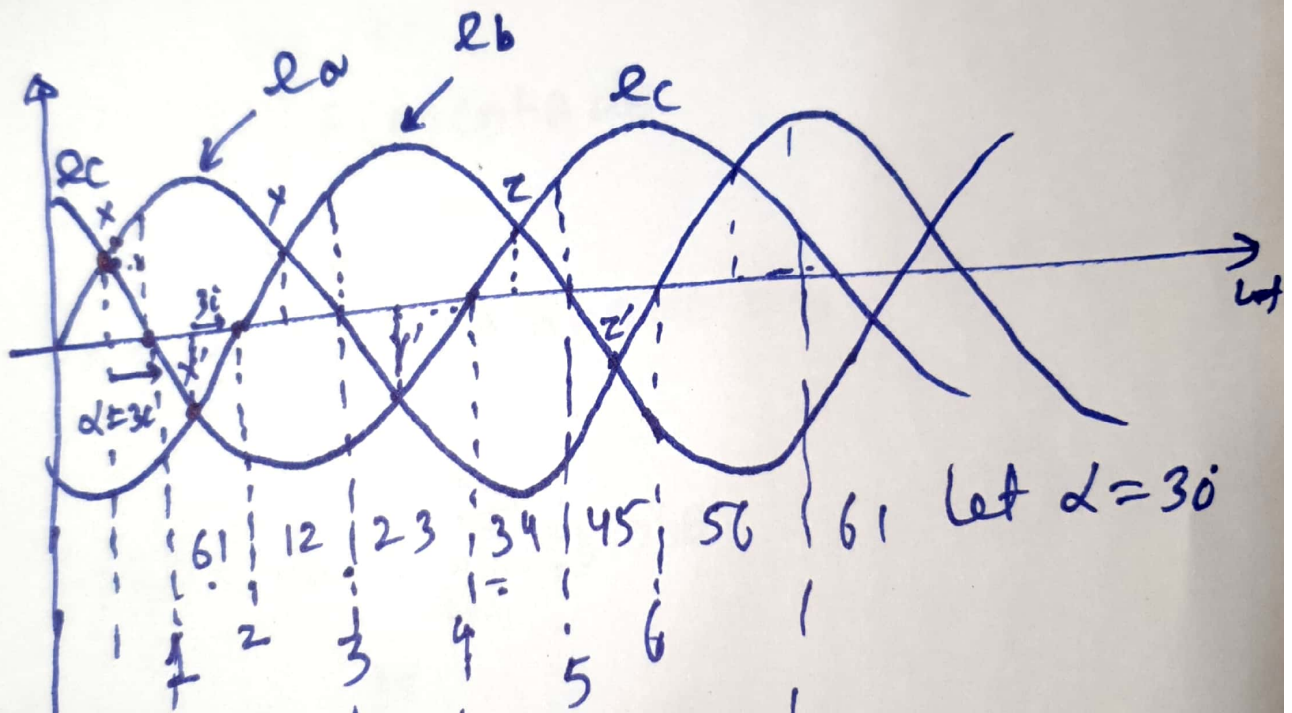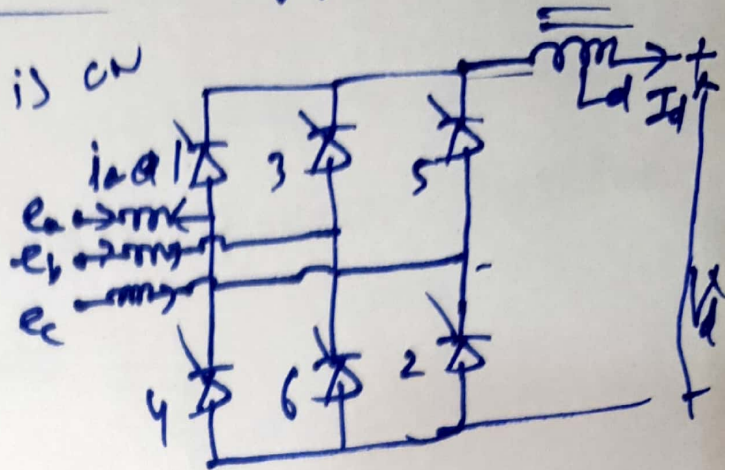- i) For  $u=0$ ; as  $\alpha \uparrow$ , Harmonics  $\uparrow$
  - ii) Magnitude of harmonics  $\downarrow$  as  $u \uparrow$ .
  - iii) Each harmonic decreases upto a certain limit at an angle of  $u = \frac{2\pi}{h}$  beyond which harmonics  $\uparrow$  slowly.
- For  $u > \frac{2\pi}{h}$ , harmonics  $\uparrow$  with  $u \uparrow$

Mathematic Expression for source or line current drawn by a converter: (4)

$i_a = +I_d$  when 1 is on  
 $i_a = -I_d$  if 4 is on



By Fourier Analysis,

$$F(\theta) = \frac{A_0}{2} + \sum_{h=1}^{\infty} (A_h \cos h\theta + B_h \sin h\theta)$$

where  $A_0$  is DC component of current and  $A_h$  and  $B_h$  are Fourier coefficients.

$$A_0 = \frac{1}{\pi} \int_0^{2\pi} F(\theta) d\theta = 0$$

$$A_h = \frac{1}{\pi} \int_0^{2\pi} F(\theta) \cos h\theta d\theta$$

$$B_h = \frac{1}{\pi} \int_0^{2\pi} F(\theta) \sin h\theta d\theta = 0$$

$$\therefore F(\theta) = i_a = \sum_{h=1}^{\infty} \underline{A_h} \cos h\theta \quad \text{--- (1)}$$

Now,  $A_h = \frac{1}{\pi} \int_0^{2\pi} F(\theta) \cos h\theta d\theta$

$$A_h = \frac{1}{\pi} \left\{ \int_0^{\pi/3} I_d \cos h\theta d\theta + \int_{2\pi/3}^{2\pi/3} 0 d\theta + \int_{4\pi/3}^{4\pi/3} -I_d \cos h\theta d\theta \right. \\ \left. + \int_{5\pi/3}^{5\pi/3} 0 d\theta + \int_{2\pi}^{2\pi} I_d \cos h\theta d\theta \right\}$$

$$A_h = \frac{I_d}{\pi h} \left\{ \left| \sinh \theta \right|_0^{\pi/3} + \left| -\sinh \theta \right|_{2\pi/3}^{4\pi/3} + \left| \sinh \theta \right|_{5\pi/3}^{2\pi} \right\} \quad (6)$$

$$A_h = \frac{I_d}{\pi h} \left[ \sinh \frac{\pi}{3} - \sinh \frac{4\pi}{3} + \sinh \frac{2\pi}{3} + \sinh 2\pi - \sinh \frac{5\pi}{3} \right]$$

For  $h=1$  (fundamental),

$$A_1 = \frac{I_d}{\pi} \left( \sin \frac{\pi}{3} - \sin \frac{4\pi}{3} + \sin \frac{2\pi}{3} + \sin 2\pi - \sin \frac{5\pi}{3} \right)$$

$$= \frac{I_d}{\pi} \left[ \frac{\sqrt{3}}{2} + \frac{\sqrt{3}}{2} + \frac{\sqrt{3}}{2} + \frac{\sqrt{3}}{2} \right]$$

$$= \frac{24\sqrt{3}}{2\pi} I_d$$

$$\Rightarrow A_1 = \frac{2\sqrt{3}}{\pi} I_d = I_{1m} \quad - \quad (2)$$

~~For  $h=2$~~ , For  $h=3$ ,

$$A_3 = \frac{I_d}{3\pi} \left[ \sin \frac{3\pi}{3} - \sin \frac{4\pi}{3} + \sin \frac{2\pi}{3} + \sin 3 \times 2\pi - \sin 3 \times \frac{5\pi}{3} \right]$$

$$A_3 = \frac{I_d}{3\pi} \left[ \sin_0 \pi - \sin_0 4\pi + \sin_0 2\pi + \sin_0 6\pi - \sin_0 5\pi \right]$$

$\therefore A_3 = 0$  — (3)


for  $h=5$ . (5th harmonic component),

$$A_5 = \frac{I_d}{5\pi} \left[ \sin \frac{5\pi}{3} - \sin \frac{20\pi}{3} + \sin \frac{10\pi}{3} + \sin_0 10\pi - \sin \frac{25\pi}{3} \right]$$

$$A_5 = \frac{I_d}{5\pi} \left[ -\frac{\sqrt{3}}{2} - \frac{\sqrt{3}}{2} - \frac{\sqrt{3}}{2} - \frac{\sqrt{3}}{2} \right]$$

$$A_5 = -\frac{2\sqrt{3}}{5\pi} I_d = -\frac{I_{1m}}{5}$$
 — (4)
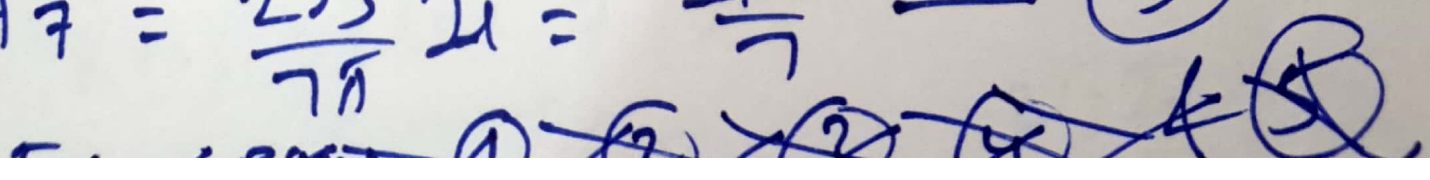
$$A_7 = \frac{2\sqrt{3}}{7\pi} I_d = \frac{I_{1m}}{7}$$
 — (5)



∴ From eqn. ①,  $i_a = \sum_{h=1}^{\infty} A_h \cos h\theta$

$$i_a = \frac{2\sqrt{3}I_d}{\pi} \left[ \cos\theta - \frac{1}{5} \cos 5\theta + \frac{1}{7} \cos 7\theta - \frac{1}{11} \cos 11\theta + \frac{1}{13} \cos 13\theta \dots \right]$$

$$i_a = A_1 \cos\theta + A_3 \cos 3\theta + A_5 \cos 5\theta + A_7 \cos 7\theta + A_9 \cos 9\theta + A_{11} \cos 11\theta + A_{13} \cos 13\theta \dots$$

Fund. comp. of currents,

$$i_{a1} = \frac{2\sqrt{3}I_d}{\pi} \cos\theta = I_{a \max.} \cos\theta$$

Peak value of fund. comp. of current,

$$I_{a \max.} = \frac{2\sqrt{3}I_d}{\pi}$$

RMS value of fund. comp. of source current,

$$I_{a1} = \frac{I_{a \max.}}{\sqrt{2}} = \frac{2\sqrt{3}I_d}{\pi \sqrt{2}} \times \frac{\sqrt{2}}{\sqrt{2}} = \frac{2\sqrt{6}I_d}{2\pi} = \boxed{\frac{\sqrt{6}}{\pi} I_d}$$

∴ For Y-Y system,



$$i_a = \frac{2\sqrt{3} I_d}{\pi} \left[ \cos \theta \frac{1}{5} \cos 5\theta + \frac{1}{7} \cos 7\theta + \frac{1}{11} \cos 11\theta + \frac{1}{13} \cos 13\theta \dots \right]$$

For Y-Δ connected system,

$$i_a = \frac{2\sqrt{3} I_d}{\pi} \left[ \cos \theta + \frac{1}{5} \cos 5\theta - \frac{1}{7} \cos 7\theta + \frac{1}{11} \cos 11\theta + \frac{1}{13} \cos 13\theta \dots \right]$$


∴ For a 12-pulse converter,
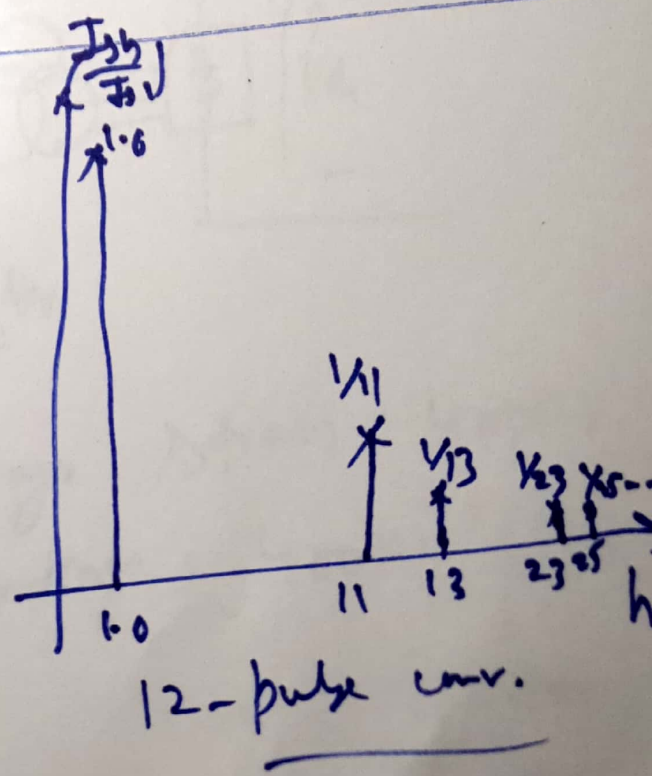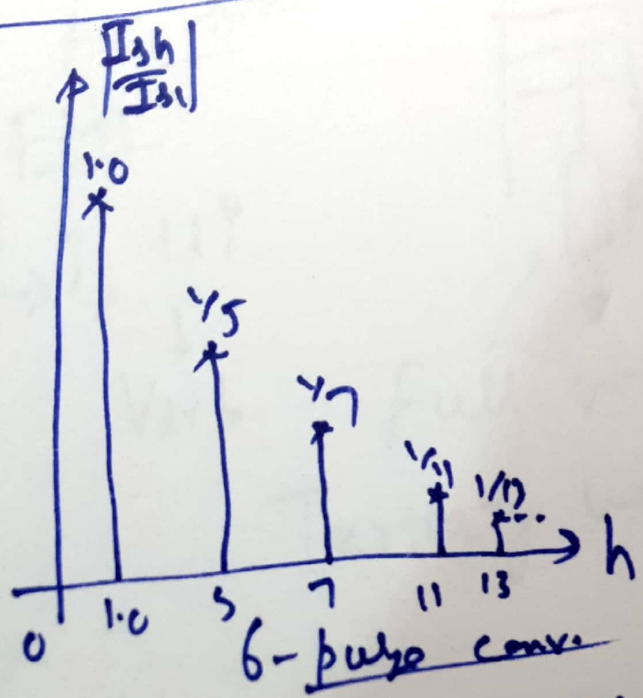
$$i_a = \frac{2\sqrt{3} I_d}{\pi} \left[ \cos \theta - \frac{1}{11} \cos 11\theta + \frac{1}{13} \cos 13\theta \dots \right]$$



Harmonic Filters: Purpose:

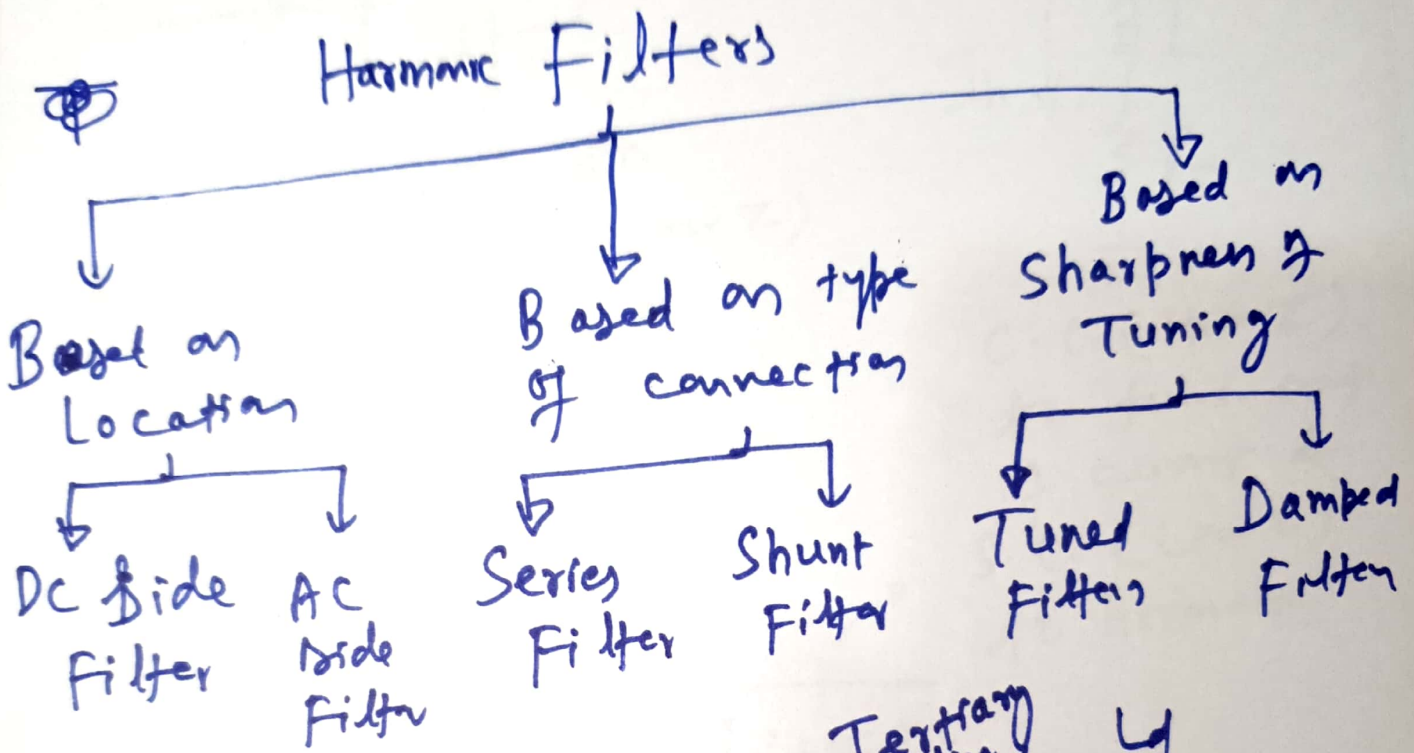
- i) To suppress harmonic currents
- ii) To provide some reactive power support



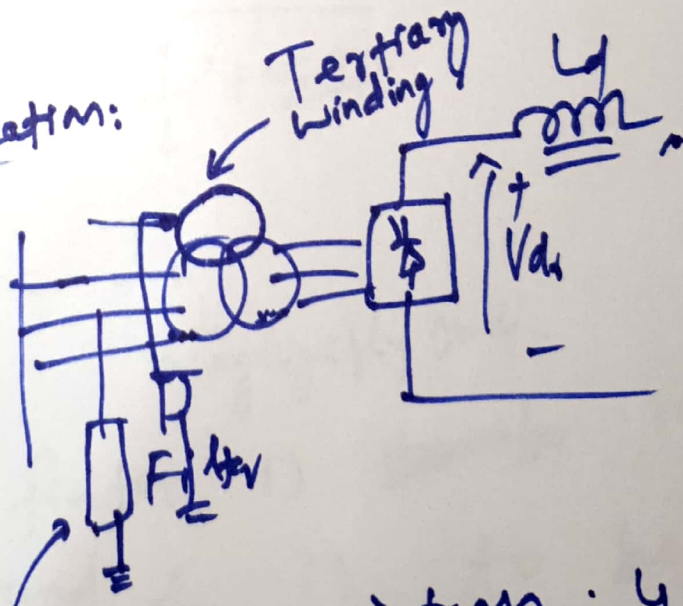a) Based on Location:

AC side Filter

$Z_s \uparrow, U_f \downarrow$   
 $V_{drb}$




Full voltage stress : 400KV

Tertiary windings : 400KV/66KV  
 ↓  
 Filter


b) Based on type of connection:

connection: (11)

i) Series Filter:

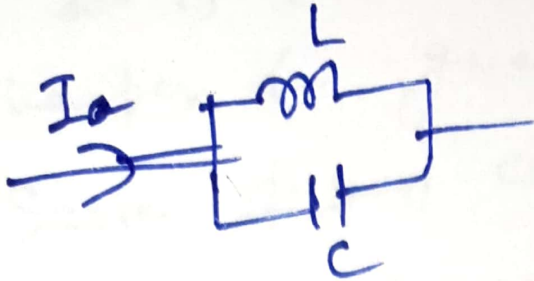

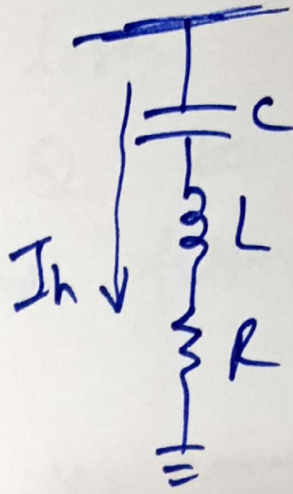O.C. (High Z) to harmonics & S.C. (Low Z) to fund. comp. of line current



O.C. (High Z) to fund. comp. of current & S.C. (Low Z) to harmonics

$$I_{\text{filter}} = \sqrt{I_1^2 + \sum I_h^2}$$

$$I_{\text{filter}} = I_h \text{ Negligibly small.}$$

Comparison:

- Series filter i) ~~to be~~ resting on ground & ii) to be insulated properly
- Series filter carries full line current  $\rightarrow$  higher cost  $\rightarrow$  bulky & more losses

On the other hand, Shunt filter has to carry smaller harmonic currents & ~~is~~ hence smaller in size, cheaper & gives low losses

- Series filters consume  $Q$  ~~to~~ as  $I^2X$  whereas shunt filters generate  $Q$ .

- Shunt filters can be  $Y$ -connected or  $\Delta$ -connected (Generally  $Y$ -connected) whereas series filters are phase filters.

c) Based on Sharpness of Tuning:

i) Tuned filters & ii) Damped filters

i) Tuned filters: a) Single-tuned filter  
b) Double-tuned filter

ii) Damped filters: charact:

- Low  $Q$  - Sharp tuning is not required
- can tolerate large steady-state variation in frequency

- Low transient voltages due to high R

- Low power loss due to C



(C-type H.P.F.)

$|Z|$  vs frequency



Type 7 filter

Circuit


Single-tuned Filter

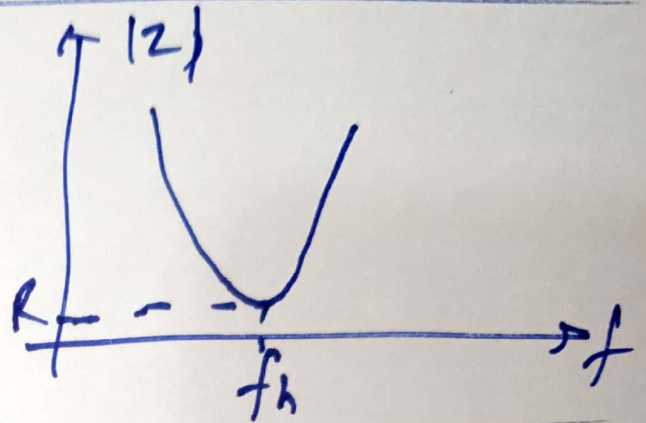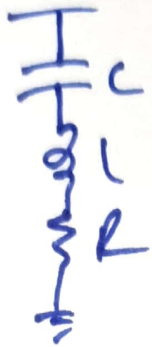

Double-tuned filter

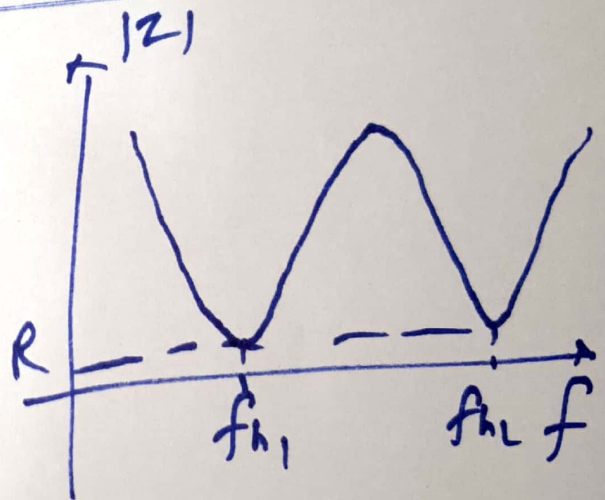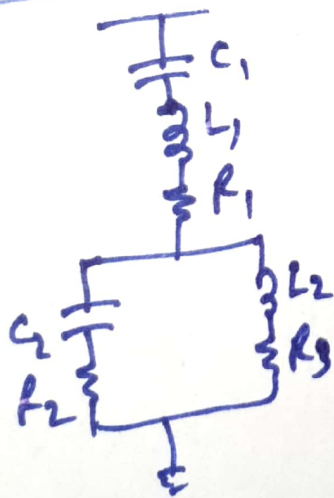

Second-order H.P.F.

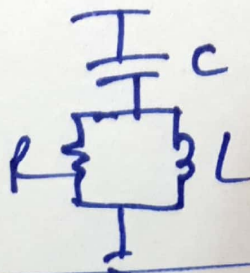

C-type H.P.F.

