

Topic \_\_\_\_\_

Date \_\_\_\_\_

## Measurement of Energy and Industrial Metering.

Energy is the total power delivered / consumed over a time interval, that is  
energy = power  $\times$  time

Electrical energy developed as work or dissipated as heat may be expressed as

$$W = \int_0^t v \cdot i \cdot dt$$

If  $v$  is expressed as  $V$ ,  $i$  in  $A$ ,  $t$  in sec, the unit of energy is joule or watt-sec. which is 1 watt over an interval of one second. If the unit of time is taken as hour, then energy is then expressed as watt hours.

### Energy Meters for AC circuits

Induction type of energy meters are universally used for measurement of energy in domestic and industrial ac circuits.

Induction type of meters possess lower friction & higher torque / weight ratio.

Induction type meters are inexpensive, accurate and retain their accuracy over a wide range of loads and temperature conditions.

Topic \_\_\_\_\_

Date \_\_\_\_\_

## Single Phase Induction Type Watt-hour Meter

Operating mechanism has four main parts

Driving  
System

Moving  
System

Braking  
System

Registering  
system

### a) Driving system

The driving system of the meter consists of two electromagnets. The core of these electromagnets is made up of silicon steel laminations.

The coil of one of the electromagnets is excited by the load current. This coil is called current coil.

The coil of second electromagnet is connected across the supply, and, therefore carries a current proportional to the supply voltage. This coil is called pressure coil. Consequently the two electromagnets are called series and shunt magnets, resp.

Copper shading bands are provided on the central limb. The position of these bands is adjustable. The function of these bands is to bring the flux produced by the shunt magnet exactly in quadrature with the applied voltage.

### b) Moving system

This consists of an aluminium disc mounted on a light alloy shaft. This disc is positioned


Topic \_\_\_\_\_

Date \_\_\_\_\_

in the air gap between series and shunt magnet. The upper bearing of the rotor (moving system) is a steel pin located in a hole in the bearing cap fixed to the top of the shaft. The rotor runs on a hardened steel pivot, screwed to the foot of the shaft. The pivot is supported by a jewel bearing. A pinion engages the shaft with the counting / registering mechanism.
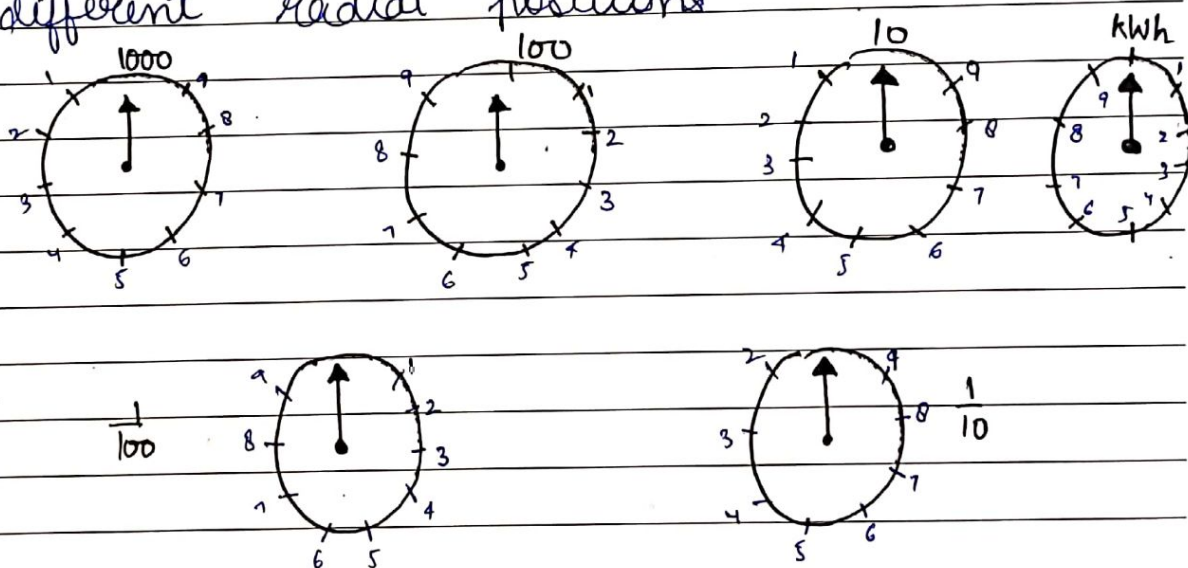
#### c) Braking System



A permanent magnet positioned near the edge of the aluminium disc forms the braking system. The aluminium disc moves in the field of this magnet and thus provides a braking torque. The position of the permanent magnet is adjustable, and, therefore braking torque can be adjusted by shifting the position of the permanent magnet to different radial positions.



Pointer type of register

d) Registering (Counting Mechanism) The function of registering / counting mechanism is to record continuously a number which is proportional to the revolutions made by the moving system. By a suitable system, a train of reduction gears, the pinion on the rotor shaft drives a series of five / six pointers. These rotate on round dials which are marked with ten equal divisions.


### Theory and Operation

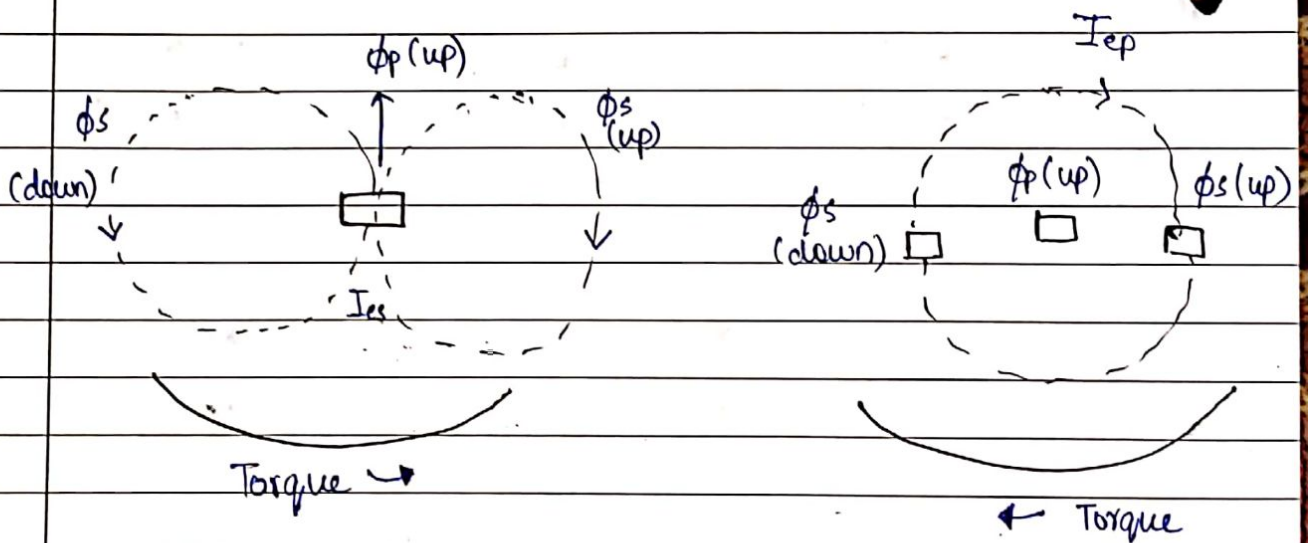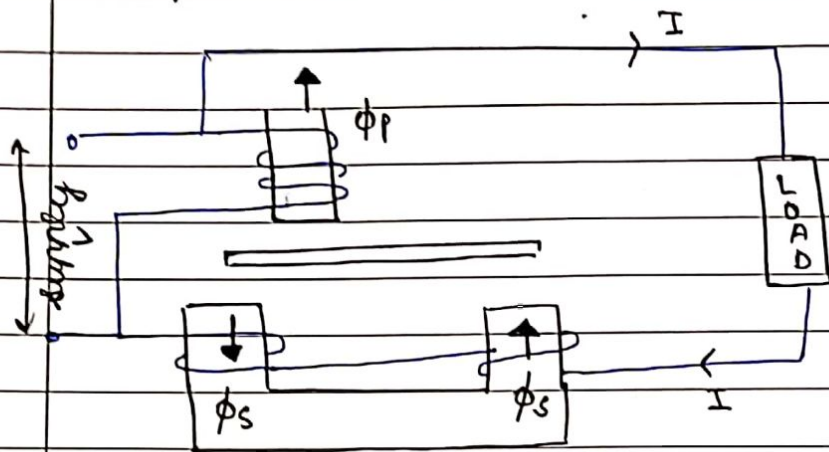

Working of a single phase induction type energy meter.

Topic

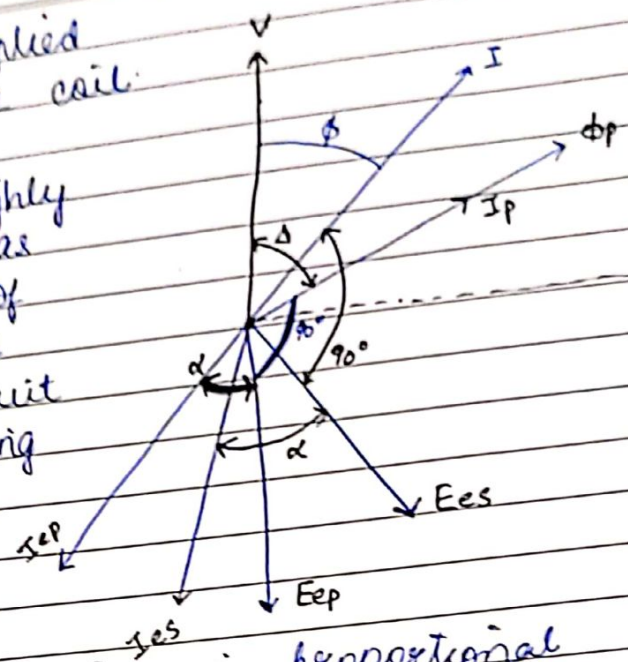- Supply voltage is applied across the pressure coil.
- Pressure coil is highly inductive as it has very large number of turns & reluctance of its magnetic circuit is very small owing to presence of air gaps of very small length.



- $I_p$  through pressure coil is proportional to the supply voltage and lags it by a few degrees less than  $90^\circ$ . This is because the winding has small resistance and there are iron losses in the magnetic circuit.

- Current  $I_p$  produces a flux  $\phi_{PE}$ . This flux divides itself into two parts -  $\phi_g$  and  $\phi_p$ . The major portion  $\phi_g$  flows across the side gaps as reluctance of this path is small.

- The reluctance of the path of flux  $\phi_p$  is large and hence magnitude is small. This flux  $\phi_p$  goes across aluminium disc and hence is responsible for production of driving torque.

• Flux  $\phi_p$  is in phase with current  $I_p$  &

Topic \_\_\_\_\_

Date \_\_\_\_\_

is proportional to it.  $\therefore \phi_p \propto$  voltage  $V$  and lags it by an angle a few degrees less than  $90^\circ$ .

- Since  $\phi_p$  is alternating in nature, it induces an eddy emf in disc which in turn produces eddy current,  $I_{ep}$ .
- The load current  $I$  flows through the current coil and produces a flux  $\phi_s$ .
- This flux is proportional to load current & is in phase with it. This flux produces eddy current  $I_{es}$  in the disc.
- Now eddy current  $I_{es}$  interacts with flux  $\phi_p$  to produce a torque & eddy current  $I_{ep}$  interacts with  $\phi_s$  to produce another torque.
- These torques are in the opposite direction and net torque is the difference of these.

Let  $V =$  applied voltage.

$I =$  load current.

$\phi =$  phase angle of load.

$I_p =$  pressure coil current

$Z =$  impedance of eddy current path

$\Delta =$  phase angle b/w supply voltage and pressure coil flux.

$f =$  frequency

Topic \_\_\_\_\_

Date \_\_\_\_\_

$E_{ep}$  = eddy emf induced by flux  $\phi_p$ .

$I_{ep}$  = eddy current due to flux  $\phi_p$ .

$E_{es}$  = eddy emf induced by flux  $\phi_s$ .

$I_{es}$  = eddy current due to flux  $\phi_s$ .

$\alpha$  = phase angle of eddy current path.

Net driving torque

$$T_d \propto \phi_1 \phi_2 \frac{f}{Z} \sin \beta \cos \alpha$$

$$= k_1 \phi_1 \phi_2 \frac{f}{Z} \sin \beta \cos \alpha$$

$k_1$  = constant.

$\beta$  = phase angle b/w fluxes  $\phi_1$  and  $\phi_2$ .

In our case,  $\phi$  are  $\phi_p$ ,  $\phi_s$ .

$$\therefore \beta = \text{phase angle between } \phi_p \text{ and } \phi_s \\ = \Delta - \phi$$

$$\therefore \text{Driving torque, } T_d = k_1 \phi_p \phi_s \frac{f}{Z} \frac{\sin(\Delta - \phi)}{\cos \alpha}$$

$$\text{But } \phi_p \propto V \quad \phi_s \propto I$$

$$\therefore T_d = k_2 \frac{V I f}{Z} \sin(\Delta - \phi) \cos \alpha$$

If  $f$ ,  $Z$  and  $\alpha$  are constant,

$$T_d = k_3 V I \sin(\Delta - \phi)$$

If  $N$  is the steady speed, braking torque

$$T_b = k_4 N$$

Topic \_\_\_\_\_

Date \_\_\_\_\_

At steady speed,  $T_d = T_b$

$$\therefore k_4 N = k_3 V I \sin(\Delta - \phi)$$

$$N = k \cdot V I \sin(\Delta - \phi)$$

If  $\Delta = 90^\circ$ ,  $N = k V I \sin(90 - \phi)$

$$\therefore N = k V I \cos \phi$$

$$N = k \times (\text{power})$$

$\therefore$  To make speed of rotation & power  $\Delta$  should be  $90^\circ$ .

$\therefore$   $\phi$  must be made to lag supply voltage by  $90^\circ$ .

$$\begin{aligned} \text{Total no' of revolutions} &= \int N \cdot dt \\ &= k \int V I \sin(\Delta - \phi) dt \end{aligned}$$

If  $\Delta = 90^\circ$ , Total no' of revolutions.

$$= k \int (V I \cos \phi) dt$$

$$= k \int (\text{power}) dt$$

$$= k \times (\text{energy}).$$

$\therefore$  Total no' of revolutions is a measure of the energy consumed directly.

Topic \_\_\_\_\_

Date \_\_\_\_\_

### VArh Metering

i, Measurement of VArh is a means of charging bulk consumers for failing to maintain a high power factor.

ii, Required for measurement of VArh.

iii, Used as a record of operating conditions when there is an exchange of energy b/w two or more interconnected power stations

Total no' of revolutions made in a specified time =  $k \int V I \sin(\Delta - \phi) dt$ .

If  $\Delta = 0^\circ$  or  $180^\circ$  (by making additional quadrature shift) then  $\cos \Delta = 1$

$$\text{No' of revolutions} = k \int V I \sin(0 - \phi) dt$$

$$= k \int V I \sin \phi dt = k \int (\text{VArh}) \cdot dt$$

$\therefore$  Induction type energy meter can be converted into reactive Volt-Ampere hour meter if pressure coil flux is brought in phase with the voltage.

## ENERGY METER TESTING.

Testing includes the checking of actual registration of the meter as well as adjustment done to bring the error of the meter within prescribed limits.

## AC METER TESTING.

- 1) At 5% of marked current with upf.
- (2) At 100 or 125% of marked current with upf.
- (3) At one intermediate load with upf.
- (4) At marked current and 0.5 lagging pf.
- (5) Creep Test : With applied voltage of 110% of its marked value of ~~current~~ & circuit of current open, meter should not revolve through more than one revolution.
- (6) Starting Test : At 0.5% of unmarked value of current and normal voltage, the meter should start and run.

## PHANTOM LOADING :

When current rating of a meter under test is high, a test with actual loading involves wastage of power.

To avoid this, phantom / fictitious loading is done.


Phantom loading consists of supplying the pressure circuit from a circuit of reqd normal voltage and the current circuit with a low voltage supply as the impedance of this circuit is very low.

Thus total power supplied for the test is due to = small pressure coil current at normal voltage + circuit current supplied at low voltage.

Thus power supplied is small.

Q. 220V, 5A dc energy meter is tested at its marked ratings. Resistance of pressure circuit is  $8000\Omega$  & that of current coil is  $0.1\Omega$ . Calculate the power consumed when testing the meter with :

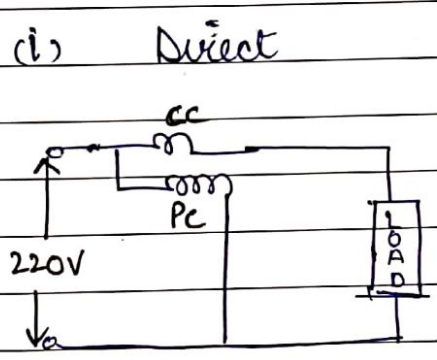- (i) direct loading
- (ii) Phantom loading with current circuit excited by a 6V battery.




Power in pressure ckt =  $\frac{(220)^2}{8000}$   
 $= 5.5W$

Power consumed in current circuit =  $220 \times 5 = 1100W$ .

$\therefore$  Total power consumed =  $5.5 + 1100 = 1105.5W$ .

ii, Phantom Loading

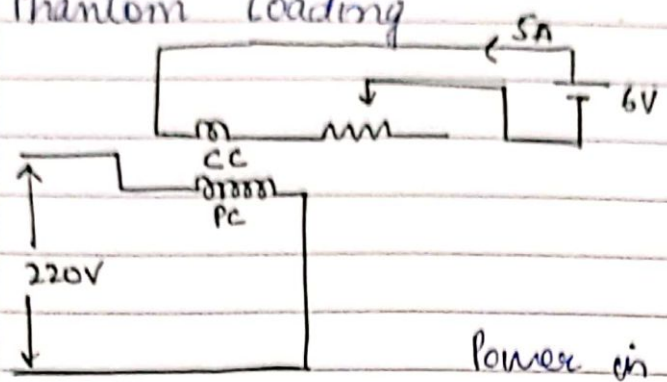

Power consumed in  
pressure circuit  

$$= \frac{(220)^2}{1000} = 5.5 \text{ W}$$

Power in current circuit =  $6 \times 5$   
 $= 30 \text{ W}$

Total power consumed =  $5.5 + 30 = 35.5 \text{ W}$ .

This power consumption is considerably smaller than the direct loading.

# Power Measurement

D.C. power may be measured by a wattmeter or by an ammeter or voltmeter, the product of whose readings gives the power in the circuit.

In a.c. circuits,

$$p = e i$$

Instantaneous power where  $e$  &  $i$  are instantaneous values of voltage & current.


For sinusoidal voltage and current and a phase angle  $\phi$  b/w them, the average power

$$P = EI \cos \phi$$

where  $E$  &  $I$  are rms values of voltage & current.

Thus we have to use a wattmeter and use of voltmeter & ammeter only can not compute power in a.c. circuits.

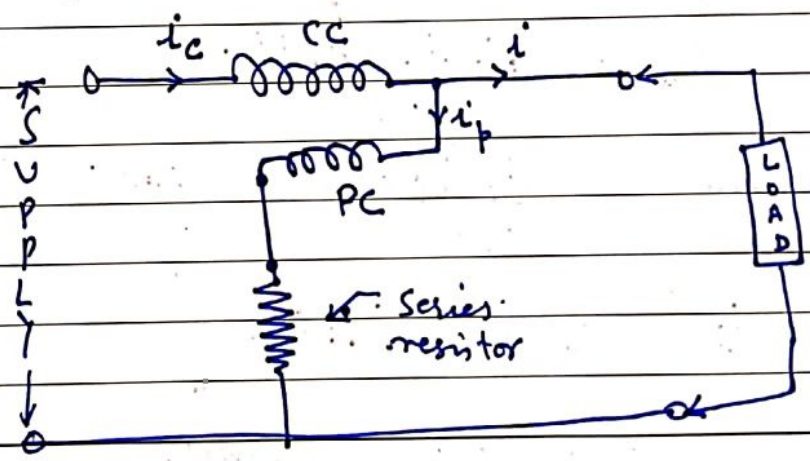Electrodynamometer type instrument principle is most commonly used wattmeter which has fixed and moving coils which react to the effect of current squared. The coils are connected in the form shown below :-



Topic

Date

The fixed or field coil carries the total line current  $i_c$ . The movable coil is located in the magnetic field of the fixed coil. A high resistance is connected in series with movable coil which limits the current  $i_p$  through it. The movable coil is also known as voltage or pressure coil. The

$$i_p = \frac{e}{R_p} \quad \text{where } e = \text{inst voltage across the load } \& R_p$$

is the total resistance of the movable coil & its series resistance.

The deflection of movable coil is proportional to the product of two currents  $i_c$  &  $i_p$ . Thus average deflection:

$$\theta_{av} = K \frac{1}{T} \int_0^T i_c i_p dt$$

$$i_c = i_p + i; \quad i_p = \frac{e}{R_p}$$

$$\theta_{av} = K' \frac{1}{T} \int_0^T (i_p + i) \frac{e}{R_p} dt$$

Since  $i_p$  is very small;  $\therefore i_c \approx i$ ,

$$\theta_{av} = K' \frac{1}{T} \int_0^T e i dt$$

$$\text{now } \frac{1}{T} \int_0^T e i dt = P_{av} = EI \cos \phi$$

$$\boxed{\theta_{av} = K' EI \cos \phi}$$

Citizen

Deflection  $\propto$  Power  
Thus an electro-dynamometer type watt indicates average power delivered to the load.

Topic \_\_\_\_\_

Date \_\_\_\_\_

The electrodynamic wattmeter consumes some power for maintenance of its magnetic field but it is actually so small as compared to load power, that it may be neglected. However if a correct reading of the load power is required, the current coil should exactly carry the load current, and the potential coil should be connected across the load terminals.

Two configurations are possible.

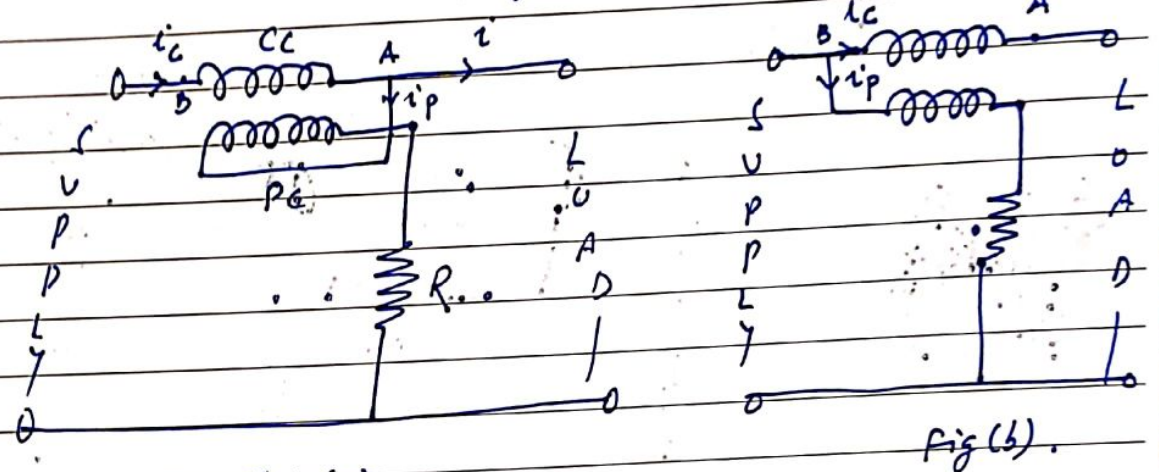


Fig (a)

Fig (b)


The voltage is properly metered but the current coil carries an extra current which is higher than load current by  $i_p$ . ( $i_c = i + i_p$ ); This wattmeter reading is higher by an amount of additional power loss in the voltage circuit.

The current is metered exactly but the voltage across pressure coil is higher than the load voltage by an amount of  $V \cdot D$  in the current coil. Thus wattmeter reading is again higher by an amount of power loss in the C.C.

choice of connection depends the situation.  
 Generally fig (a) is preferred for HCLV applications and fig (b) is preferred for HVLC applications.

However we can exactly measure load power by providing compensation to this increase reading.

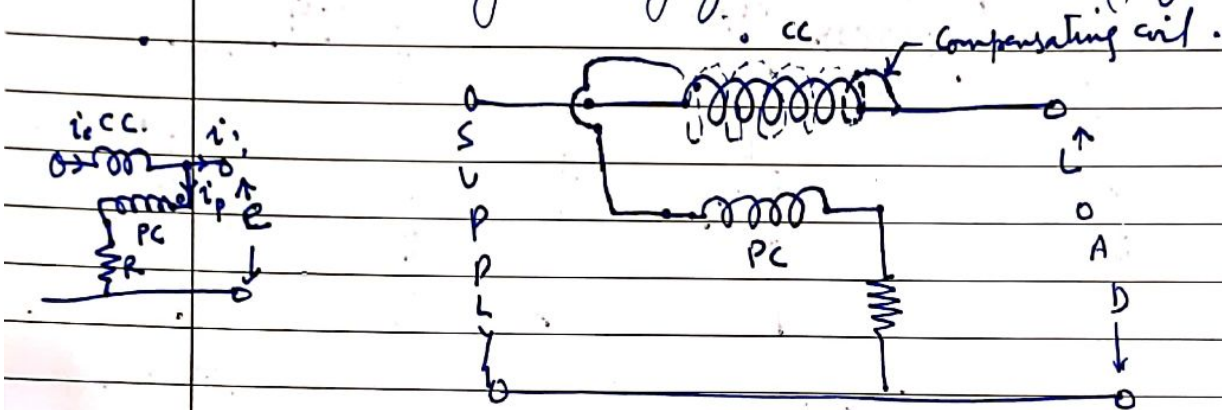Consider for configuration shown in fig (a).




The compensating coil is in series

with the voltage coil ~~circuit~~ but in such a way that it produces magnetic effect that opposes the magnetic effect produced by current coil current. Thus neutralizes the voltage coil component of the current in the current coil.


Under no load, the deflection would be zero.

# Measurement of power without using a wattmeter

## ii. Three-voltmeter method

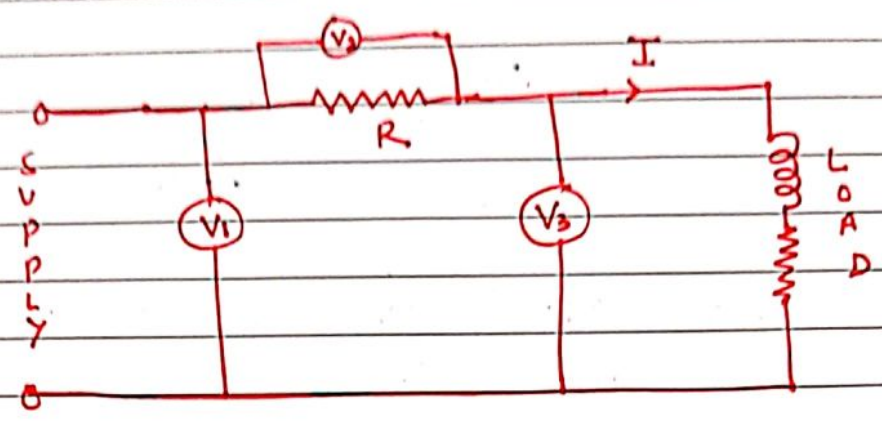

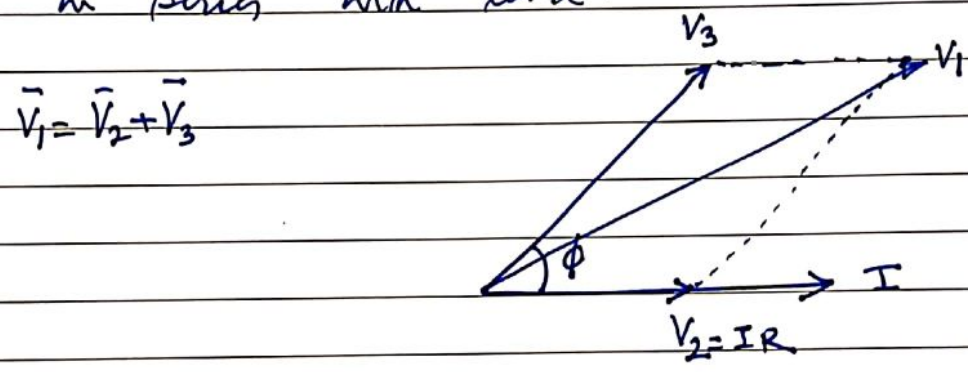These voltmeters  $V_1$ ,  $V_2$  and  $V_3$  are connected as shown b/w supply & load.  $R$  is a non-inductive resistor connected in series with load.



$$V_1^2 = V_2^2 + V_3^2 + 2V_2V_3 \cos \phi$$

neglecting currents taken by voltmeters  $V_2$  &  $V_3$ ,  $R$  carries the same load current; Thus  $V_2 = IR$ .

$$\therefore V_1^2 = V_2^2 + V_3^2 + 2IRV_3 \cos \phi$$

$$= V_2^2 + V_3^2 + 2R(V_3 I \cos \phi);$$

Now  $V_3 I \cos \phi =$  load power;

Topic

Date


$$\therefore \text{power in load } V_3 I \cos \phi = \frac{V_1^2 - V_2^2 - V_3^2}{2R}$$

and power factor is given by


$$\cos \phi = \frac{V_1^2 - V_2^2 - V_3^2}{2 V_2 V_3}$$

Two assumptions are made: - R contains the same current as load current.  
 & Resistor is entirely non-inductive.

iii) Three Ammeter method

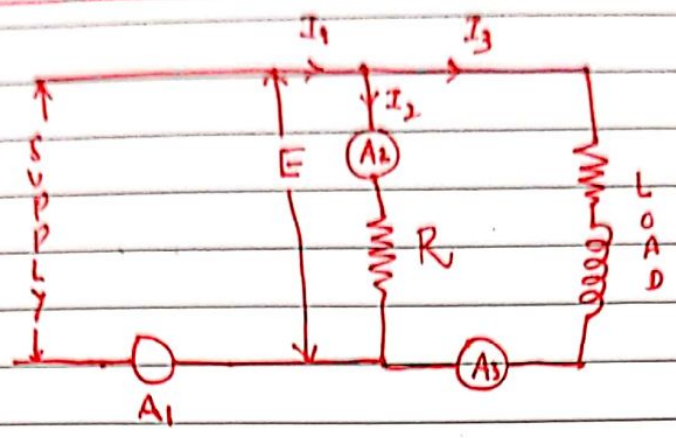

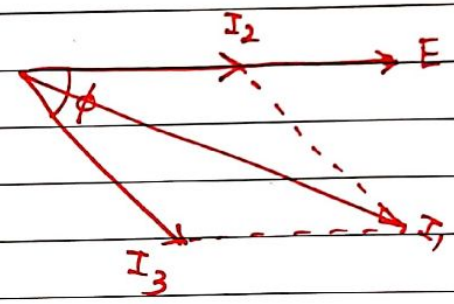The reading of Ammeter  $A_1$  is the vector sum of readings of Ammeters  $A_2$  &  $A_3$ .



$R$  is a non inductive resistor through current  $I_2$  flows which is in phase with voltage  $E$ .

from vector diagram;  $I_1^2 = I_2^2 + I_3^2 + 2I_2I_3\cos\phi$

but  $I_2 = E/R$ ;

$$I_1^2 = I_2^2 + I_3^2 + 2 \cdot \frac{E}{R} I_3 \cos\phi$$

$$= I_2^2 + I_3^2 + \frac{2}{R} (EI_3 \cos\phi)$$

Hence load power is  $E I_3 \cos\phi = \frac{(I_1^2 - I_2^2 - I_3^2) R}{2}$

$\therefore$  p.f.  $\cos\phi = \frac{I_1^2 - I_2^2 - I_3^2}{2 I_2 I_3}$


Topic

Date

# Measurement of Power in 3-phase circuits (3-φ).

(a) using 1-wattmeter:

## Blondal's Theorem

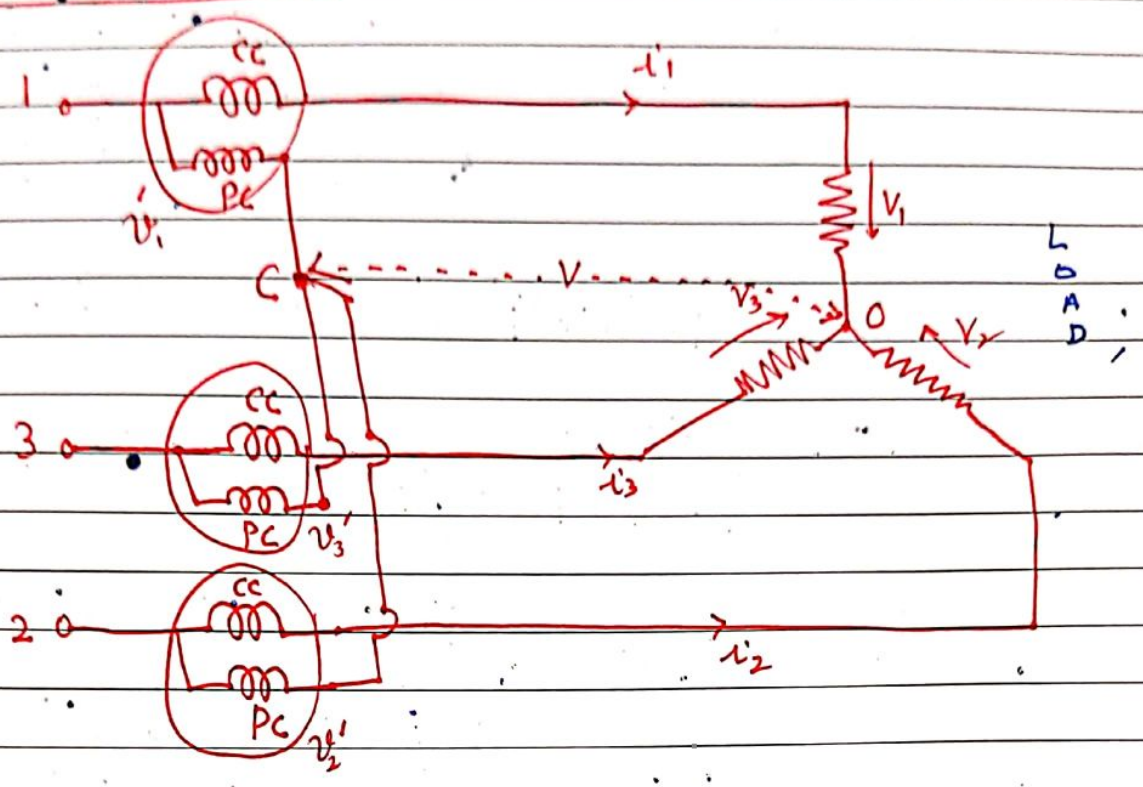

If a network is supplied through  $n$  conductors, the total power is measured by summing the readings of  $n$  wattmeters so arranged that a current element of a wattmeter is in each line and the corresponding voltage element is connected between that line and a common point. If the common point is located on one of the lines, then the power may be measured by  $(n-1)$  wattmeters.

Consider a Y-connected 3-phase load supplied from a 3-φ supply with wattmeters connect in each line. The common point of pressure coils is at C which is different from the potential at O by  $[V]$ .

Topic \_\_\_\_\_

Date \_\_\_\_\_

Total instantaneous power in the load  

$$p = v_1 i_1 + v_2 i_2 + v_3 i_3$$

Now reading of wattmeter 1,  $p_1 = v_1' i_1$   
 " " " 2,  $p_2 = v_2' i_2$   
 " " " 3,  $p_3 = v_3' i_3$

Now  $v_1 = v + v_1'$ ,  $v_2 = v + v_2'$ ,  $v_3 = v + v_3'$

Also;  
 $\therefore p_1 = (v_1 - v) i_1$ ,  $p_2 = (v_2 - v) i_2$ ,  $p_3 = (v_3 - v) i_3$

$$\begin{aligned} \therefore p_1 + p_2 + p_3 &= v_1 i_1 - v i_1 + v_2 i_2 - v i_2 + v_3 i_3 - v i_3 \\ &= v_1 i_1 + v_2 i_2 + v_3 i_3 - v(i_1 + i_2 + i_3) \end{aligned}$$

now ~~total power~~  $= v_1 i_1 + v_2 i_2 + v_3 i_3$   
 ~~$p =$~~


Thus sum of three wattmeters is nothing but  
 the three phase power.

$$p_1 + p_2 + p_3 = 3-\phi \text{ power} =$$

Topic \_\_\_\_\_

Date \_\_\_\_\_

Two wattmeter Method

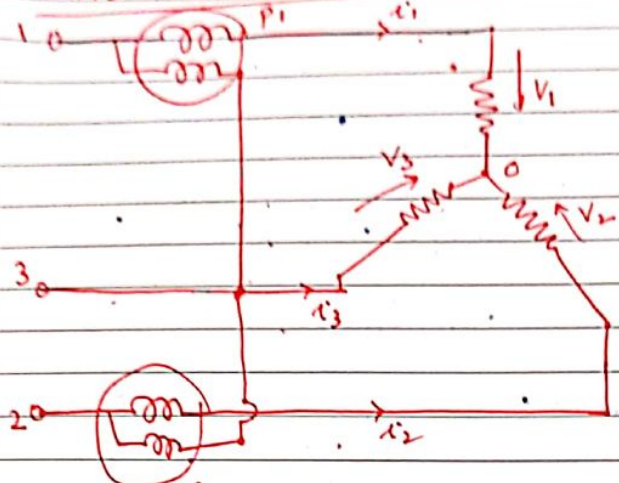

Y-Connected Load.

Reading of wattmeter 1 ;  $P_1 = i_1(V_1 - V_3)$

" " " " 2  $P_2 = i_2(V_2 - V_3)$

Sum of wattmeter readings  $S = P_1 + P_2$


$= i_1 V_1 - i_1 V_3 + i_2 V_2 - i_2 V_3$

$= V_1 i_1 + V_2 i_2 - V_3 (i_1 + i_2)$

KCL at o  $\rightarrow i_1 + i_2 + i_3 = 0 \therefore i_1 + i_2 = -i_3$

$S = P_1 + P_2 = V_1 i_1 + V_2 i_2 + V_3 i_3$   
 $= 3\text{-}\phi \text{ power}$

$\Delta$ -Connected Load.

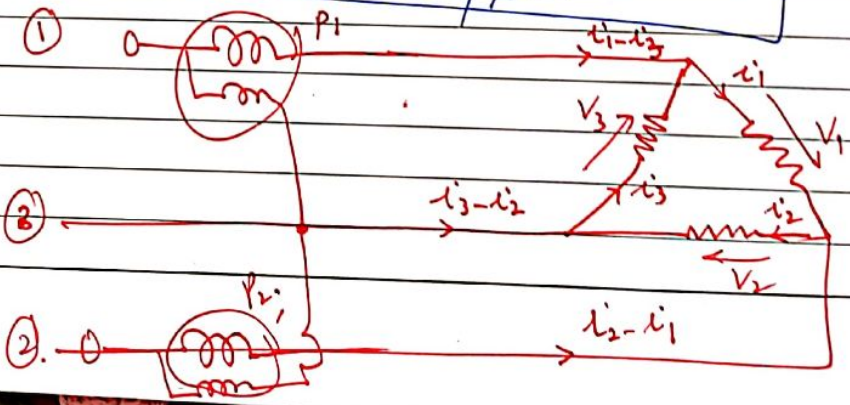

Citizen

In  $\Delta$  connected load :

$$P_1 = (i_1 - i_3)(-V_3)$$

$$P_2 = (i_2 - i_1)(V_2)$$


$$\begin{aligned} \text{Sum } P_1 + P_2 &= -i_1 V_3 + i_3 V_3 + i_2 V_2 - i_1 V_2 \\ &= -i_1 (V_2 + V_3) + V_2 i_2 + V_3 i_3 ; \end{aligned}$$

$$\text{KVL in loop} = V_1 + V_2 + V_3 = 0 \Rightarrow V_2 + V_3 = -V_1$$

$$\therefore P_1 + P_2 = V_1 i_1 + V_2 i_2 + V_3 i_3 = \text{3-phase power}$$

3-phase Balanced System

$V_{10}$  (Y-connection).

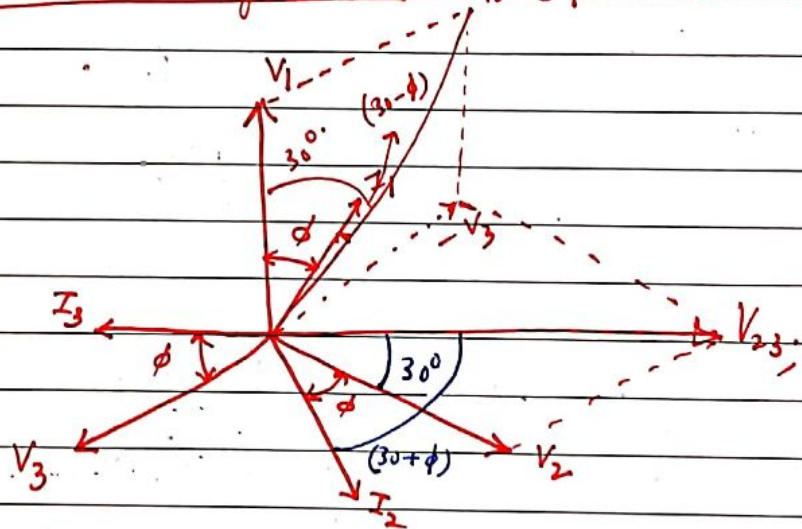

Topic

for a balanced system. Date


Let  $V_1 = V_2 = V_3 = V$  (rms phase voltage).

$I_1 = I_2 = I_3 = I$  (rms phase current).

$V_{13} = V_{23} = V_{12} = \sqrt{3}V$  line voltages.

Pro  $\rightarrow$  line current is same as phase current for Y-connection.

Let power factor =  $\cos \phi$ ;

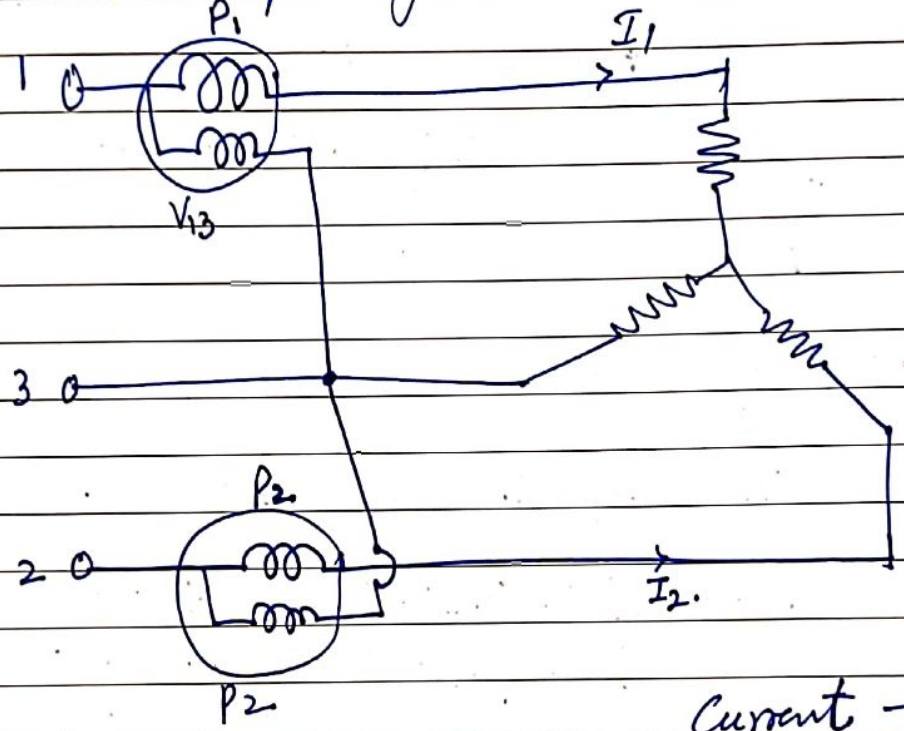

Reading of wattmeter 1  $\rightarrow$

Current -  $I_1$ ;

voltage -  $V_{13}$ .

$\therefore$  b/w  $I_1, V_{13} = 30 - \phi$ ;

$$P_1 = V_{13} I_1 \cos(30 - \phi)$$

$$P_1 = \sqrt{3} V I \cos(30 - \phi).$$

Reading of wattmeter 2  $\rightarrow$

Current -  $I_2$

voltage -  $V_{23}$

$\therefore$  b/w  $I_2, V_{23} = 30 + \phi$ .

$$P_2 = V_{23} I_2 \cos(30 + \phi)$$

$$= \sqrt{3} V I \cos(30 + \phi).$$

$$\text{Now } P_1 + P_2 = \sqrt{3}VI [\cos(30-\phi) + \cos(30+\phi)]$$

$$= 3VI \cos \phi; = \underline{3-\phi \text{ power}}$$

Power factor:

$$\text{Similarly } P_1 - P_2 = \sqrt{3}VI [\cos(30-\phi) - \cos(30+\phi)]$$

$$= \sqrt{3}VI \sin \phi;$$

$$\therefore \frac{P_1 - P_2}{P_1 + P_2} = \frac{\sqrt{3}VI \sin \phi}{3VI \cos \phi} = \frac{\tan \phi}{\sqrt{3}};$$

$$\therefore \phi = \tan^{-1} \sqrt{3} \left( \frac{P_1 - P_2}{P_1 + P_2} \right)$$

Effect of Power factor upon readings of wattmeter.

i) with P.f = 1.0 ;  $\cos \phi = 1$  ;  $\phi = 0^\circ$  ;

$$P_1 = \sqrt{3}VI \cos(30+\phi) = \frac{3}{2}VI$$

$$P_2 = \sqrt{3}VI \cos(30-\phi) = \frac{3}{2}VI$$

Total 3- $\phi$  power:  $P = 3VI$  ; at unity p.f.

ii) When P.f = 0.5 ;  $\phi = 60^\circ$  ;

$$P_1 = \sqrt{3}VI \cos(30+60) = \frac{3}{2}VI;$$

$$P_2 = \sqrt{3}VI \cos(30-60) = \text{zero};$$

$$\therefore \text{Total power } P = \frac{3}{2}VI + \text{zero} = \frac{3}{2}VI;$$

$$\text{now } 3-\phi \text{ power} = 3VI \cos \phi = \frac{3}{2}VI;$$

Topic \_\_\_\_\_

Date \_\_\_\_\_

⑧ When  $P.F = 0$ ;  $\phi = 90^\circ$ ;

$$P_1 = \sqrt{3} VI \cos(30+90^\circ) = \frac{\sqrt{3}}{2} VI$$


$$P_2 = \sqrt{3} VI \cos(30-90^\circ) = -\frac{\sqrt{3}}{2} VI$$

Total power  $P = P_1 + P_2 = \text{Zero}$ .

Readings of two wattmeters are same but of opposite sign. Total 3- $\phi$  power is zero.
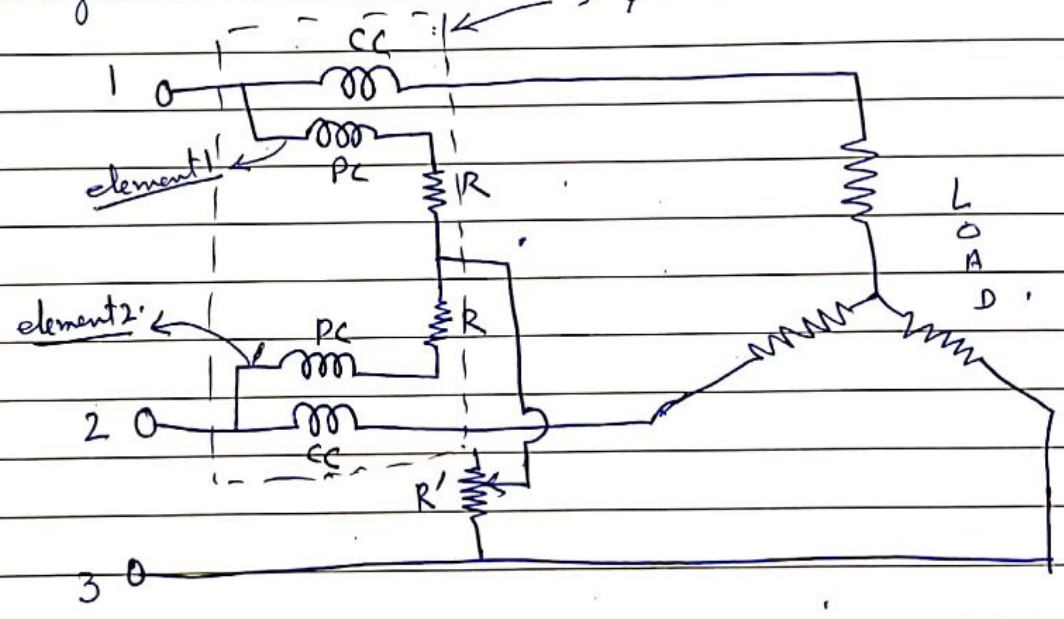
### Three phase wattmeter

The dynamometer type three phase wattmeter consists of two separate wattmeter moments mounted together in one case on the same spindle. The arrangement looks like :- 3- $\phi$  wattmeter



The connections of 2 elements of a 3- $\phi$  wattmeter are the same as that for two wattmeter



Topic

Date

### Measurement of Reactive power :-

$$\text{Reactive power } \Rightarrow Q = VI \sin \phi$$


The apparent power is  $VI$  which determines the line and generator capacity. The value of apparent power is determined by


$$VI = \sqrt{P^2 + Q^2}$$

$P = VI \cos \phi$ $Q = VI \sin \phi$ $S = P + jQ$
--
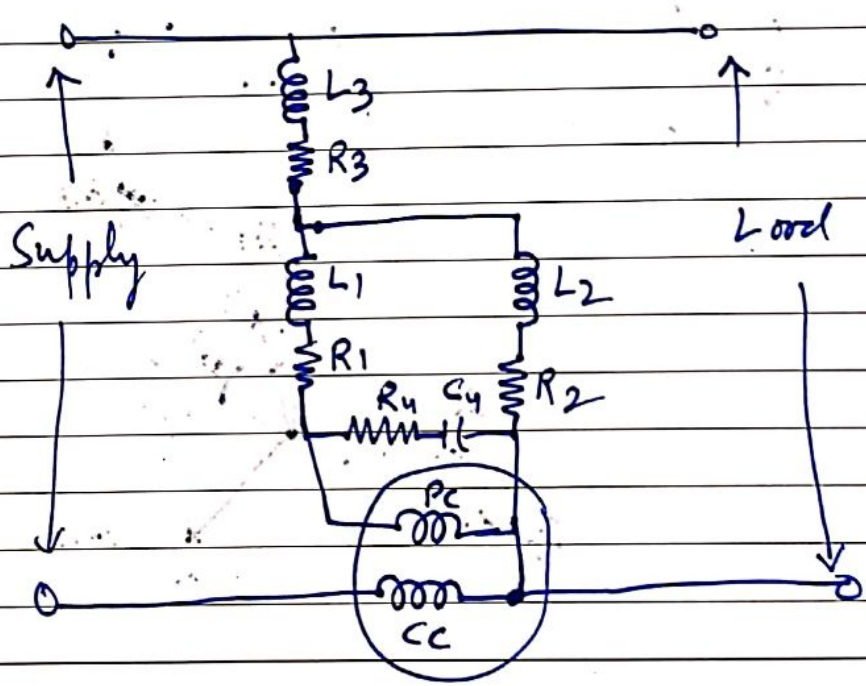
### Single phase VAR Meter

This is the same electro-dynamometer wattmeter in whose pressure coil circuit a large inductive reactance is substituted for the series resistance. So that the pressure coil current is in quadrature with the voltage.





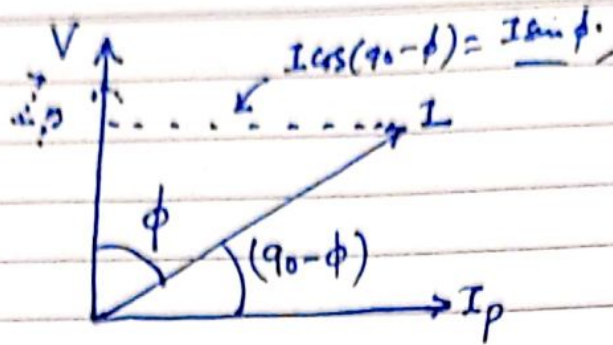

under these conditions the wattmeter again reads  $V I \cos(90 - \phi) = V I \sin \phi = \text{reactive power}$ .

Three phase VAR Meter :-

a) Making use of a wattmeter (1-phi).

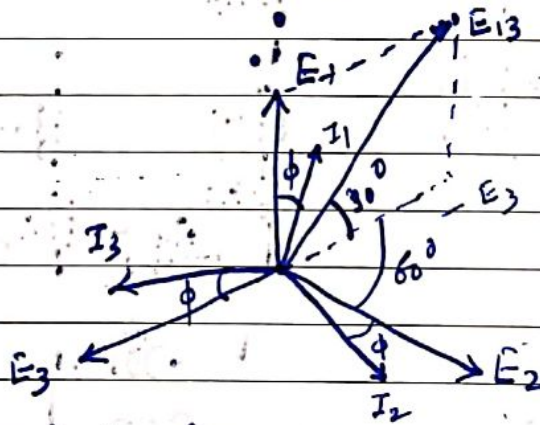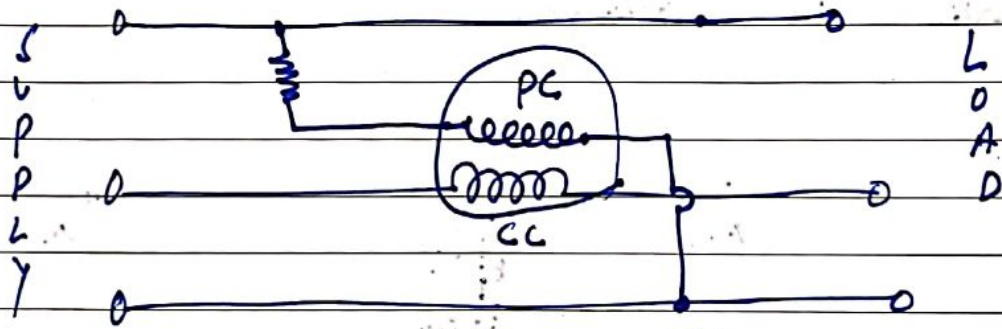

The single phase wattmeter is connected as shown with current coil in line 2 and pressure coil across lines 1 & 3.

Current in the current coil =  $I_2$

voltage across press. coil =  $E_{13} = E_1 - E_3$ ;

angle b/w  $E_{13}$  and  $I_2 = 30 + 60 + \phi = (90 + \phi)$

$$\begin{aligned} \therefore \text{Wattmeter reading} &= I_2 E_{13} \cos(90 + \phi) \\ &= -\sqrt{3} EI \sin \phi; \\ &= -W_r. \end{aligned}$$

$$\begin{aligned} \text{Now } 3\text{-}\phi \text{ reactive power} &= 3 EI \sin \phi \\ &= 3 \times \frac{W_r}{\sqrt{3}} \end{aligned}$$

$$\boxed{3\text{-}\phi \text{ VAR} = \sqrt{3} W_r}$$


Let  $W$  is Total active power ( $3\text{-}\phi$ );



$$\boxed{\phi.f = \tan^{-1} \frac{\sqrt{3} W_r}{W}}$$

∴
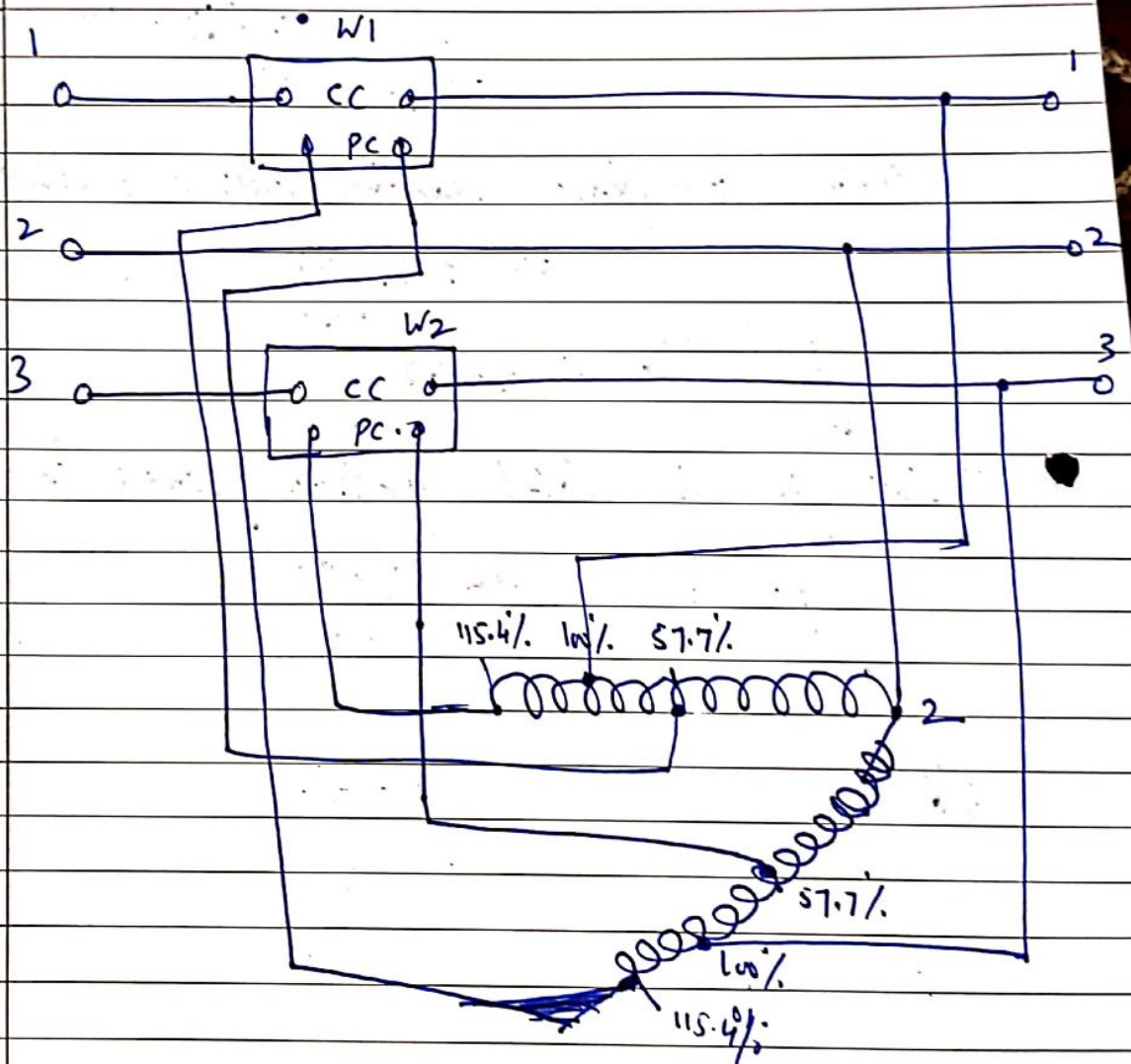
### 3-phase VAR meter :-

In three phase circuits phase shifting necessary for the measurement of reactive power is usually obtained with the help of phase shifting transformer. This phase shifting may be done with two auto transformers connected in open-delta configuration as shown in following ckt diagram.



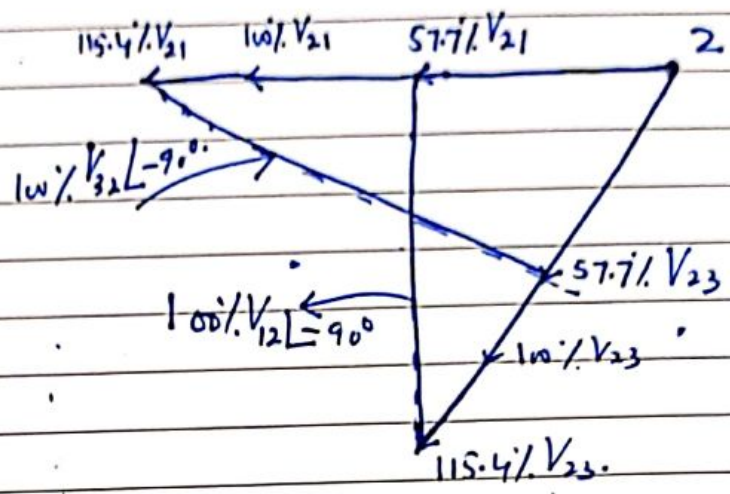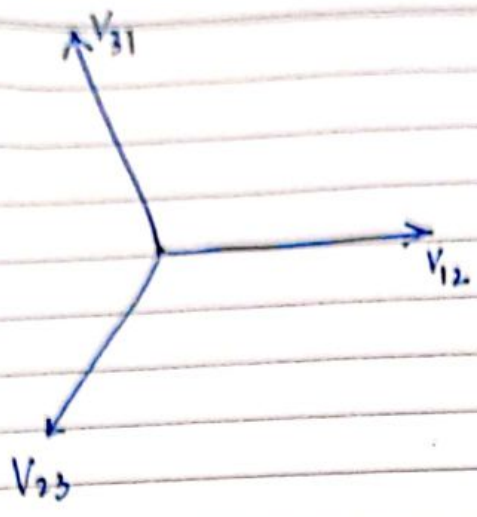

The current coils of the wattmeters are connected in series with the lines as usual. The potential coils are connected as shown. Phase 2 is connected to the common terminals of the two autotransformers and phase 1 & 3 of lines are connected to 100% taps on the Xmers. Both transformers will produce 115.4% of the line voltage across the total winding.

The pressure coil of wattmeter 1 is connected from 57.7% tap on transformer 1 to the 115.4% tap on transformer 2 which produces a voltage equal to line voltage but shifted by 90° as shown in phasor diagram. The pressure coil of wattmeter 2 is connected in a similar way. Since both coils receive a voltage equal to the line voltage but displaced by 90° the wattmeters indicate the reactive power consumed by load. The arithmetic sum of two wattmeters gives the total 3-φ reactive power.

Citizen