

# Nodal Analysis

Nodal analysis uses node voltages as circuit variables rather than currents as used in mesh analysis. This is very convenient as well reduces the number of equations.

Nodal analysis is very comfortable to be used for circuits that have only current sources where as mesh analysis is comfortable to use with circuit having voltage sources.

Steps involved in nodal analysis are

Step I Select one node as reference node. Assign node voltages  $V_1, V_2, V_3, \dots$  to rest of nodes. These voltages are referenced w.r.t. reference voltage.


Step II Apply KCL at nodes  $V_1, V_2, V_3, \dots$  using Ohm's law to express branch currents.

Step III Solve the simultaneous equations to obtain unknown node voltages. Subsequently find branch currents through all elements.

The reference node is commonly called ground and it is assumed to have zero potential.



Consider a circuit given below :-

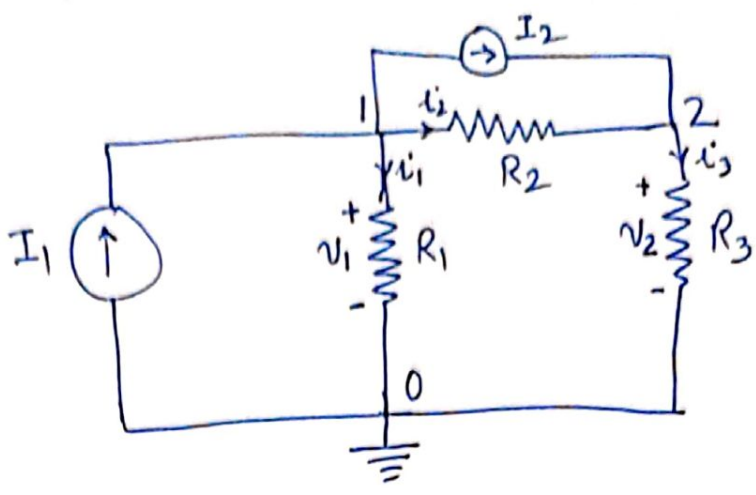

Node 0  $\rightarrow$  reference.

There are two other nodes ① & ② whose voltages w.r.t. to reference are selected as  $V_1$  &  $V_2$ .

Apply KCL at ① & ②.

$$I_1 = I_2 + i_1 + i_2 \quad \& \quad I_2 + i_2 = i_3$$

now  $i_1 = \frac{V_1 - 0}{R_1}$ ;  $i_2 = \frac{V_1 - V_2}{R_2}$ ;  $i_3 = \frac{V_2 - 0}{R_3}$ ;

$$I_1 = I_2 + \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} \quad \text{--- ①.}$$

$$\text{or } I_2 = \frac{V_2 - 0}{R_3} - \frac{V_1 - V_2}{R_2} \quad \text{--- ②.}$$

$$\left( \frac{V_1}{R_1} + \frac{V_1}{R_2} \right) - \frac{V_2}{R_2} = I_1 - I_2 \quad \text{--- ③.}$$

$$\left( \frac{V_2}{R_3} + \frac{V_2}{R_2} \right) - \frac{V_1}{R_2} = I_2 \quad \text{--- ④.}$$

$$\begin{aligned} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) V_1 - \left( \frac{1}{R_2} \right) V_2 &= I_1 - I_2 \\ \left( \frac{1}{R_2} + \frac{1}{R_3} \right) V_2 - \left( \frac{1}{R_2} \right) V_1 &= I_2 \end{aligned} ;$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right) V_1 - \left(\frac{1}{R_2}\right) V_2 = I_1 - I_2$$

$$\left(-\frac{1}{R_2}\right) V_1 + \left(\frac{1}{R_2} + \frac{1}{R_3}\right) V_2 = I_2$$

we can express in matrix form as;

$$\begin{bmatrix} \left(\frac{1}{R_1} + \frac{1}{R_2}\right) & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \left(\frac{1}{R_2} + \frac{1}{R_3}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 - I_2 \\ I_2 \end{bmatrix}$$

We can solve these two equations to find  $V_1$  &  $V_2$ .

How to write the above equations by mere inspection;


The first element is  $(2 \times 2)$  matrix;

All diagonal elements are +ve and off diagonal elements are negative. The first element is sum of reciprocals of resistances connected to node 1. The second element is minus times reciprocal of resistance b/w node 1 & node 2. The third similarly -ve of ~~sum~~ reciprocal of resistance b/w node 2 & 1 and the last is sum of reciprocals of resistances connected to nodes ②.

The 2nd element is matrix of node voltages  $V_1, V_2$ .

The third element is ~~sum~~ matrix of the currents; first element is sum of currents entering and leaving the node. Current entering is taken +ve and current away from node is -ve.

Example :-

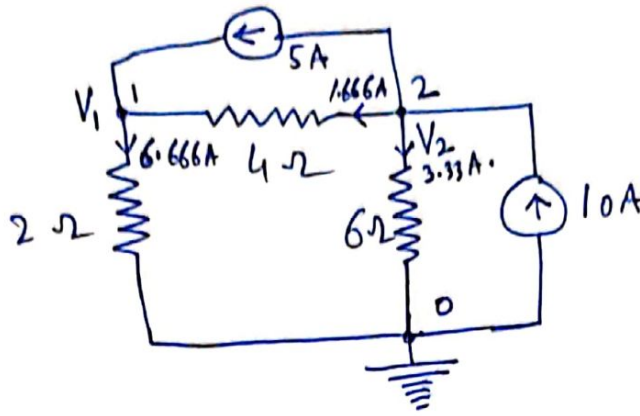

$$\frac{\frac{1}{4} + \frac{1}{6}}{3+2} = \frac{5}{12}$$

$$12 \left( \frac{50}{4} \right) \cdot 0.17$$

Two nodes ① & ② with  $V_1$  &  $V_2$  and node 0 as reference nodes.

$$\begin{bmatrix} \left(\frac{1}{2} + \frac{1}{4}\right) & -\frac{1}{4} \\ -\frac{1}{4} & \left(\frac{1}{4} + \frac{1}{6}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 10 - 5 \end{bmatrix}$$

$$\begin{bmatrix} 0.75 & -0.25 \\ -0.25 & 0.41 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 5 \end{bmatrix}$$

$$0.75 V_1 - 0.25 V_2 = 5$$

$$-0.25 V_1 + 0.41 V_2 = 5$$

Solve for  $V_1$  &  $V_2$  to get ; ;


$$\begin{aligned} V_1 &= 13.333 \text{ V} \\ V_2 &= 20 \text{ V} \end{aligned}$$

Current through  $6\Omega = \frac{20}{6} = 3.33 \text{ A}$ ;

Current through  $4\Omega = \frac{V_2 - V_1}{4} = \frac{20 - 13.33}{4} = \frac{6.667}{4} = \frac{6.67}{4} = \underline{\underline{1.66 \text{ A}}}$

Current through  $2\Omega = \frac{V_1}{2} = \frac{13.333}{2} = \underline{\underline{6.666 \text{ A}}}$

Example

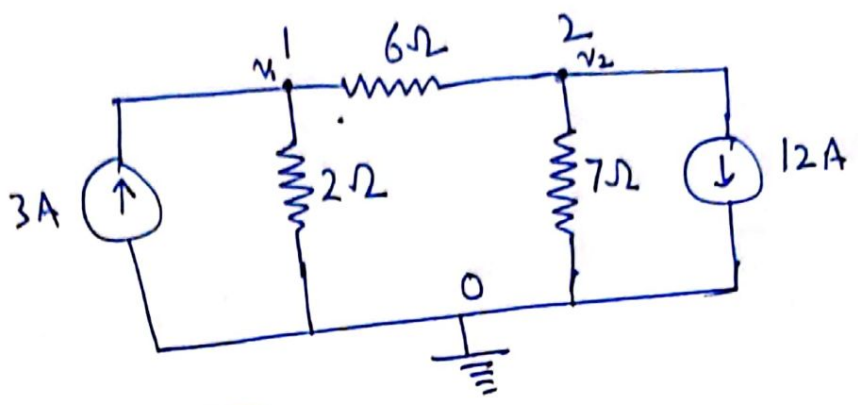

Find  $V_1$  &  $V_2$


write  $V_1 = -6V$  ;  $V_2 = -42V$

Nodal Analysis with voltage sources.

We consider two possibilities;

Case 1 If a voltage source is connected between the reference node and a non reference node. we simply set the voltage at the non-reference node equal to voltage of the voltage source.

Consider following example.

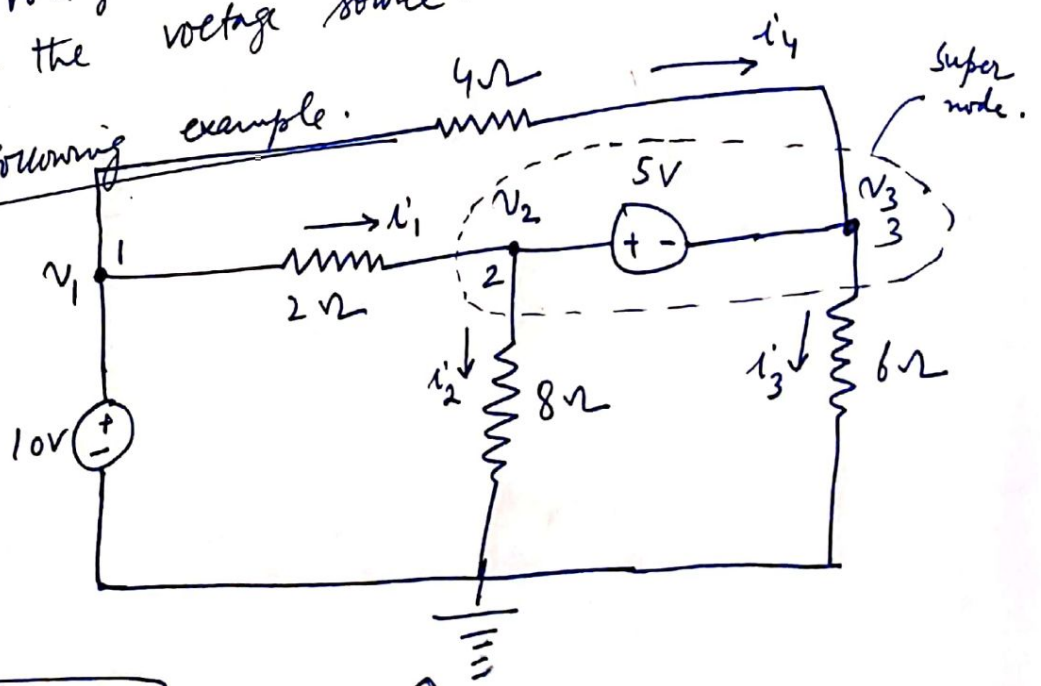

$V_1 = 10V$


Case 2 If the voltage source (dependent or independent) is connected b/w two non reference nodes, the two non reference nodes form a generalized node or super node. we apply KCL & KVL to determine the node voltages.

Thus nodes (2) & (3) form a super node.

KCL at super node:

$$i_1 + i_4 = i_2 + i_3$$
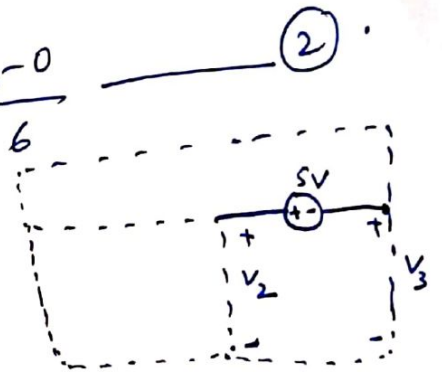
$$\frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} = \frac{V_2 - 0}{8} + \frac{V_3 - 0}{6}$$



KVL in super node:-

$$V_2 - 5 - V_3 = 0$$




$$V_2 - V_3 = 5$$

Solve in (1), (2), & (3) to get  $V_1, V_2$  &  $V_3$ .

Properties of a Super node.

1. The voltage source inside a super node provides a constraint equation needed to solve for node voltages.
2. A super node has no voltage of its own
3. A super node requires the application of both KCL and KVL.

Example.

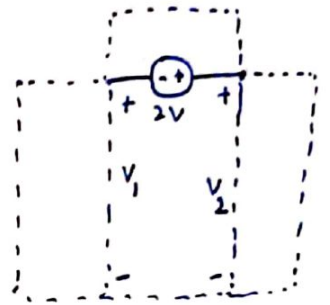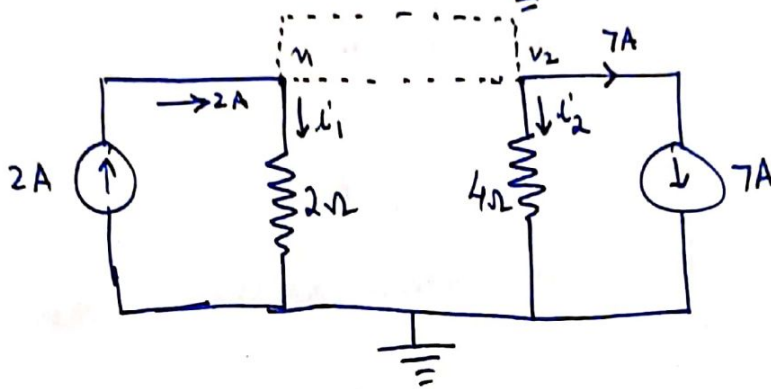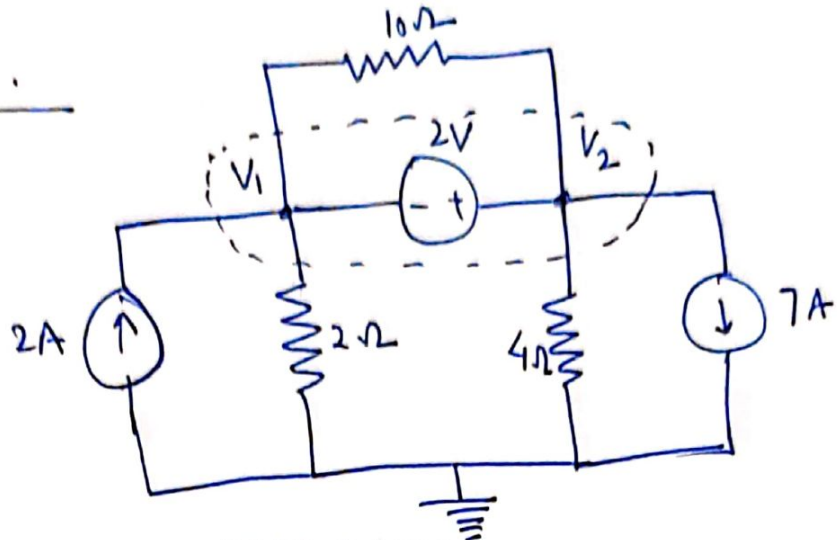

Apply KCL  $2 = i_1 + i_2 + 7$

$$2 = \frac{V_1}{2} + \frac{V_2}{4} + 7$$

$$\frac{V_1}{2} + \frac{V_2}{4} = -5$$

$$\frac{2V_1 + V_2}{4} = -5$$

$$\text{or } 2V_1 + V_2 = -20$$

$$V_2 = -20 - 2V_1$$

Apply KVL ;  $V_1 + 2 - V_2 = 0$

$$V_1 - V_2 = -2 \quad \therefore V_1 = V_2 - 2$$

$$\therefore V_2 = -20 - 2(V_2 - 2)$$

$$= -20 - 2V_2 + 4$$

$$V_2 + 2V_2 = -16$$

$$3V_2 = -16$$

$$V_2 = \frac{-16}{3} = -5.333$$


$$\therefore V_1 = -5.333 - 2$$

$$V_1 = -7.333$$

$$V_1 = -7.333 \text{ V}$$

$$V_2 = -5.333 \text{ V} \quad \text{Ans.}$$


Example.

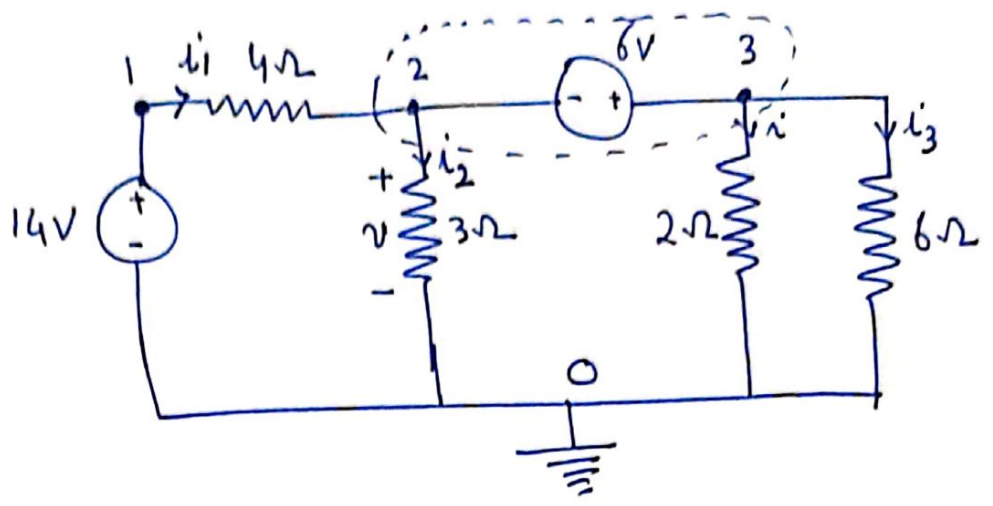

Sol. voltage source between 0 & ①;  $\therefore 14V$ ;

$$V_1 = 14V$$

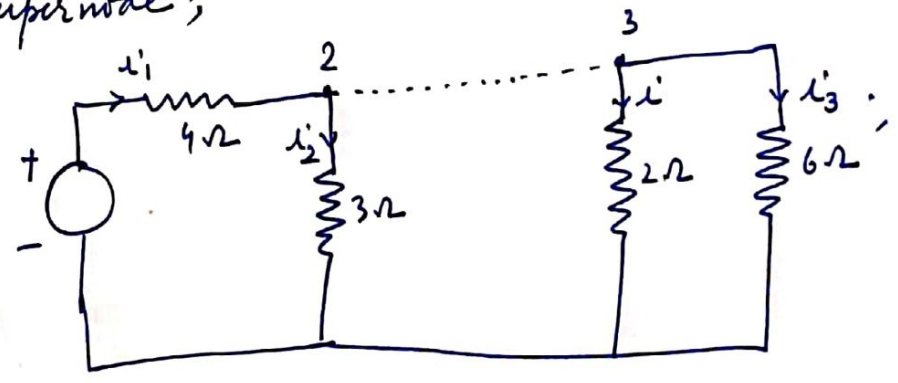6V voltage source b/w ② & ③;  $6V$ ;  
 non-reference nodes;  
 results a supernode;



KCL at supernode.

$$i_1 = i_2 + i + i_3$$

$$\frac{V_1 - V_2}{4} = \frac{V_2}{3} + \frac{V_3}{2} + \frac{V_3}{6}$$


$$\frac{V_1}{4} = \frac{V_2}{4} + \frac{V_2}{3} + \frac{V_3}{2} + \frac{V_3}{6}$$

$$= \frac{3V_2 + 4V_2 + 6V_3 + 2V_3}{12}$$

$$\frac{V_1}{4} = \frac{7V_2 + 8V_3}{12}$$

$$V_1 = \frac{7V_2 + 8V_3}{3}$$

KVL in supernode

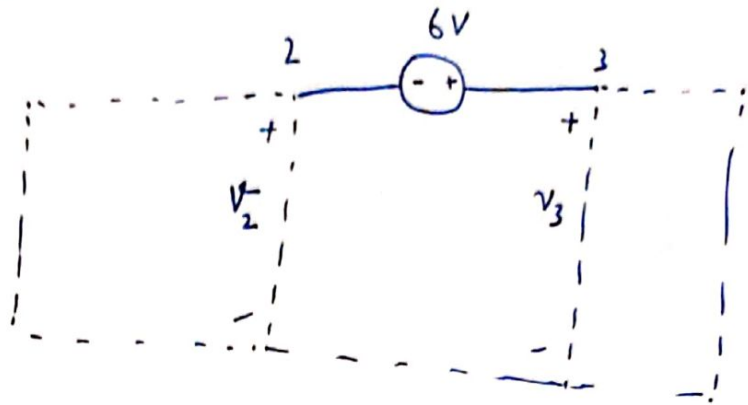

$$V_2 + 6 - V_3 = 0$$

$$V_3 = V_2 + 6; \quad \text{Also } V_1 = 14$$

$$\therefore 14 = \frac{7V_2 + 8(V_2 + 6)}{3}$$

$$7V_2 + 8V_2 + 48 = 42$$

$$15V_2 = -6$$

$$V_2 = \frac{-6}{15} = -0.4$$

$$V_2 = \frac{-2}{5} = -0.4V$$

$$V_2 = 0.4 \times 1000 \text{ mV}$$

$$V_2 = 400 \text{ mV}$$

$$\therefore V_3 = -0.4V + 6$$

$$V_3 = 5.6V$$

$$\therefore I' = \frac{5.6}{2} = 2.8A$$

$$I_1 = 2.8A$$