
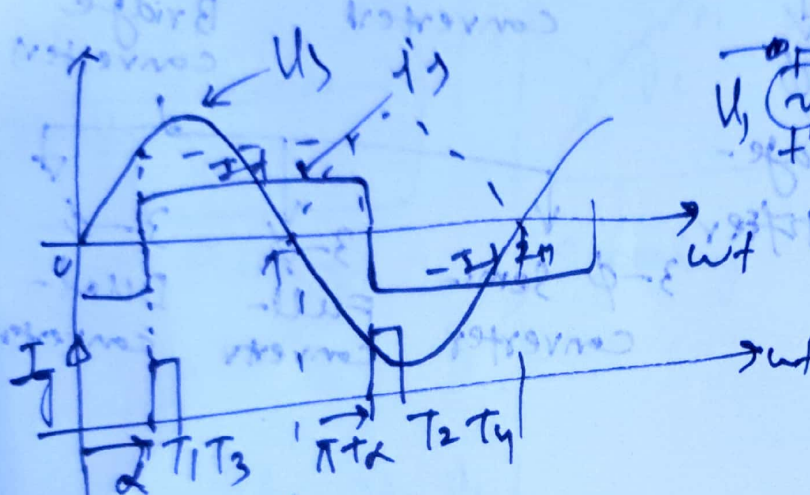





Effect of Free Wheeling Diode:

For Semi-converter: Inherent free wheeling

Full-converter:

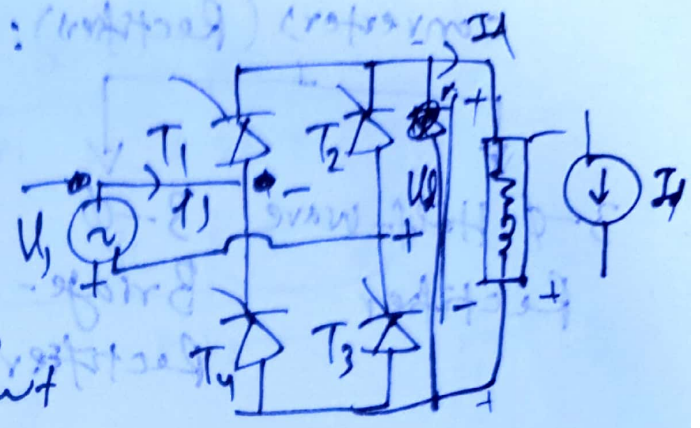


Without F.W.D.

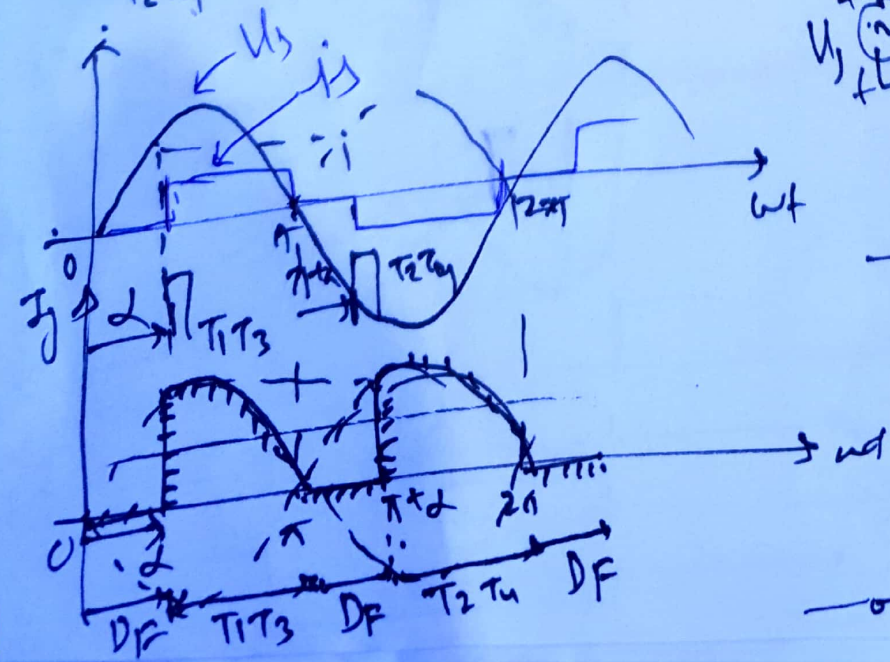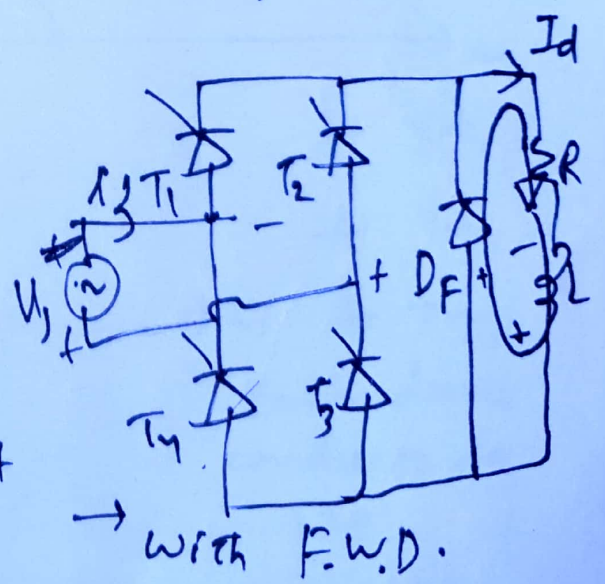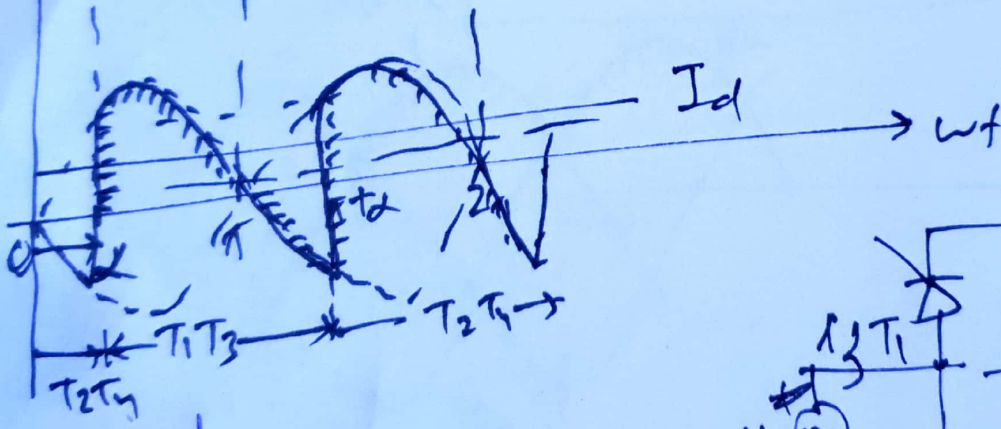

With F.W.D.

Three-phase conversion

Uncontrolled converters (Rectifiers)

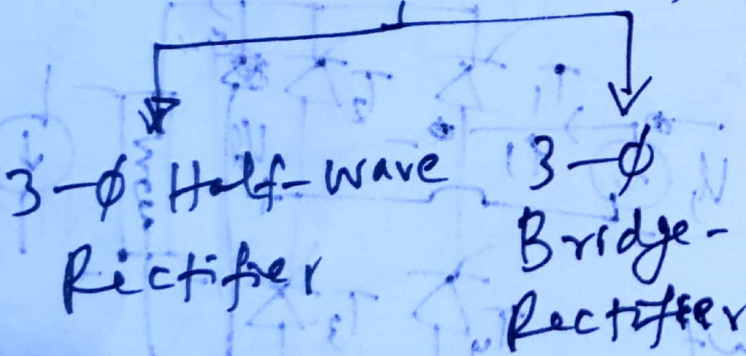

Phase-controlled converters

3- ϕ Half-wave converters

3- ϕ Bridge converters



3- ϕ Semi-converter

3- ϕ Full-converter

3- ϕ Dual-converter

3- ϕ Half-Wave Rectifier:

Power circuit Diagram

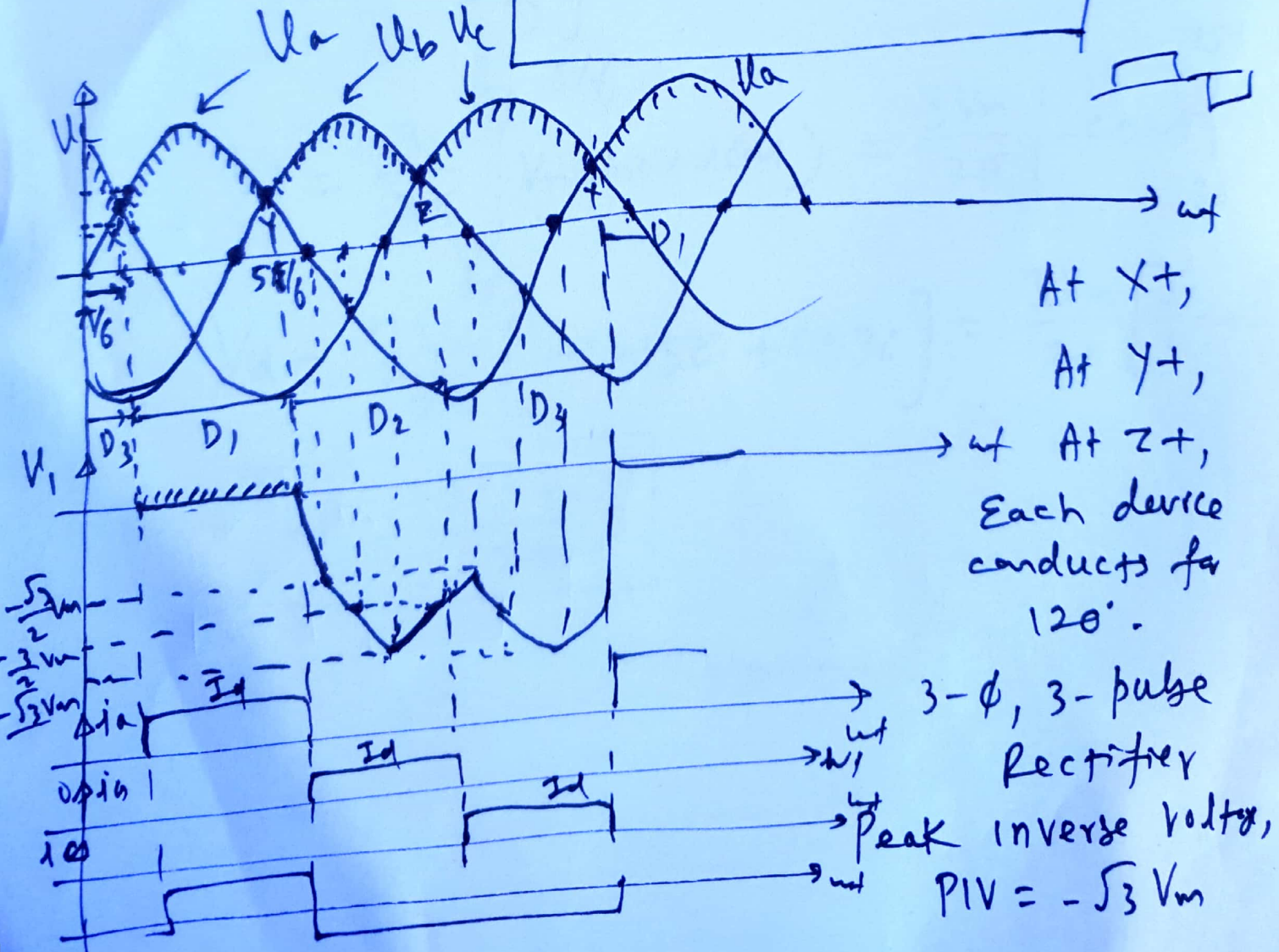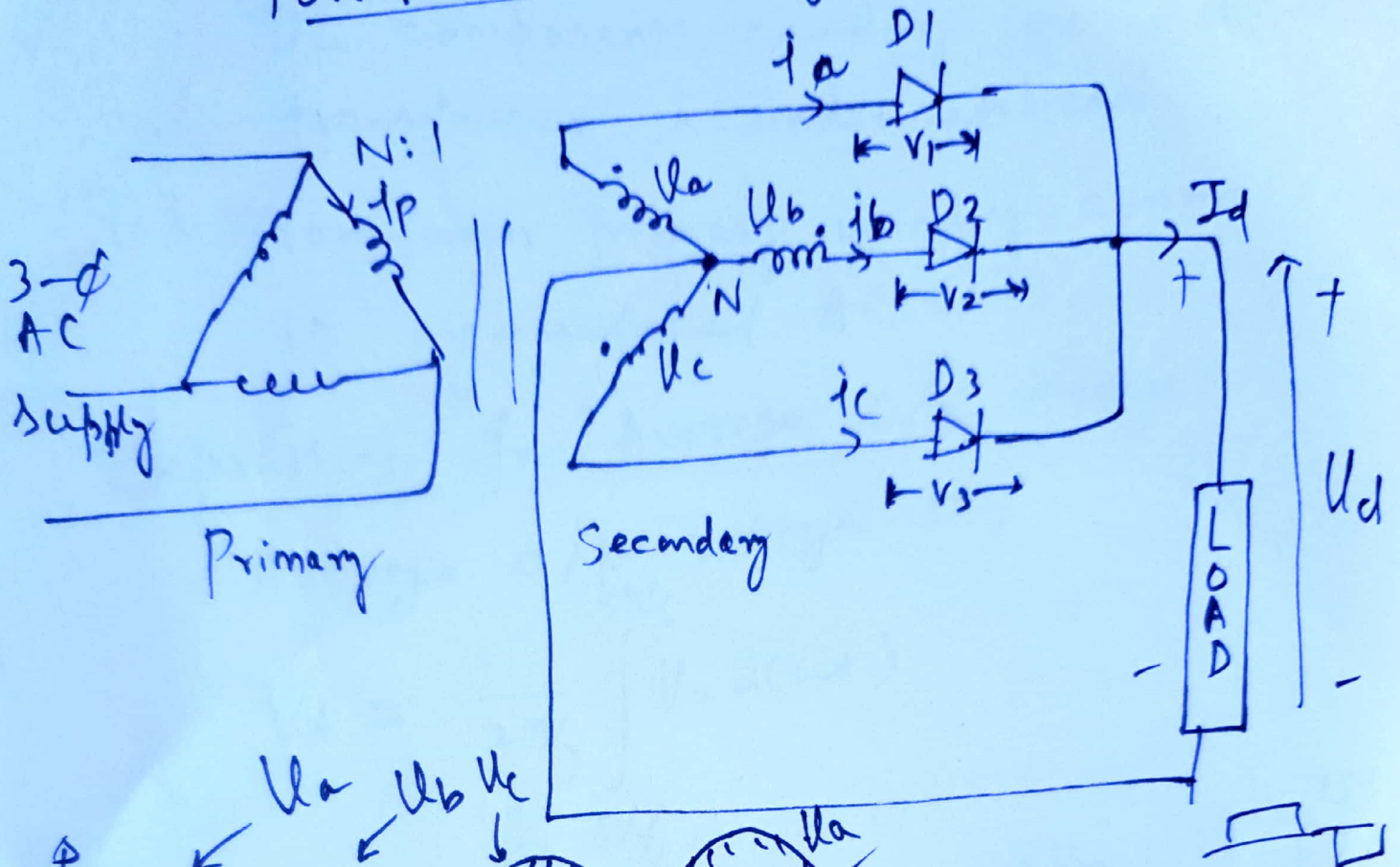

Drawbacks: i) Transformer secondary winding currents ~~to~~ contain strong DC components, leading to saturation & transformer is under-utilized;

ii) Transformer primary winding current is asymmetrical AC.

Expression for Average O/p voltage..


Average o/p voltage is,

$$V_d = \frac{1}{2\pi/3} \int_{\pi/6}^{5\pi/6} V_m \sin \omega t \, d(\omega t)$$

$$V_d = \frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} V_m \sin \omega t \, d(\omega t) = \frac{3V_m}{2\pi} \left[-\cos \omega t \right]_{\pi/6}^{5\pi/6}$$


$$V_d = \frac{3V_m}{2\pi} \left[-\cos 150^\circ + \cos 30^\circ \right] = \frac{3V_m}{2\pi} \left[\frac{\sqrt{3}}{2} + \frac{\sqrt{3}}{2} \right]$$
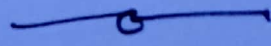
$$\Rightarrow \boxed{V_d = \frac{3\sqrt{3} V_m}{2\pi}}$$




3-φ Bridge Rectifier: $V_1 = V_a - V_c = V_{ac}$

$V_{Anode} = V_a$
 $V_{Cathode} = V_c$

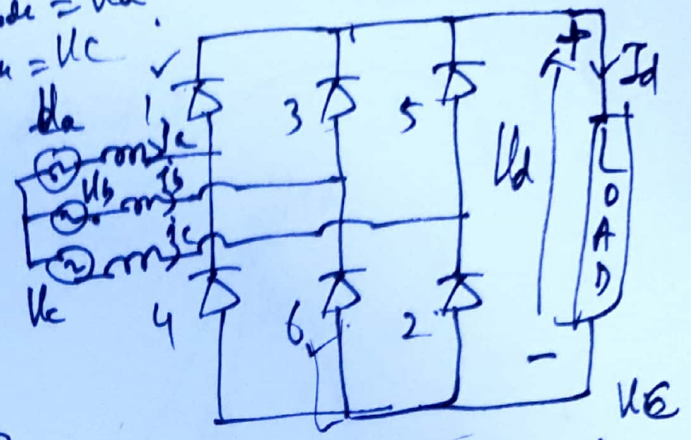


A device goes into conduction only when its commutation voltage becomes positive (i.e., when it is forward-biased).

Sequence of conduction is as:

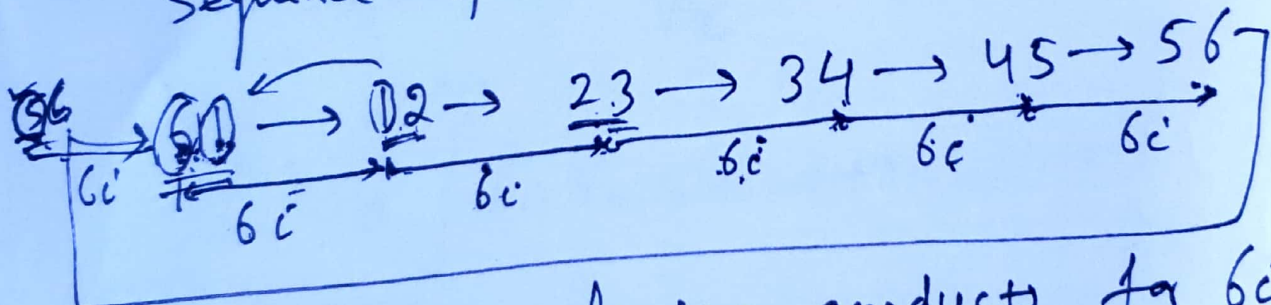

- Each pair of devices conducts for 60° .
- Each device conducts for 120° .

Device	Commutation Voltage
1	$V_{ac} =$
2	$V_{bc} =$
3	V_{ba}
4	V_{ca}
5	V_{cb}
6	V_{ab}

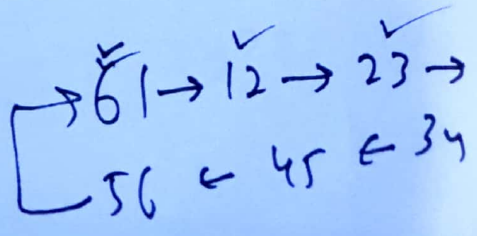

Expression for Average o/p voltage.


Average o/p voltage,

$$V_d = \frac{1}{\pi/3} \int_0^{\pi/3} \underline{u_{bc}} d(\omega t)$$

Taking u_{ba} as reference.

$$\therefore u_{ba} = \sqrt{3} V_m \sin \omega t$$
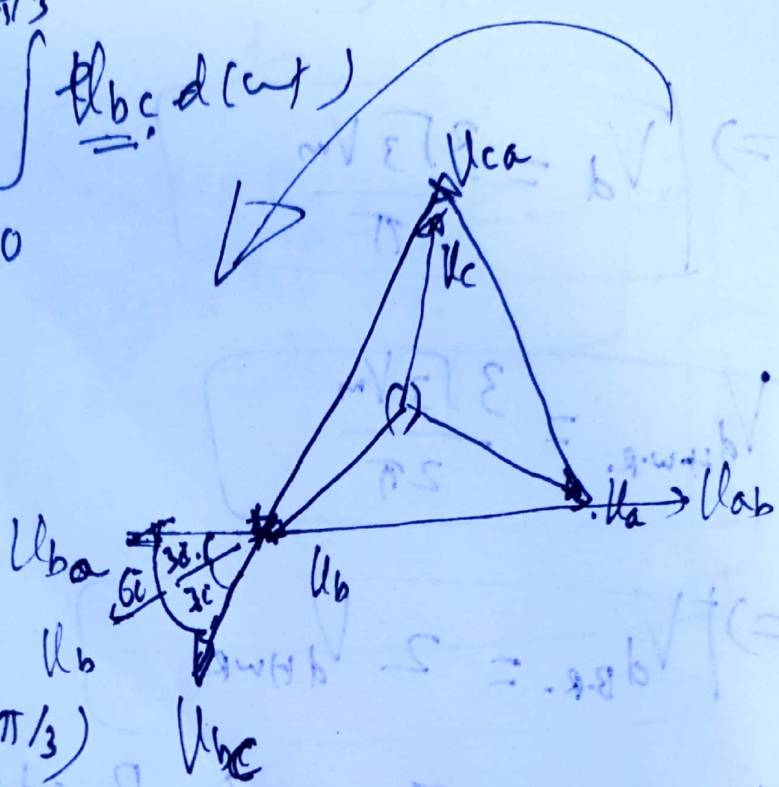
$$\therefore u_{bc} = \sqrt{3} V_m \sin(\omega t + \pi/3)$$



$$\therefore V_d = \frac{3}{\pi} \int_0^{\pi/3} \sqrt{3} V_m \sin(\omega t + \pi/3) d(\omega t)$$

$$= \frac{3\sqrt{3} V_m}{\pi} \left[-\cos(\omega t + \pi/3) \right]_0^{\pi/3}$$

$$= \frac{3\sqrt{3} V_m}{\pi} \left[-\cos(\pi/3 + \pi/3) + \cos \pi/3 \right]$$

$$= \frac{3\sqrt{3} V_m}{\pi} \left[-\cos 2\pi/3 + \cos \pi/3 \right]$$

$$V_d = \frac{3\sqrt{3} V_m}{\pi} \left[\frac{1}{2} + \frac{1}{2} \right]$$

$$\Rightarrow V_d = \frac{3\sqrt{3} V_m}{\pi}$$

$$V_{dHWR} = \frac{3\sqrt{3} V_m}{2\pi}$$

$$\Rightarrow V_{dB.R.} = 2 V_{dHWR}$$




Advantages of 3- ϕ Bridge Rectifier:

- i) Av. o/p voltage ~~is~~ double that produced by 3- ϕ Half-wave rectifier
- ii) Transformer secondary as well as primary currents are ~~greater~~ AC \rightarrow NO DC comp.
- iii) No transformer saturation & transformer utilization is better.

3- ϕ Phase-controlled converters:


(6)

3- ϕ Half-wave converters:

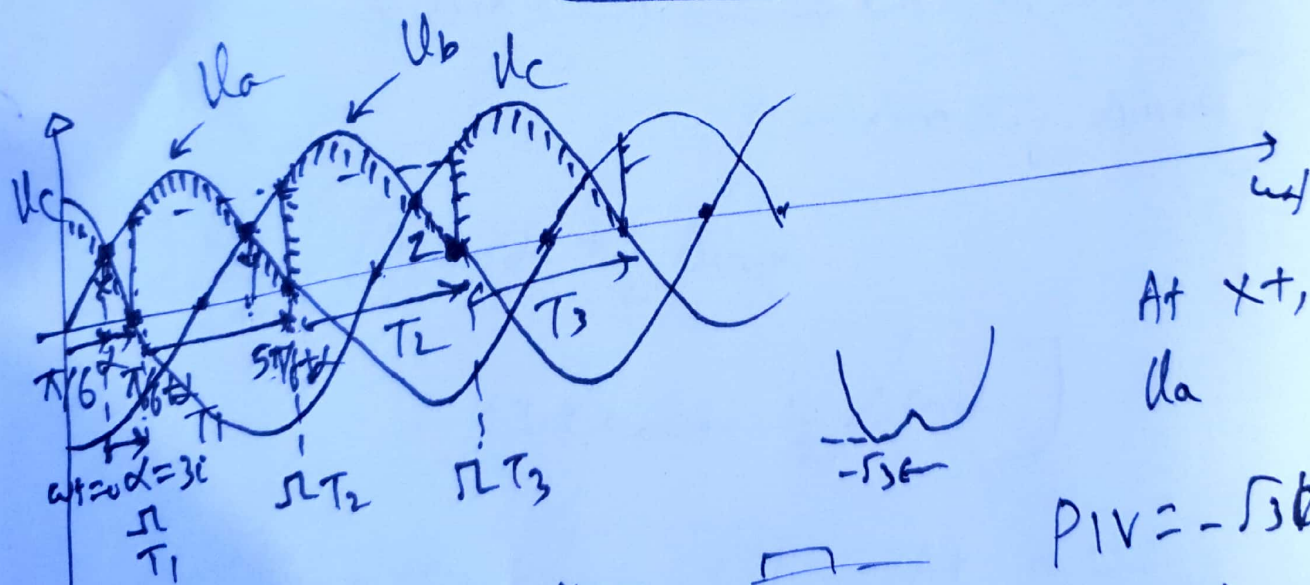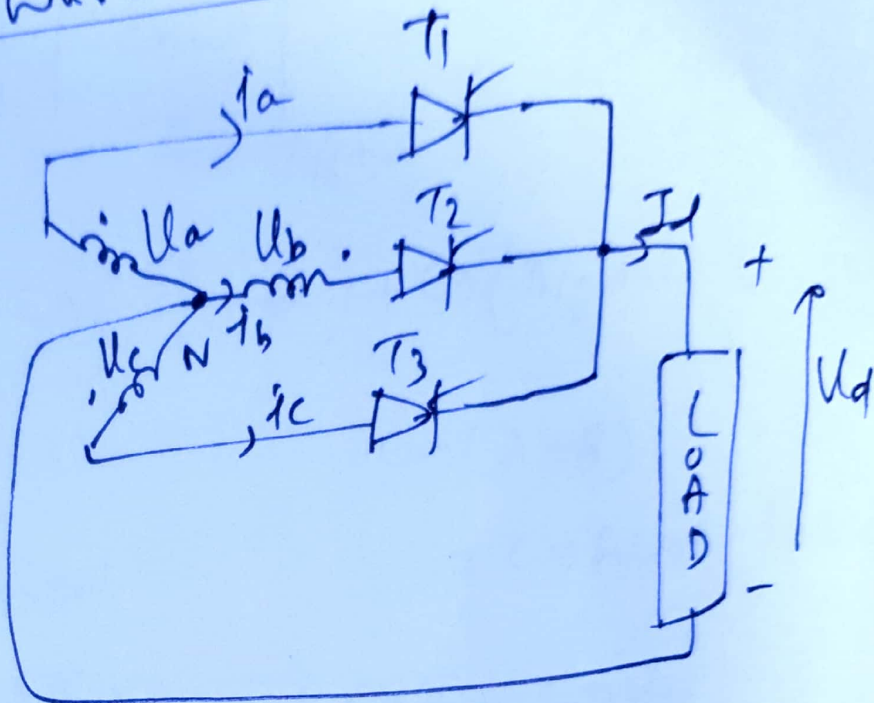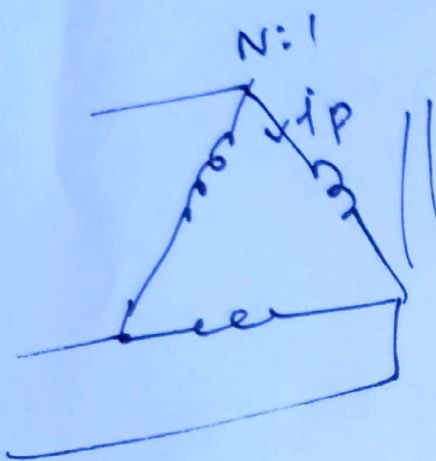

Average o/p voltage,
 $\frac{3\sqrt{3}V_m}{2\pi} \int_{\alpha}^{\pi} \sin(\omega t) d\omega t$
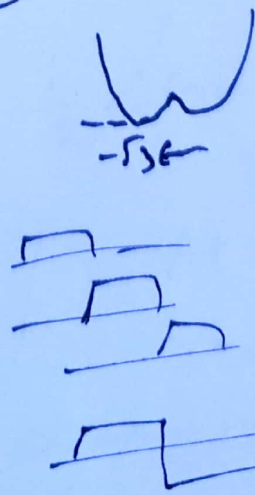
$$V_d = \frac{1}{2\pi/3} \int_{\pi/6}^{\pi} U_d d(\omega t)$$



At ωt ,
 U_a
 $PIV = -\sqrt{3}V_m$

Each device is on for $2\pi/3$ (120°)

(7)

$$V_d = \frac{3}{2\pi} \int_{\pi/6+\alpha}^{5\pi/6+\alpha} V_m \sin \omega t d(\omega t)$$

$$= \frac{3V_m}{2\pi} \left[-\cos \omega t \right]_{\pi/6+\alpha}^{5\pi/6+\alpha}$$

$$= \frac{3V_m}{2\pi} \left[-\cos \left(\frac{5\pi}{6} + \alpha \right) + \cos \left(\frac{\pi}{6} + \alpha \right) \right]$$

$$\cos(A+B)$$

$$= \cos A \cos B - \sin A \sin B$$

$$V_d = \frac{3V_m}{2\pi} \left[-\cos \frac{5\pi}{6} \cdot \cos \alpha \right.$$

$$+ \sin \frac{5\pi}{6} \sin \alpha + \cos \frac{\pi}{6} \cdot \cos \alpha$$

$$\left. - \sin \frac{\pi}{6} \cdot \sin \alpha \right]$$

$$= \frac{3V_m}{2\pi} \left[\frac{\sqrt{3}}{2} \cos \alpha + \frac{1}{2} \sin \alpha \right.$$


$$\left. + \frac{\sqrt{3}}{2} \cos \alpha - \frac{1}{2} \sin \alpha \right]$$

$$\therefore V_d = \frac{3\sqrt{3}V_m}{2\pi} \cos \alpha$$

$$\text{At } \alpha = 0,$$

$$\cos \alpha = \cos 0 = 1$$

When 1 is on
When 4 is on

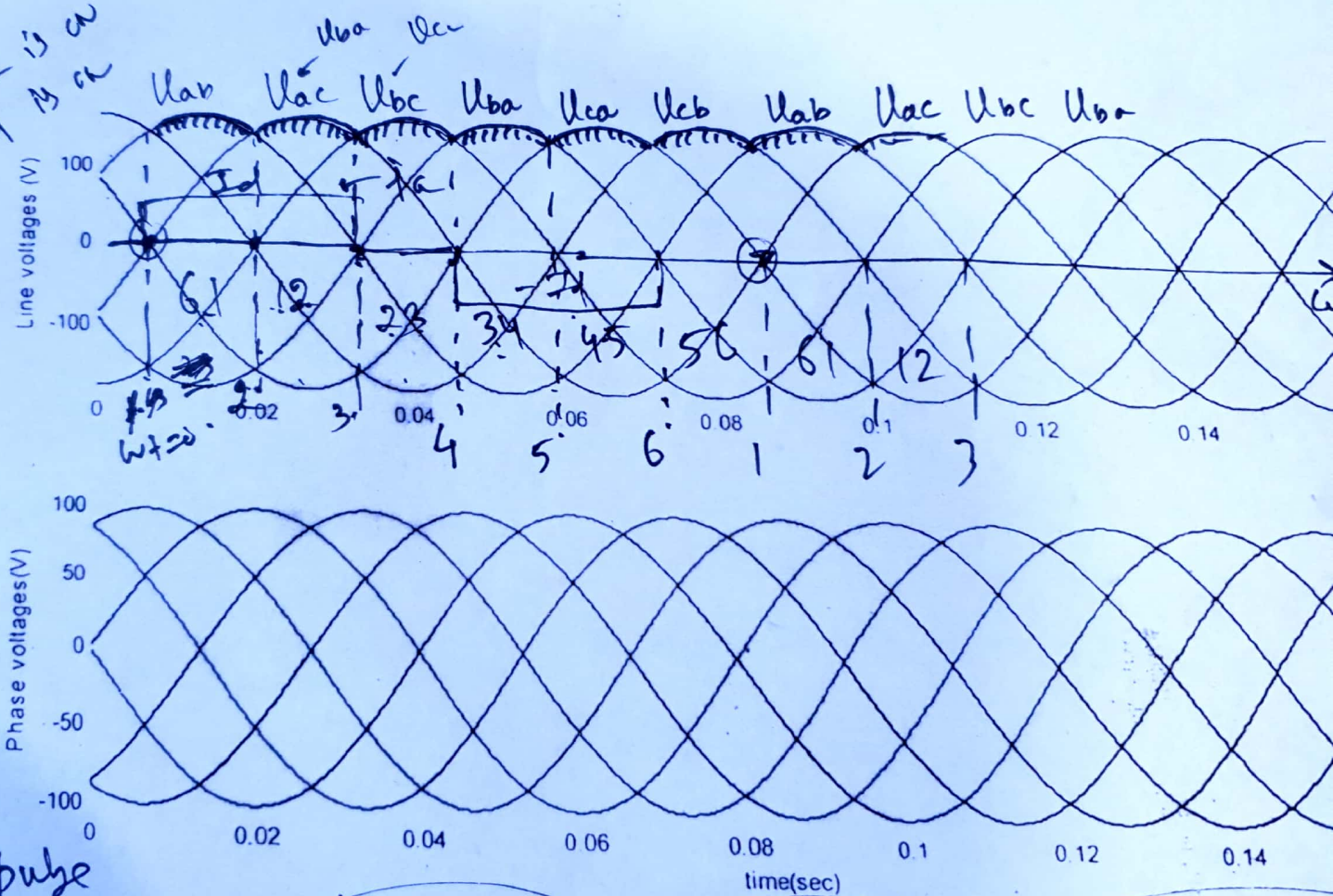

6-pulse
rectifier

